

Example

EE6

_____ : Convert the following from rectangular to polar form.

$$\bar{C} = -6 + j3$$

Solution

$$C = \sqrt{(-6)^2 + (3)^2} = \sqrt{45} = 6.71$$

$$\theta = \tan^{-1}\left(\frac{3}{6}\right)$$


$$= 26.57^\circ$$

$$\Rightarrow \phi = 180^\circ - 26.57^\circ$$

$$= 153.43^\circ$$

\(\therefore \bar{C}\) in polar form is:
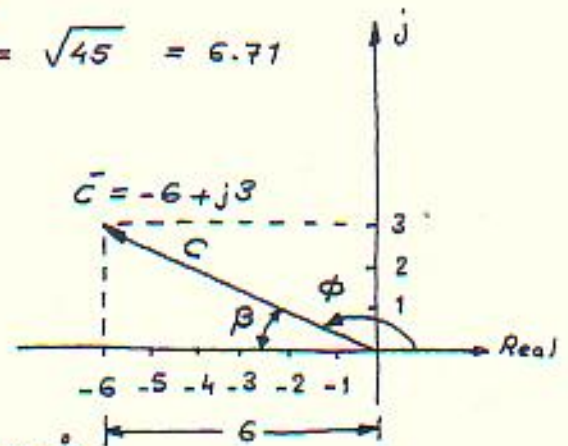
$$\bar{C} = C / \phi = 6.71 / 153.43^\circ$$



Example

_____ : Convert from polar to rectangular form.

$$\bar{C} = 10 / 230^\circ$$

Solution

_____ :

$$A = 10 \cos \beta$$

$$= 10 \cos (230^\circ - 180^\circ)$$

$$= 10 \cos 50^\circ$$

$$= 6.428$$

$$B = 10 \sin \beta$$


$$= 10 \sin (230^\circ - 180^\circ)$$

$$= 10 \sin 50^\circ$$

$$= 7.66$$

\(\therefore \bar{C}\) in rectangular form is

$$\bar{C} = -6.428 - j7.66$$

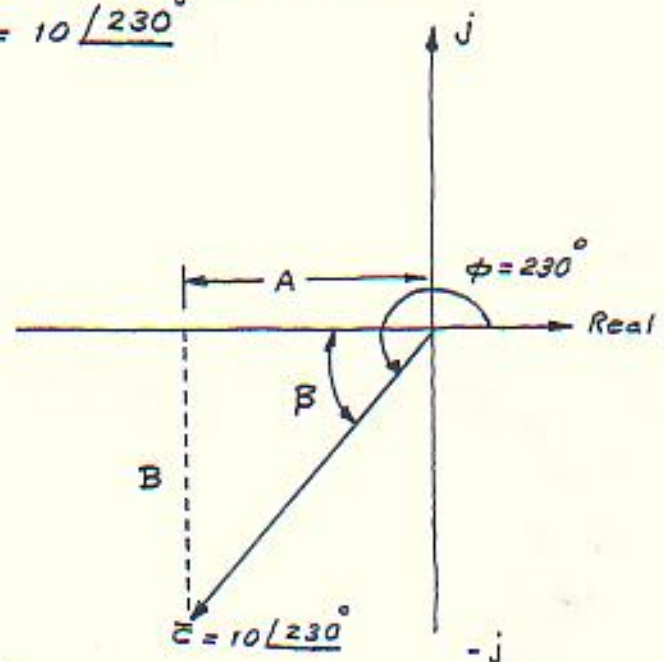


Mathematical Operations in the Polar Form

EE6


* Addition and Subtraction

 : Addition or subtraction cannot be performed in polar form unless the complex numbers have the same angle ϕ or differ only by multiples of 180°
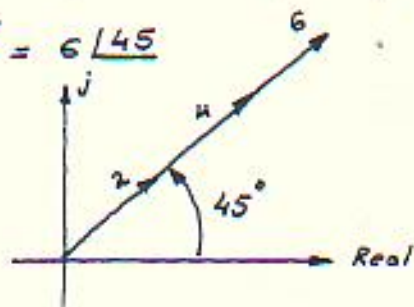
$$\text{Ex: } 2 \angle 45^\circ + 4 \angle 45^\circ = 6 \angle 45^\circ$$


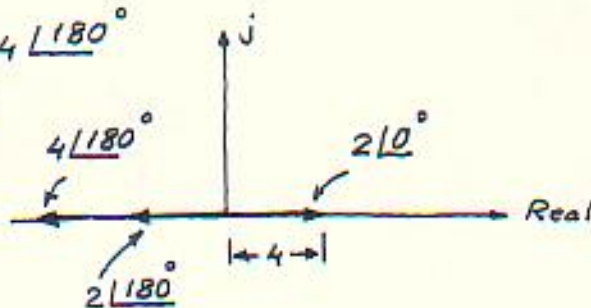
$$\begin{aligned} \text{Ex: } 2 \angle 0^\circ + 4 \angle 180^\circ \\ = 2 \angle 180^\circ \end{aligned}$$



* Multiplication

If we have two complex numbers

$$\bar{C}_1 = C_1 \angle \phi_1$$

$$\bar{C}_2 = C_2 \angle \phi_2$$

$$\text{Then } \bar{C}_1 \cdot \bar{C}_2 = C_1 C_2 \angle \phi_1 + \phi_2$$

$$\text{Ex: Find } \bar{C}_1 \bar{C}_2 \text{ , if } \bar{C}_1 = 5 \angle 20^\circ \text{ , and } \bar{C}_2 = -10 \angle 30^\circ$$

$$\bar{C}_1 \cdot \bar{C}_2 = (5)(-10) \angle 20^\circ + 30^\circ = \underline{\underline{-50 \angle 50^\circ}}$$

* Division

 : If we have two complex numbers

$$\bar{C}_1 = C_1 \angle \phi_1 \text{ and } \bar{C}_2 = C_2 \angle \phi_2 \text{ ,}$$

$$\text{Then } \frac{\bar{C}_1}{\bar{C}_2} = \frac{C_1}{C_2} \angle \phi_1 - \phi_2$$

$$\text{Ex: Given } \bar{C}_1 = 15 \angle 10^\circ \text{ and } \bar{C}_2 = 2 \angle 7^\circ \text{ , find } \frac{\bar{C}_1}{\bar{C}_2}$$

$$\frac{C_1}{C_2} = \frac{15}{2} \angle 10^\circ - 7^\circ = \underline{\underline{7.5 \angle 3^\circ}}$$

7. Series & Parallel AC Circuits


EE7

7.1 Series AC Circuits

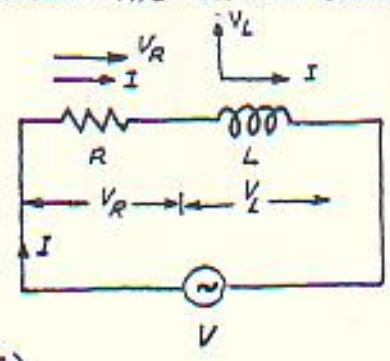7.1.1 AC Through R and L

Consider the circuit shown below;

V = the rms value of the applied voltage.
 I = the rms value of the resultant current.




$$\vec{V} = \vec{V}_R + \vec{V}_L$$

$\Rightarrow V_R = IR$ (in phase with I)
 $V_L = IX_L$ (leading I by 90°)

The vector diagram for these voltage drops can be obtained as:
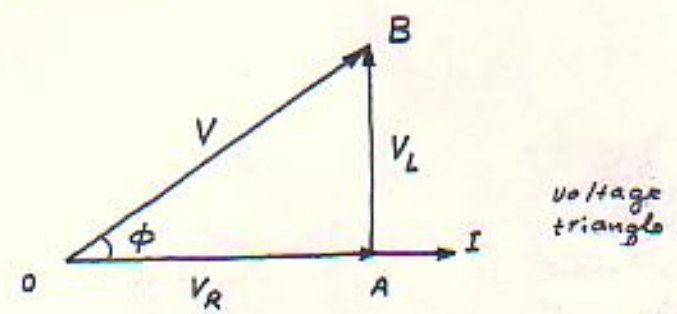
$$\begin{aligned} \Rightarrow V &= \sqrt{V_R^2 + V_L^2} \\ &= \sqrt{(IR)^2 + (IX_L)^2} \\ &= I\sqrt{R^2 + X_L^2} \end{aligned}$$



$$\Rightarrow I = \frac{V}{\sqrt{R^2 + X_L^2}} = \frac{V}{Z_T}$$

* The phase difference angle ϕ can be determined as:

$$\tan \phi = \frac{V_L}{V_R} = \frac{IX_L}{IR} = \frac{\omega L}{R}$$

$$\therefore \phi = \tan^{-1} \frac{X_L}{R}$$

$$\cos \phi = \frac{R}{Z_T}$$

$\Rightarrow Z$ is known as the impedance of the circuit

$$Z_T = \sqrt{R^2 + X_L^2}$$

$$Z_T^2 = R^2 + X_L^2$$


Impedance triangle

It is clear that the current I lags behind the applied voltage V by an angle (ϕ), then if:

$$\begin{aligned} v &= V_m \sin \omega t & \Rightarrow & i = I_m \sin (\omega t - \phi) \\ \text{where } I_m &= \frac{V_m}{Z} & \Rightarrow & v_R = I_m R \sin (\omega t - \phi) \\ & & \Rightarrow & v_L = I_m X_L \sin (\omega t - \phi + 90^\circ) \end{aligned}$$

* In phasor notation

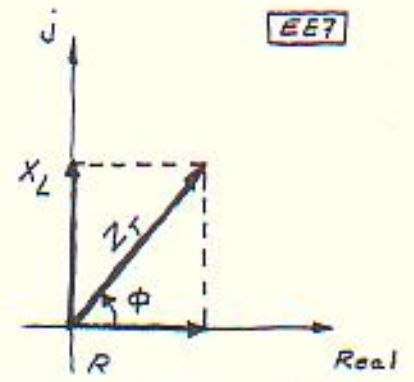
$$\begin{aligned} \bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 \\ &= R \angle 0^\circ + X_L \angle 90^\circ \\ \Rightarrow \therefore \bar{Z}_T &= R + jX_L \end{aligned}$$



Impedance diagram

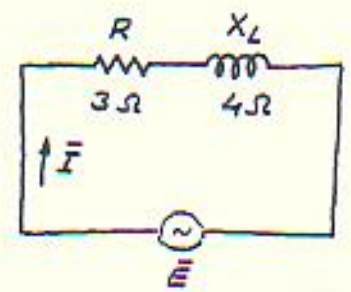
Example

For the circuit shown, determine the total impedance and draw the impedance diagram



Solution
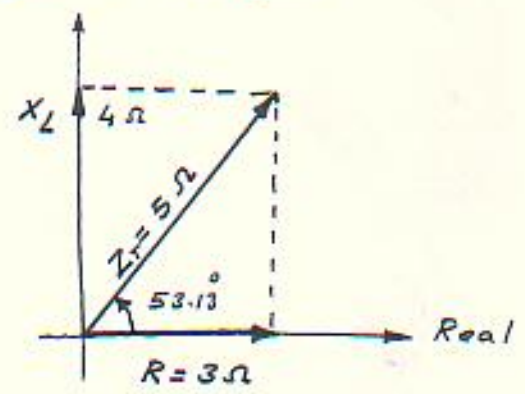
$$\begin{aligned} \bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 = R \angle 0^\circ + X_L \angle 90^\circ = R + jX_L \\ &= 3 + j4 \\ \Rightarrow \therefore \bar{Z}_T &= 5 \angle 53.13^\circ \end{aligned}$$




Note that, the angle ϕ ($= 53.13^\circ$ in this example) is always positive in the impedance diagram.

$$\begin{aligned} \phi &= \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{4}{3} \\ &= 53.13^\circ \end{aligned}$$

The phasor diagram

The phasor diagram of the voltages of the RL series circuit can be as shown:
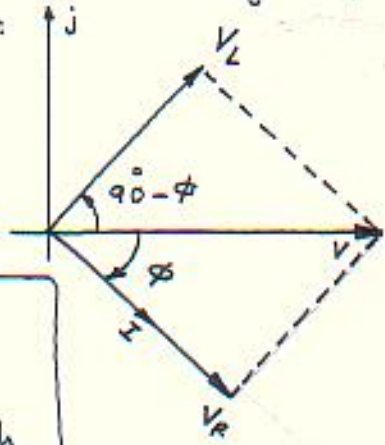
$$\begin{aligned} \bar{V} &= \bar{V}_R + \bar{V}_L = \bar{I}R + \bar{I}X_L \\ &= IR \angle -\phi + IX_L \angle 90-\phi \end{aligned}$$



phasor diagram

The total power (average power) in (Watts) delivered to the circuit is given by the product of V and the component of the current I which is in phase with the applied voltage V

كذلك تسمى بالقدرة الحقيقية (true power)

⇒ Then:

$$P_T = VI \cos \phi$$

Watts

⇐ where $\cos \phi$ is the power factor

* The power factor

The power factor can be defined as the cosine of the angle (lead or lag) between the current and voltage;

$$\Rightarrow \text{Power factor} = \cos \phi$$

② or it may be defined as the ratio $\frac{R}{Z}$ (see the impedance triangle)

③ or it may be defined as the ratio $\frac{\text{true power}}{\text{apparent power}}$

$$\Rightarrow \text{Power factor} = \frac{\text{true power}}{\text{apparent power}} \Rightarrow \frac{\text{Watts}}{\text{Volt-ampere}}$$

* Active and Reactive Components of the Circuit Current

* The active component is that which is in phase with the applied voltage V, i.e. $(I \cos \phi)$; it is also called the wattful component.

from the phasor diag. ⇒

* The reactive component is that which is in quadrature with V, i.e. $(I \sin \phi)$; it is also called the wattless component or the idle component.

⇒ According to these definitions, we have also two components of power each relating its corresponding current component

* Active, Reactive and Apparent Power (The Power Triangle)

* The Apparent Power

It is the product of the rms values of the applied voltage and the circuit current

Apparent power = S = VI = (IZ). I = I^2 Z
volt-ampere (VA)

* The Active Power

It is the power which is actually dissipated in the circuit resistance.

Active power = P = I^2 R = VI cos phi watts (W)

* The Reactive Power


It is the power developed in the inductive reactance of the circuit.

Reactive Power = Q = I^2 X_L = I^2 (Z sin phi)

Q = VI sin phi
Volt-ampere reactive (VAR)

These three powers are shown in the power triangle:
From the power triangle:


S^2 = P^2 + Q^2
or
S = sqrt(P^2 + Q^2)

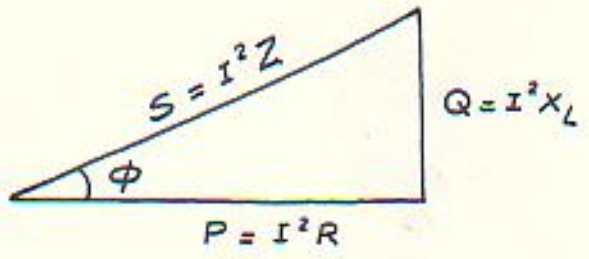

The power triangle

* The quality factor of the Coil

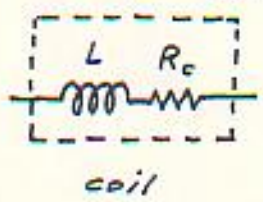It is defined as the reciprocal of the power factor of the coil. Hence:



Q factor = 1 / power factor = 1 / cos phi = Z / R_c = sqrt(R_c^2 + X_L^2) / R_c
if R_c is too small compared with X_L, then:


Q_factor = X_L / R_c

EE?

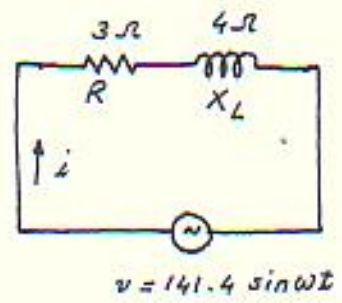Example

For the circuit shown, draw the phasor diagram of the voltages across each element and the applied voltage, and determine:

- The power factor.
- The active and reactive power.
- The apparent power.



Solution

* $\therefore v = 141.4 \sin \omega t \Rightarrow \bar{V} = 100 \angle 0^\circ$

* $\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 = R + jX_L$
 $= 3 + j4$
 $= 5 \angle 53.13^\circ$

* The current $\bar{I} \Rightarrow \bar{I} = \frac{\bar{V}}{\bar{Z}_T}$
 $\therefore \bar{I} = \frac{100 \angle 0^\circ}{5 \angle 53.13^\circ} = 20 \angle -53.13^\circ$

* The voltage drops \bar{V}_R and \bar{V}_L :

$\bar{V} = \bar{V}_R + \bar{V}_L$


$\therefore \bar{V} = 36 - j48 + 64 - j48$
 $= 100$
 $= 100 \angle 0^\circ$

$\Rightarrow \bar{V}_R = \bar{I}R = (20 \angle -53.13^\circ)(3)$
 $= 60 \angle -53.13^\circ$
 $= 36 - j48$

$\Leftarrow \bar{V}_L = \bar{I}X_L = (20 \angle -53.13^\circ)(4 \angle 90^\circ)$
 $= 80 \angle 36.87^\circ$
 $= 64 + j48$

كما في الصورة السابقة

* The phasor diagram

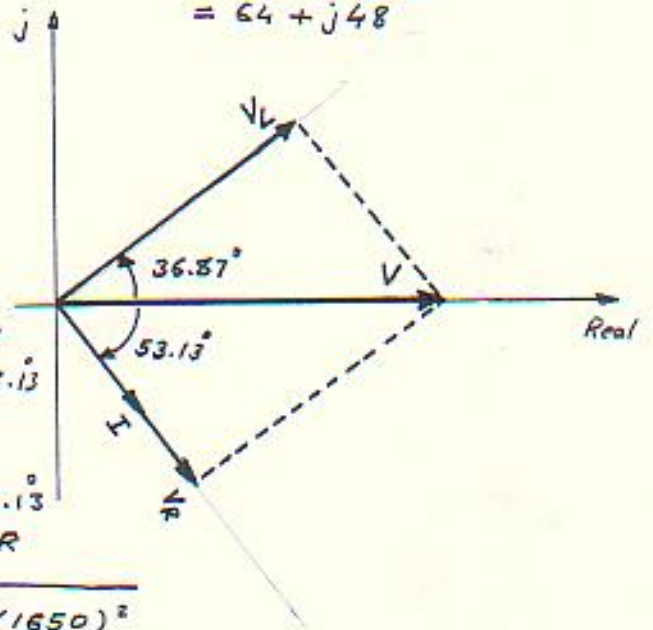

* Powers

active power (real) (average)

$P = I^2 R = (20)^2 (3) = 1200 \text{ W}$
 or $P = VI \cos \phi = (100)(20) \cos 53.13^\circ$
 $= 1200 \text{ W} = 1.2 \text{ kW}$

reactive power

$Q = VI \sin \phi = (100)(20) \sin 53.13^\circ$
 $= 1600 \text{ VAR} = 1.6 \text{ kVAR}$

$S = \sqrt{P^2 + Q^2} = \sqrt{(1200)^2 + (1600)^2}$
 $= 1968 \text{ VA} = 1.968 \text{ kVA}$

* The power factor: $P.f = \cos \phi = \cos 53.13^\circ = 0.6 \text{ lagging}$

اعتباراً على التيار بالنسبة في التوليد

7.1.2 AC Through R and C

Consider the circuit shown, where

V = rms value of the applied voltage.
 I = rms value of the resultant current.

$$V_R = IR \quad (\text{in phase with } I)$$

$$V_C = IX_C \quad (\text{lagging } I \text{ by } 90^\circ)$$

* In Vector Notations:

$$\bar{V} = \sqrt{\bar{V}_R^2 + \bar{V}_C^2}$$

$$= \sqrt{I^2 R^2 + I^2 X_C^2}$$

$$= I \sqrt{R^2 + X_C^2}$$

$$\text{or } I = \frac{V}{\sqrt{R^2 + X_C^2}} = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \frac{X_C}{R}$$

$$\therefore \text{p.f.} = \cos \phi = \frac{R}{Z}$$

It is clear that I lead V by an angle ϕ . Hence if:

$$v = V_m \sin \omega t$$

then:

$$i = I_m \sin(\omega t + \phi)$$

so that the current i lead the applied voltage v by an angle ϕ , and

$$V_R = I_m R \sin(\omega t + \phi)$$

$$V_C = I_m X_C \sin(\omega t + \phi - 90^\circ)$$





* The phasor diagram of the voltages of the series RC circuit can be as shown:

$$\bar{V} = V \angle 0$$

$$\bar{I} = I \angle \phi$$

$$\bar{V}_R = V_R \angle \phi$$
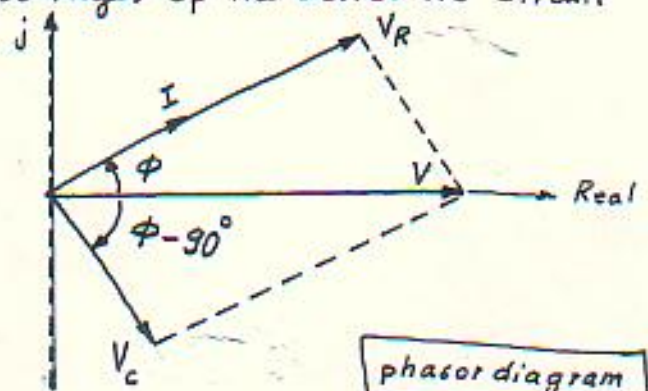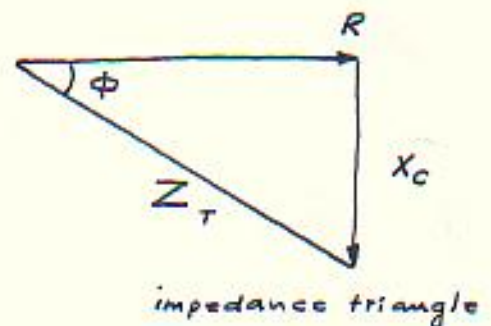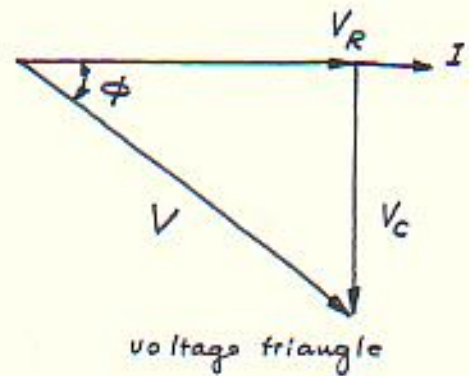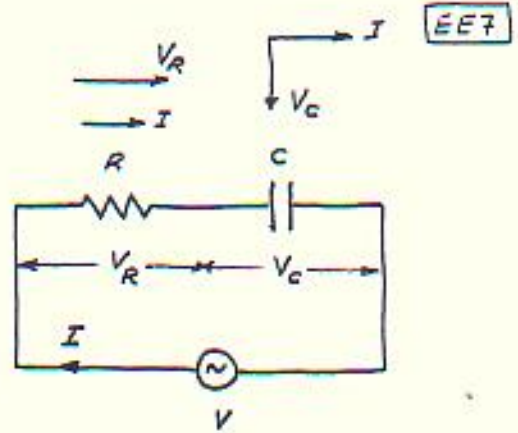
$$\bar{V}_C = V_C \angle \phi - 90^\circ$$



* The impedance diagram


EE7

in phasor notation

$$\begin{aligned} \bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 = R \angle 0^\circ + X_C \angle -90^\circ \\ &= R - jX_C \end{aligned}$$

$$\begin{aligned} \therefore \bar{Z}_T &= \sqrt{R^2 + X_C^2} \\ &= Z_T \angle \phi \end{aligned}$$

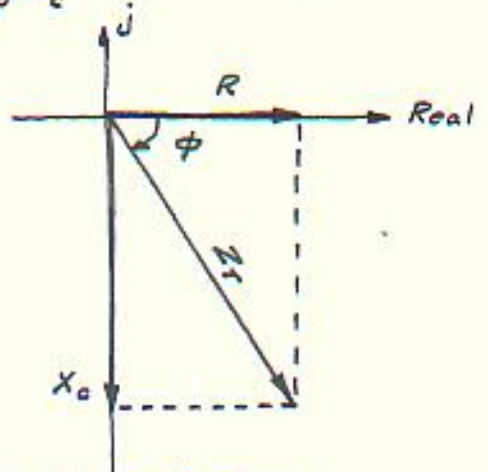
⇒ Note that ϕ is always negative for RC circuits.



Example

For the circuit shown, draw the phasor diagram.

$R=6\Omega$ $X_C=8\Omega$

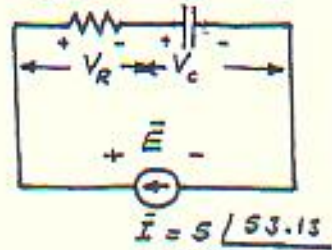

Solution

$$\begin{aligned} * \bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 \\ &= 6 \angle 0^\circ + 8 \angle -90^\circ \\ &= 6 - j8 = 10 \angle -53.13^\circ \end{aligned}$$

$$\begin{aligned} * \bar{E} ? \quad \bar{E} &= \bar{I} \bar{Z}_T = (5 \angle 53.13^\circ)(10 \angle -53.13^\circ) \\ &= 50 \angle 0 \end{aligned}$$


$$\begin{aligned} \bar{V}_R ? \quad \bar{V}_R &= \bar{I} R = (5 \angle 53.13^\circ)(6) \\ &= 30 \angle 53.13^\circ \end{aligned}$$

$$\begin{aligned} \bar{V}_C ? \quad \bar{V}_C &= \bar{I} X_C = (5 \angle 53.13^\circ)(8 \angle -90^\circ) \\ &= 40 \angle -36.87^\circ \end{aligned}$$

* you can find that:

$$\bar{E} = \bar{V}_R + \bar{V}_C$$

using the above values.

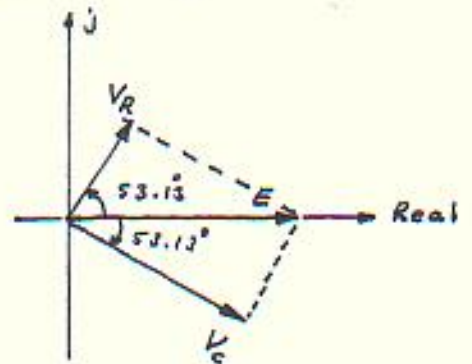

* Similarly, as in the case of series RL circuit, the active (average or true) power, reactive power can be determined.

* The active power P is

$$P = VI \cos \phi$$

$$P = I^2 R$$

* The reactive power Q is:

$$Q = VI \sin \phi$$

$$Q = I^2 X_c$$

* and the apparent power $S = \sqrt{P^2 + Q^2}$

* Dielectric Loss and the Power Factor of a Capacitor

* A pure (ideal) capacitor is one in which there are no losses and whose current lead the voltage by 90° as shown:

* In practice, it is impossible to get such a capacitor although close approximation is achieved by proper design.

* In every capacitor, there is always some dielectric loss, and hence absorbs part of the power from the circuit. Due to this loss, the phase angle is somewhat less than 90°.

* This dielectric loss appears as heat
* ψ is the phase difference given by:


$$\psi = 90^\circ - \phi$$

where ϕ is the actual phase angle.

* Since ψ is generally small $\Rightarrow \sin \psi = \psi$

$$\therefore \tan \psi = \psi = \cos \phi$$

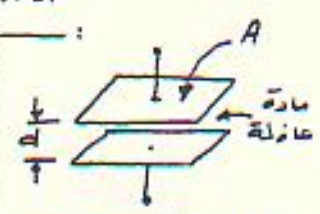
* It should be noted that dielectric loss increases with the frequency of the applied voltage.




For parallel-plate capacitor

$$C = \epsilon \frac{A}{d}$$

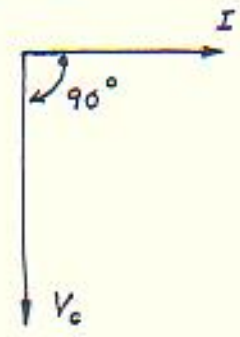- C = capacitance (F)
- ϵ = dielect constant
- A = Area of plate m^2
- d = Separation m



V_c and I for ideal (pure) capacitor,

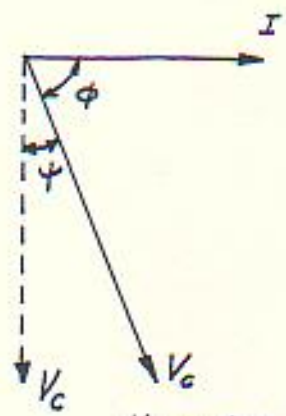


V_c and I for Actual capacitor.

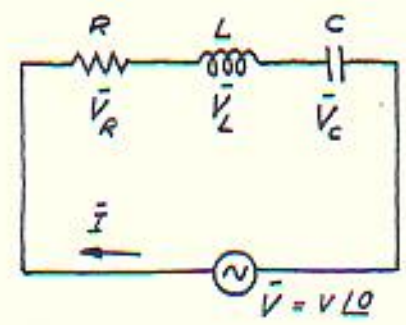7.2.3 AC Through RLC series circuit:

EE7

$$\begin{aligned} \bar{Z} &= R + jX_L - jX_C \\ &= R + j(X_L - X_C) = Z \angle \phi \end{aligned}$$



$$\bar{I} = \frac{V \angle 0}{Z \angle \phi} = I \angle -\phi$$

$$\begin{aligned} \bar{V}_R &= \bar{I} R = (I \angle -\phi) (R \angle 0^\circ) \\ &= IR \angle -\phi \end{aligned}$$

$$\begin{aligned} X_L &= \omega L \\ X_C &= \frac{1}{\omega C} \end{aligned}$$


$$\bar{V}_L = \bar{I} X_L = (I \angle -\phi) (X_L \angle 90^\circ) = I X_L \angle 90^\circ - \phi$$

$$\bar{V}_C = \bar{I} X_C = (I \angle -\phi) (X_C \angle -90^\circ) = I X_C \angle -(90^\circ + \phi)$$

* The impedance diagram:

$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

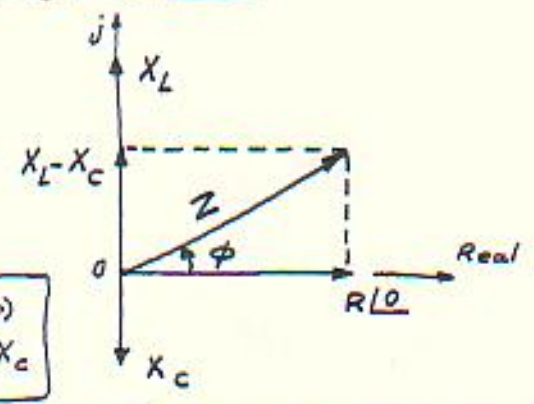The angle ϕ may be (+ve) or (-ve) depending on the values of X_L and X_C




impedance phasor diagram for $X_L > X_C$

* The voltage phasor diagram

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$
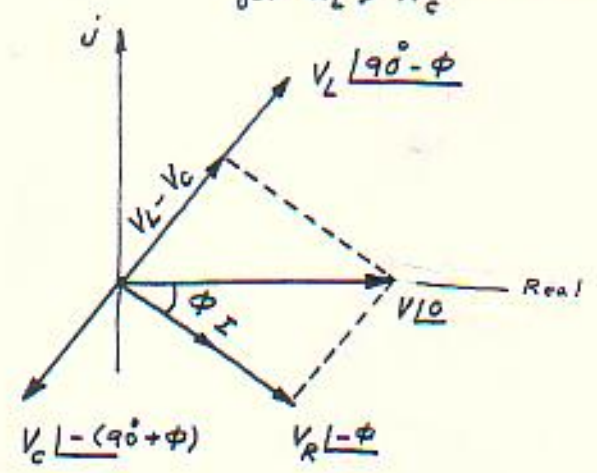
$$\therefore \bar{V} = \bar{I} R + \bar{I} X_L + \bar{I} X_C$$



* The active, reactive and the apparent powers can be determined as mentioned previously.


* When $X_L > X_C \Rightarrow X_L - X_C = (+ve) \Rightarrow \phi = \text{positive}$ in the impedance diagram.

* When $X_L < X_C \Rightarrow X_L - X_C = (-ve) \Rightarrow \phi = (-ve)$ in the voltage phasor diagram. so $\phi \Rightarrow (-ve)$ in the impedance diagram, $\phi = (+ve)$ in the phasor diagram.

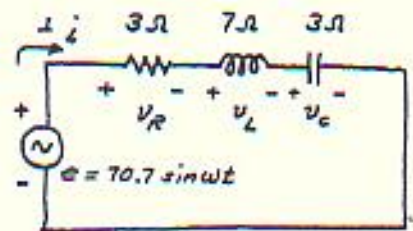Example

_____ : For the circuit shown, determine :

- \bar{Z}_T , and draw the impedance diagram.
- \bar{I} , \bar{V}_R , \bar{V}_L , \bar{V}_C in the phasor domain, and draw the phasor diagram.
- i , v_R , v_L , v_C in the time domain.
- The power factor of the circuit.
- The active, reactive and the apparent powers.





Solution

_____ : In phasor notation the circuit is redrawn as :

$$\begin{aligned} * \quad \bar{Z}_T &= \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3 \\ &= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\ &= 3 + j7 - j3 \\ &= 3 + j4 \end{aligned}$$

$$\therefore \bar{Z}_T = 5 \angle 53.13^\circ$$

* The impedance diagram is \Rightarrow

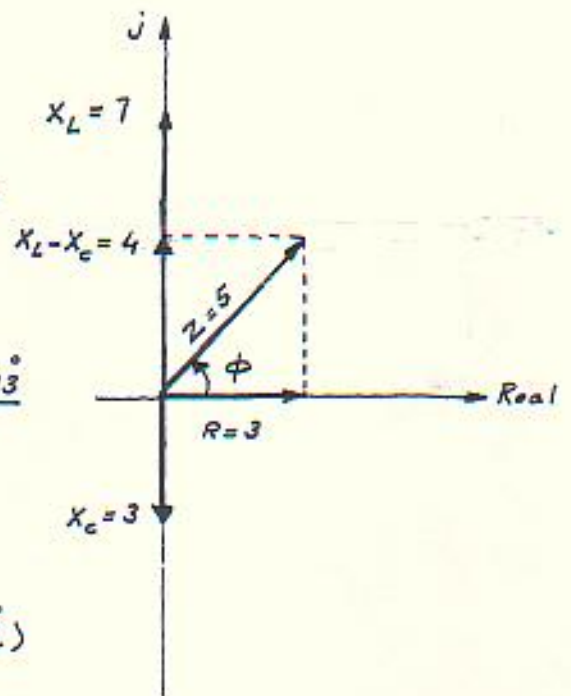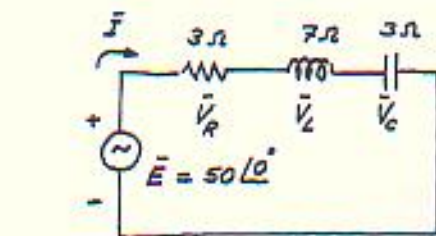


$$\bar{I} = \frac{\bar{E}}{\bar{Z}} = \frac{50 \angle 0^\circ}{5 \angle 53.13^\circ} = 10 \angle -53.13^\circ$$

$$\begin{aligned} \bar{V}_R &= \bar{I}R = (10 \angle -53.13^\circ)(3 \angle 0^\circ) \\ &= 30 \angle -53.13^\circ \end{aligned}$$

$$\begin{aligned} \bar{V}_L &= \bar{I}X_L = (10 \angle -53.13^\circ)(7 \angle 90^\circ) \\ &= 70 \angle 36.87^\circ \end{aligned}$$

$$\begin{aligned} \bar{V}_C &= \bar{I}X_C = (10 \angle -53.13^\circ)(3 \angle -90^\circ) \\ &= 30 \angle -143.13^\circ \end{aligned}$$

* The phasor diagram

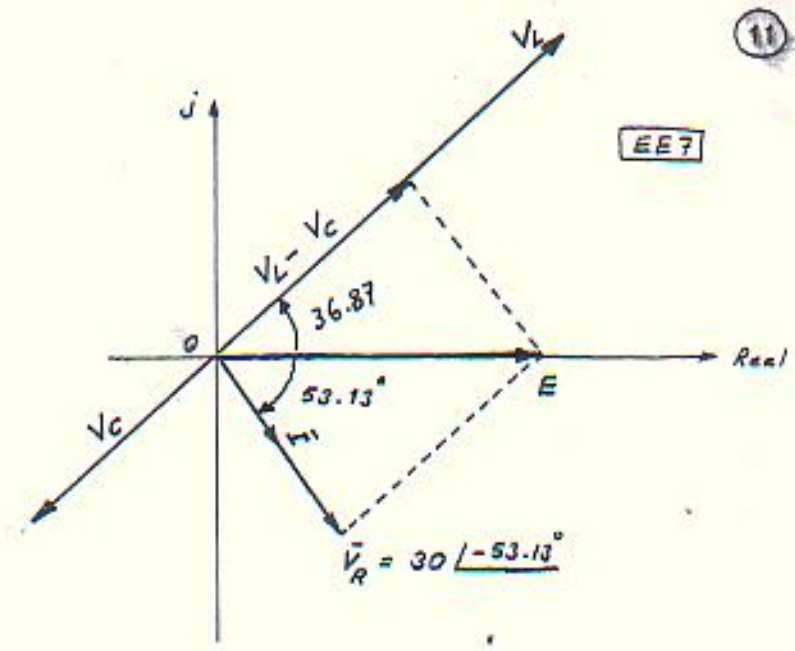

* The time domain

$$\begin{aligned}
 i &= \sqrt{2} (10) \sin(\omega t - 53.13^\circ) = 14.14 \sin(\omega t - 53.13^\circ) \\
 v_R &= \sqrt{2} (30) \sin(\omega t - 53.13^\circ) = 42.42 \sin(\omega t - 53.13^\circ) \\
 v_L &= \sqrt{2} (70) \sin(\omega t + 36.87^\circ) = 98.98 \sin(\omega t + 36.87^\circ) \\
 v_C &= \sqrt{2} (30) \sin(\omega t - 143.13^\circ) = 42.42 \sin(\omega t - 143.13^\circ)
 \end{aligned}$$

* The total power

$$P_T = VI \cos \phi = (50)(10) \cos 53.13^\circ = \underline{300 \text{ W}}$$

or $P_T = I^2 R = (10)^2 (3) = \underline{300 \text{ W}}$

from the voltage phasor diagram

* The power factor

$$\begin{aligned}
 \text{p.f.} &= \cos \phi = \cos 53.13^\circ \\
 &= \underline{0.6 \text{ lagging}}
 \end{aligned}$$


or $\text{p.f.} = \cos \phi = \frac{R}{Z_T} = \frac{3}{5} = 0.6 \text{ lagging}$

- P ⇒ Active power = true power = $VI \cos \phi = (50)(10) \cos 53.13^\circ = 300 \text{ W}$
- Q ⇒ Reactive power = $Q = VI \sin \phi = (50)(10) \sin 53.13^\circ = 400 \text{ VAR}$
- S ⇒ Apparent power = $S = \sqrt{P^2 + Q^2} = \sqrt{(300)^2 + (400)^2} = 500 \text{ VA}$

∴ The power triangle

$$\bar{S} = P + jQ$$

\bar{S} ⇒ Complex apparent power.

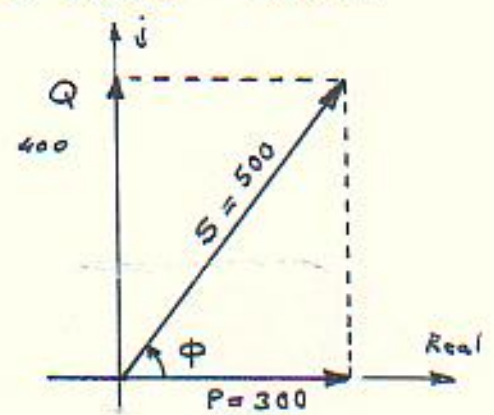

7.2 Parallel AC Circuits

EE7


* Admittance and Susceptance

- In the dc circuit analysis, we had used the term conductance to represent the reciprocal of the resistance R ; i.e:

$$G = \frac{1}{R} \quad \text{where } G \text{ is the conductance}$$

The total conductance of the parallel circuit is then found by adding the conductance of each branch.

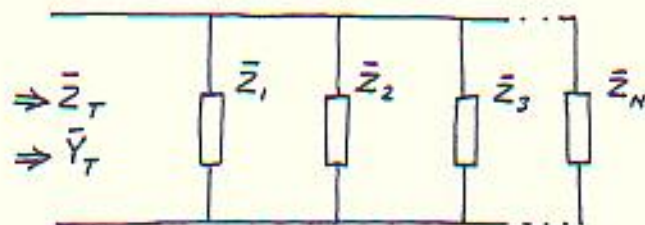- In AC circuit analysis, we define the admittance (\bar{Y}) as equal to $1/\bar{Z}$. For the parallel circuit shown:



* The total admittance \bar{Y}_T :

$$\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 + \dots + \bar{Y}_N$$

then since $\bar{Y} = \frac{1}{\bar{Z}}$; so the total impedance \bar{Z}_T :

$$\frac{1}{\bar{Z}_T} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3} + \dots + \frac{1}{\bar{Z}_N}$$

- As mentioned earlier, for 2 branches parallel ac circuit, then:

$$\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$$

- Also for 3 parallel branches;

$$\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2 \bar{Z}_3}{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}$$

⊕ IN GENERAL, we have: $\bar{Z}_T = R \mp jX$, the

$$\bar{Y}_T = \frac{1}{R} \mp \frac{j}{X} = \boxed{G \pm jB}$$

where: $G \Rightarrow$ Conductance $= \frac{1}{R}$
 $B \Rightarrow$ Susceptance $= \frac{1}{X}$


(Siemens, S) نسيان جوفت
(Siemens, S)

Example

EE7

For the circuit shown;

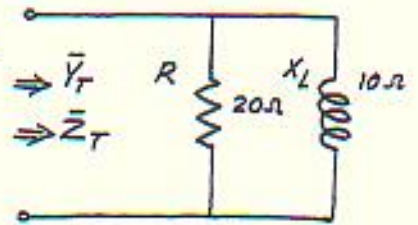- a. Determine the admittance of each branch.
- b. Find the input admittance.
- c. Calculate the input impedance.
- d. Draw the admittance diagram.



Solution

a:

$$Y_1 = G = \frac{1}{R} = \frac{1}{20} = 0.05 \angle 0^\circ = 0.05 + j0$$

$$Y_2 = B_L = \frac{1}{X_L} \angle -90^\circ = \frac{1}{10} \angle -90^\circ = 0 - j0.1 = -j0.1$$

$$b: Y_T = Y_1 + Y_2 = 0.05 - j0.1 = G - jB_L$$

$$c: Z_T = \frac{1}{Y_T} = \frac{1}{0.05 - j0.1} = \frac{1}{0.112 \angle -63.43^\circ} = 8.93 \angle 63.43^\circ$$

OR


$$Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(20 \angle 0^\circ)(10 \angle 90^\circ)}{20 + j10}$$

$$= \frac{200 \angle 90^\circ}{22 \angle 26.57^\circ}$$

$$= 8.93 \angle 63.43^\circ$$

← which is the same as calculated above.

d: The admittance diagram:

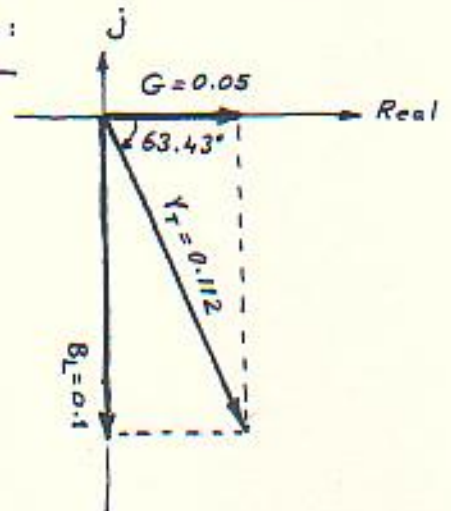


Example

EE7

_____ : For the circuit show;

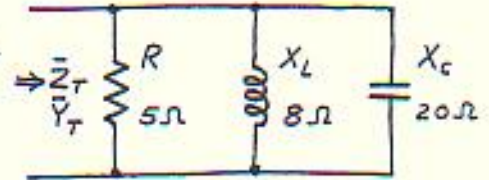- a. Determine the admittance of each branch.
- b. Find the input admittance.
- c. Calculate the input impedance.
- d. Draw the admittance diagram.



Solution

_____ : (a). $\bar{Y}_1 = \bar{G} = \frac{1}{R \angle 0^\circ} = \frac{1}{5} \angle 0^\circ = 0.2 \angle 0^\circ = 0.2 + j0 = 0.2$

$\bar{Y}_2 = \bar{B}_L = \frac{1}{X_L \angle 90^\circ} = \frac{1}{8 \angle 90^\circ} = \frac{1}{8} \angle -90^\circ = 0.125 \angle -90^\circ = -j0.125$


$\bar{Y}_3 = \bar{B}_C = \frac{1}{X_C \angle -90^\circ} = \frac{1}{20 \angle -90^\circ} = \frac{1}{20} \angle 90^\circ = 0.05 \angle 90^\circ = +j0.05$

(b). $\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3$
 $= 0.2 - j0.125 + j0.05$
 $= 0.2 - j0.075$
 $= 0.2136 \angle -20.56^\circ$

(c). $\bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.2136 \angle -20.56^\circ}$
 $= 4.68 \angle 20.56^\circ$


or $\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2 \bar{Z}_3}{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}$
 $= \frac{(5 \angle 0^\circ)(8 \angle 90^\circ)(20 \angle -90^\circ)}{(5 \angle 0^\circ)(8 \angle 90^\circ) + (8 \angle 90^\circ)(20 \angle -90^\circ) + (5 \angle 0^\circ)(20 \angle -90^\circ)}$
 $= \frac{800 \angle 0^\circ}{40 \angle 90^\circ + 160 \angle 0^\circ + 100 \angle -90^\circ}$
 $= \frac{800 \angle 0^\circ}{j40 + 160 - j100} = \frac{800 \angle 0^\circ}{160 - j60}$
 $= \frac{800 \angle 0^\circ}{170.88 \angle -20.56^\circ} = 4.68 \angle 20.56^\circ$

(d). The Admittance Diagram

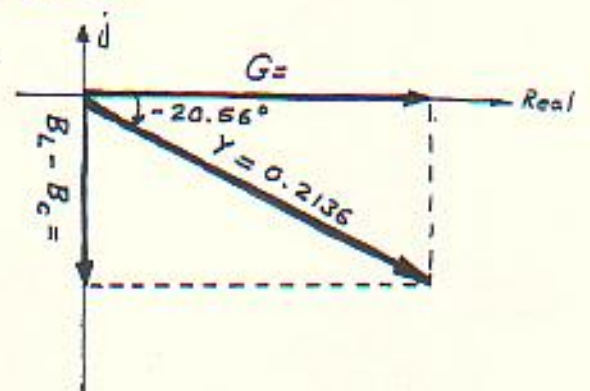

Example

Find the admittance of the circuit shown

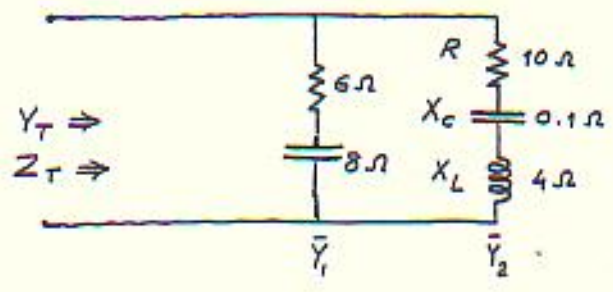

Solution

$\bar{Z}_1 = 6 - j8$

$$\Rightarrow \bar{Y}_1 = \frac{1}{\bar{Z}_1} = \frac{1}{6 - j8} = \frac{6 + j8}{6^2 + 8^2} = \frac{6}{100} + j\frac{8}{100} = 0.06 + j0.08$$

$$\bar{Z}_2 = 10 + j4 - j0.1 = 10 + j3.9$$

$$\Rightarrow \bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{10 + j3.9} = \frac{10 - j3.9}{10^2 + 3.9^2} = \frac{10}{115.21} - j\frac{3.9}{115.21} = 0.087 - j0.034$$

$$\begin{aligned} \therefore \bar{Y}_T &= \bar{Y}_1 + \bar{Y}_2 \\ &= 0.06 + j0.08 + 0.087 - j0.034 \\ &= 0.147 + j0.046 \\ &= 0.154 \angle 17.3762^\circ \end{aligned}$$

* \Rightarrow OR you can try again to get \bar{Y}_T as follows:

$$\begin{aligned} \bar{Z}_T &= \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} \\ &= \frac{(6 - j8)(10 + j3.9)}{(6 - j8) + (10 + j3.9)} \end{aligned}$$

and proceed to get $\bar{Z}_T \Rightarrow Y_T$ must be the same value

$$\bar{Y}_T = \frac{1}{\bar{Z}_T} = 0.154 \angle 17.3762^\circ$$

Illustrative Examples on R-L, R-C, and R.L.C
Parallel AC Circuits


EE7

* R-L parallel ac circuits

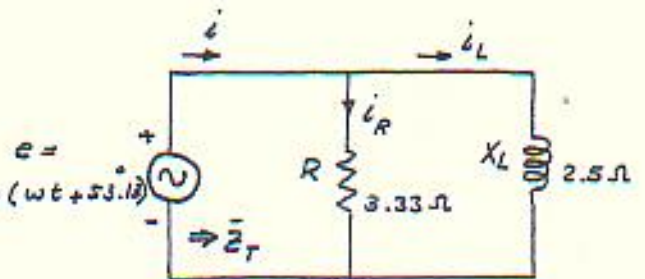Example


For the circuit shown ;

- \bar{Z}_T
- Draw the admittance diagram
- The currents \bar{I} , \bar{I}_R , and \bar{I}_L
- Draw the current phasor diagram.
- Calculate the active, reactive, and complex apparent powers.
- Determine the power factor.



Solution

Draw the circuit with phasor notation

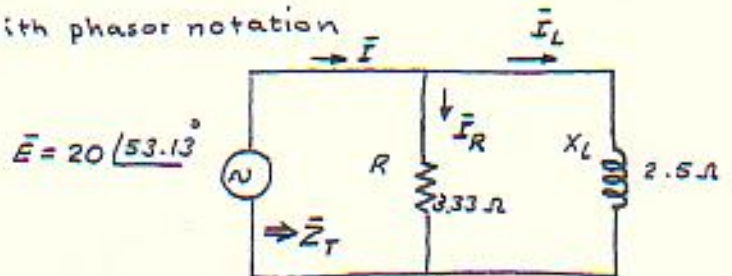


(a) \bar{Z}_T :

$$\begin{aligned} \bar{Y}_T &= \bar{Y}_1 + \bar{Y}_2 = G + B_L = \frac{1}{3.33} \angle 0^\circ + \frac{1}{2.5} \angle -90^\circ \\ &= 0.3 - j0.4 \\ &= 0.5 \angle -53.13^\circ \end{aligned}$$

$$\therefore \bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.5 \angle -53.13^\circ} = 2 \angle 53.13^\circ$$

(b) The admittance diagram

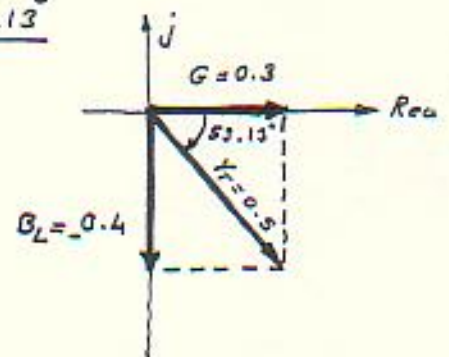

Ⓒ. $\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{20 \angle 53.13^\circ}{2 \angle 53.13^\circ} = 10 \angle 0^\circ$ EE7

$\bar{I}_R = \frac{\bar{E}}{R} = \frac{20 \angle 53.13^\circ}{3.33 \angle 0^\circ} = 6 \angle 53.13^\circ$

$\bar{I}_L = \frac{\bar{E}}{X_L} = \frac{20 \angle 53.13^\circ}{2.5 \angle 90^\circ} = 8 \angle -36.87^\circ$


* For check

using KCL $\Rightarrow \bar{I} = \bar{I}_R + \bar{I}_L$

$\Rightarrow \bar{I} = 6 \angle 53.13^\circ + 8 \angle -36.87^\circ$
 $= (3.6 + j4.8) + (6.4 - j4.8)$
 $= 10 + j0$
 $= 10 \angle 0^\circ$

which is the same as calculated above

Ⓓ. The current phasor diagram

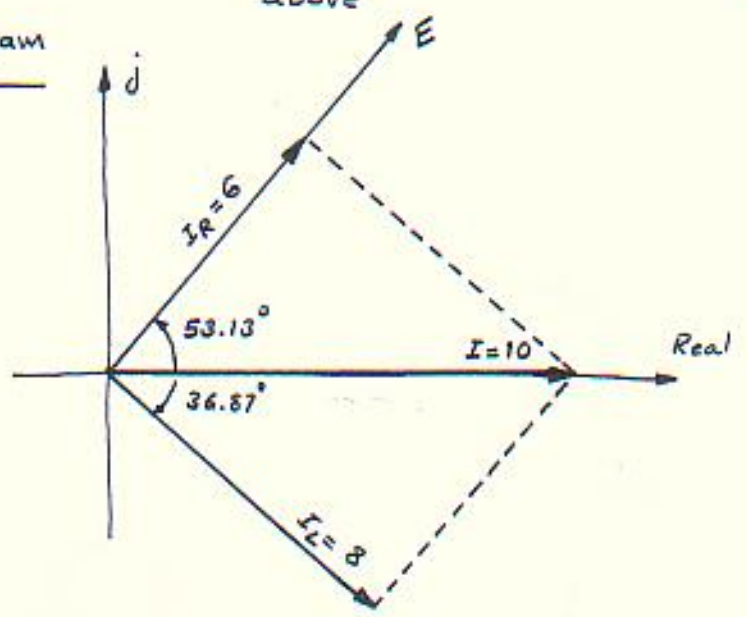

Ⓔ. Active power = $P = EI \cos \phi = (20)(10) \cos 53.13^\circ = 120 \text{ W}$

Reactive power = $Q = EI \sin \phi = (20)(10) \sin 53.13^\circ = 160 \text{ VAR}$

\therefore Complex apparent power = $\bar{S} = P + jQ = 120 + j160$

$\therefore \bar{S} = \sqrt{P^2 + Q^2} = 200 \text{ VA}$

from the phasor dig.

Ⓕ. The power factor $P.f = \cos \phi = \cos 53.13^\circ = 0.6$ lagging

or $\cos \phi = \frac{P}{EI} = \frac{E^2/R}{EI} = \frac{EG}{I} = \frac{G}{Y_T}$


ملفظة: يمكنه حساب \bar{Z}_T حسب العلاقة $\frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$ والحصول على النتيجة نفسها

* R-C parallel AC circuit

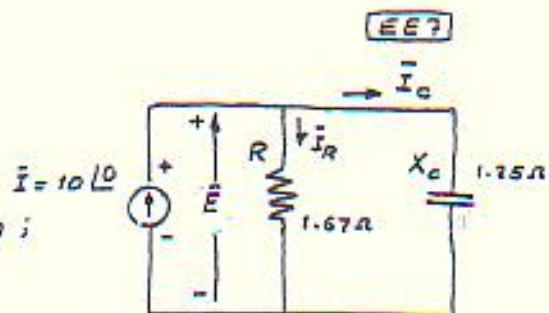Example

: For the circuit shown;

- Determine \bar{Z}_T .
- Draw the admittance diagram.
- Calculate \bar{E} , \bar{I}_R , and \bar{I}_C , and draw the current phasor diagram.
- Active, reactive, and apparent powers.
- Determine the power factor for the circuit.



Solution

(a) $\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 = \frac{1}{R \angle 0} + \frac{1}{X_c \angle -90} = \frac{1}{1.67} \angle 0 + \frac{1}{1.25} \angle 90$
 $= 0.6 + j0.8 = 1 \angle 53.13$

Also: $\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$

$\Rightarrow \bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{1 \angle 53.13} = 1 \angle -53.13$


(b) $\bar{E} = \frac{\bar{I}}{\bar{Y}_T} = \frac{10 \angle 0}{1 \angle 53.13} = 10 \angle -53.13$ or $\bar{E} = \bar{I} \bar{Z}_T$

$\bar{I}_R = \bar{E} \bar{G} = (10 \angle -53.13)(0.6) = 6 \angle -53.13$ or $\bar{I}_R = \frac{\bar{E}}{R}$

$\bar{I}_C = \bar{E} \bar{B}_C = (10 \angle -53.13)(0.8 \angle 90) = 8 \angle 36.87$ or $\bar{I}_C = \frac{\bar{E}}{X_c}$

\Rightarrow As a check?
 $\bar{I} = \bar{I}_R + \bar{I}_C = 6 \angle -53.13 + 8 \angle 36.87 = 10 \angle 0$

(c) The phasor diagram:

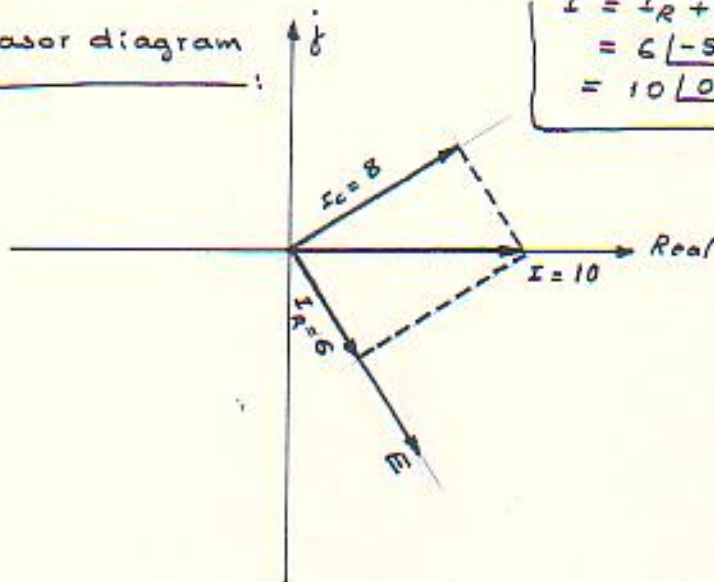

(d). Active power = $P = EI \cos \phi$
 $= (10)(10) \cos 53.13^\circ$
 $= 60 \text{ W}$

EE7

* or $P = E^2 G$
 $= (10)^2 (0.6)$
 $= 60 \text{ W}$

Reactive power = $Q = EI \sin \phi$
 $= (10)(10) \sin 53.13^\circ$
 $= 80 \text{ VAR}$

\therefore Apparent power $S = \sqrt{P^2 + Q^2} = \sqrt{(60)^2 + (80)^2}$
 $= 100 \text{ VA}$

(e). The power factor

p.f = $\cos 53.13$
 $= 0.6 \text{ leading}$


← from the phasor diagram
 \bar{I} leads \bar{E}

* R-L-C parallel AC circuit:

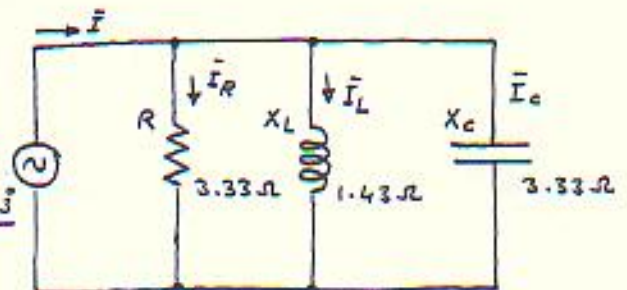Example

For the circuit shown;

- Determine \bar{Z}_T .
- Calculate \bar{I} , \bar{I}_R , \bar{I}_L & \bar{I}_C .
- Draw the phasor diag. $\bar{E} = 100 \angle 53.13^\circ$
- Calculate the active (real) power
- Determine the power factor



Solution

(a). $\bar{Z}_T = ?$

$$\begin{aligned} \bar{Y}_T &= \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 \\ &= \frac{1}{R} \angle 0^\circ + \frac{1}{X_L} \angle -90^\circ + \frac{1}{X_C} \angle 90^\circ \\ &= \frac{1}{3.33} \angle 0^\circ + \frac{1}{1.43} \angle -90^\circ + \frac{1}{3.33} \angle 90^\circ \\ &= 0.3 - j0.7 + j0.3 \\ &= 0.3 - j0.4 \\ &= 0.5 \angle -53.13^\circ \end{aligned}$$

$$\therefore \bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.5 \angle -53.13^\circ} = 2 \angle 53.13^\circ$$

(b). $\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{100 \angle 53.13^\circ}{2 \angle 53.13^\circ} = 50 \angle 0^\circ$

$\bar{I}_R = \frac{\bar{E}}{R} = \sqrt{\dots}$ ←

$I_R = \bar{E} \bar{G} = (100 \angle 53.13^\circ)(0.3 \angle 0^\circ)$
 $= 30 \angle 53.13^\circ$


$$\Rightarrow \bar{I}_L = \frac{\bar{E}}{X_L} \quad \boxed{EE7}$$

$$\bar{I}_L = \bar{E} \bar{B}_L = (100 \angle 53.13^\circ)(0.7 \angle -90^\circ) = 70 \angle -36.87^\circ$$

$$\bar{I}_C = \bar{E} \bar{B}_C = (100 \angle 53.13^\circ)(0.3 \angle 90^\circ) = 30 \angle 143.13^\circ$$

Prove that : $\bar{I} = \bar{I}_R + \bar{I}_L + \bar{I}_C$

Ⓒ. The current phasor diagram :

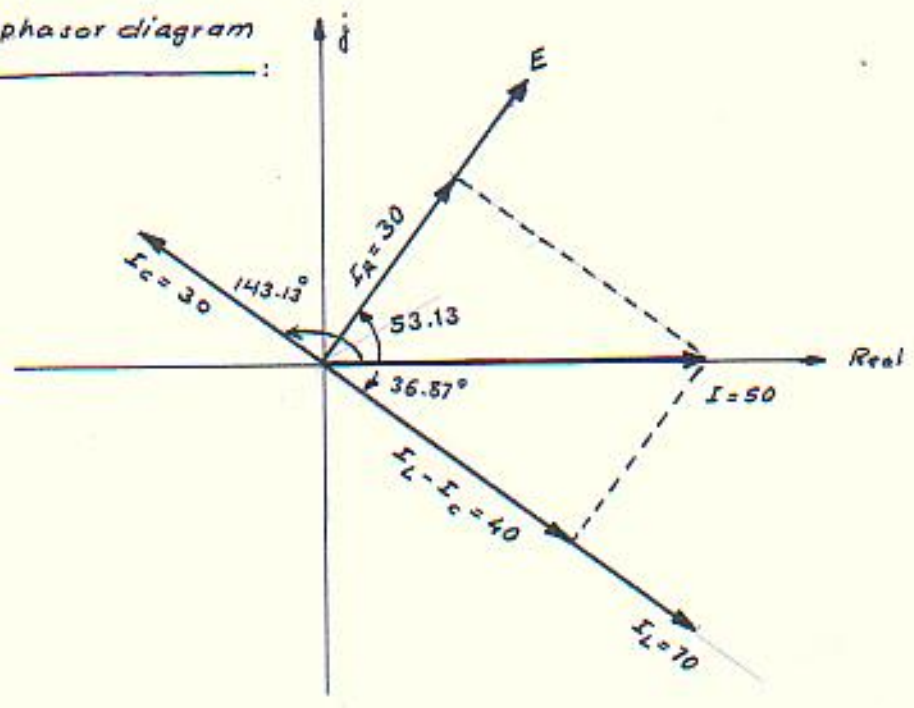

Ⓓ. Active power = P = EI cos φ
 (Real power) = (100)(50) cos 53.13°
 = 3000 W
 = 3.0 kW

⇒ or P = E²G
 = (100²)(0.3)
 = 3.0 kW


Ⓔ. The power factor ⇒ p.f = cos φ
 = cos 53.13
 = 0.6 lagging ← from the phasor diagram.

$$\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2 \bar{Z}_3}{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}$$

← ملاحظة : من الممكن كذلك حساب \bar{Z}_T والمحصول على النتيجة نفسه.

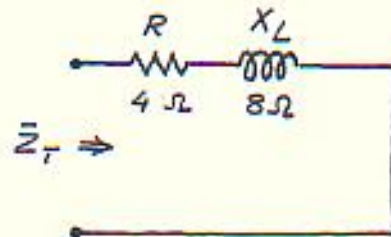Example

_____ : Draw the impedance diagram for the circuit shown and find the total impedance.




Solution

_____ : $\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2$

$$= R \angle 0^\circ + X_L \angle 90^\circ = R + jX_L = 4 + j8$$
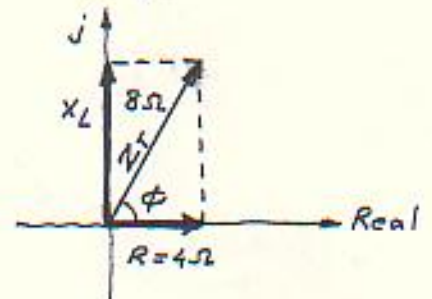
$$\therefore \bar{Z}_T = 8.944 \angle 63.43^\circ \Omega$$



Example

_____ : Determine the input impedance to the series network shown

Solution

_____ :

$$\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3$$

$$= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ$$


$$= R + jX_L - jX_C$$

$$= R + j(X_L - X_C)$$

$$= 6 + j(10 - 12)$$

$$= 6 - j2$$
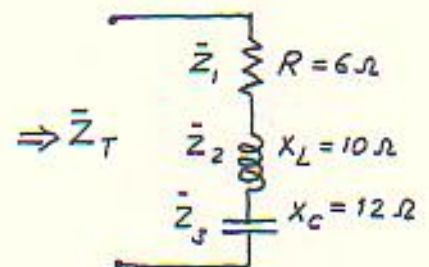
$$\Rightarrow \bar{Z}_T = 6.325 \angle -18.43^\circ \Omega$$




Example

- _____ : A 60 Hz sinusoidal voltage ($v = 141 \sin \omega t$) is applied to a series R-L circuit. The values of the resistance and the inductance are 3Ω and 0.0106 H respectively.
- Compute the rms value of the current in the circuit and its phase angle with respect to the voltage.
 - Write the expression for the instantaneous current in the circuit.
 - Find the average power dissipated by the circuit.
 - Calculate the p.f of the circuit.

Solution

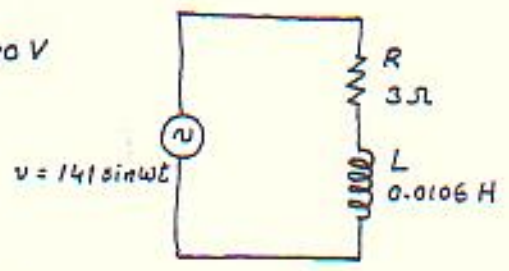_____ : We have ; $v = V_m \sin \omega t$
 $\Rightarrow V = \frac{V_m}{\sqrt{2}} = \frac{141}{\sqrt{2}} = 100 \text{ V}$
 $\therefore \bar{V} = 100 \angle 0$



(a). $\bar{I} = \frac{\bar{V}}{\bar{Z}}$

$\bar{Z} = R + jX_L$
 $= R + j(2\pi fL)$
 $= 3 + j(2\pi \times 60 \times 0.0106)$
 $= 3 + j4$
 $\therefore \bar{Z} = 5 \angle 53.1^\circ$

$\Rightarrow \bar{I} = \frac{100 \angle 0}{20 \angle 53.1^\circ}$

$\therefore \bar{I} = 20 \angle 53.1^\circ \Rightarrow$ the current lags the voltage by 53.1°

(b). $i = I_m \sin(\omega t - 53.1^\circ)$
 $= \sqrt{2}(20) \sin(\omega t - 53.1^\circ) = \underline{28.28 \sin(\omega t - 53.1^\circ)}$

(c). $P = VI \cos \phi$
 $= (100)(20) \cos 53.1^\circ = 1200 \text{ W}$

or $P = I^2 R = (20)^2(3) = 1200 \text{ W}$

(d). p.f = $\cos \phi$
 $= \cos 53.1^\circ$
 $= 0.6$ lagging

Example

_____ : A two elements series circuit is connected across an ac circuit having a source ($e = \sqrt{2}(200) \sin(\omega t + 20^\circ) \text{ V}$). The current in the circuit is then found to be $i = \sqrt{2}(10) \cos(341t - 25^\circ)$. Determine the parameters of the circuit.

Solution

The applied voltage is :

$$v = \sqrt{2}(200)\sin(\omega t + 20^\circ)$$

$$\Rightarrow \bar{V} = 200 \angle 20^\circ$$

The current is :

$$i = \sqrt{2}(10)\cos(\omega t - 25^\circ)$$

$$= \sqrt{2}(10)\sin(\omega t - 25^\circ - 90^\circ)$$

$$\therefore i = \sqrt{2}(10)\sin(\omega t + 65^\circ)$$

$$\Rightarrow \bar{I} = 10 \angle 65^\circ$$

$$\Rightarrow \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{200 \angle 20^\circ}{10 \angle 65^\circ} = 20 \angle -65^\circ$$

Note $\phi = -45^\circ$
(leading)

$$= 14.14 - j 14.14$$

This impedance represents a series circuit with $R = 14.14 \Omega$ and a capacitive reactance (because of the $-j$) of $X_c = 14.14 \Omega$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

سرعة التيار $\omega = 314$ rad/sec.

$$\therefore 14.14 = \frac{1}{314 C} \Rightarrow C = \frac{1}{(14.14)(314)} = 2.25 \times 10^{-4} \text{ F}$$


\therefore The circuit has $R = 14.14 \Omega$
and $C = 225 \mu\text{F}$

Example

Two coils A and B are connected in series across 240 V, 50 Hz supply. The resistance of A is 5Ω and the inductance of B is 0.015 H . If the input supply is 3 kW and 2 kVAR, find the resistance of B and the inductance of A. Calculate the voltage across each coil.

Solution

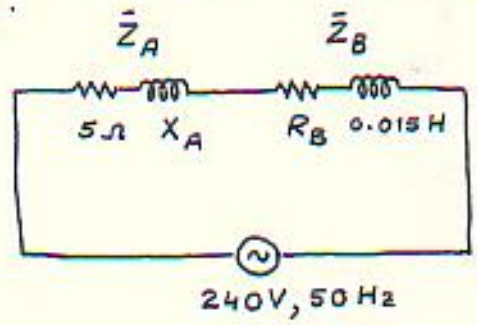* From the power triangle, and the circuit shown,



$$S = \sqrt{P^2 + Q^2} = \sqrt{3^2 + 2^2} = 3.606 \text{ KVA}$$

$$S = VI \Rightarrow I = \frac{S}{V} = \frac{3606}{240} = 15.025 \text{ A}$$

$$\text{But, } P = 3 \text{ kW} = 3000 \text{ W} \\ = I^2 R_T = I^2 (R_A + R_B)$$

$$\therefore 3000 = (15.025)^2 (R_A + R_B)$$

$$\Rightarrow R_A + R_B = 13.3 \Omega$$

$$\therefore \text{Since } R_A = 5 \Omega \Rightarrow R_B = 13.3 - 5 = \underline{8.3 \Omega}$$

T57

Similarly, we have:

ملحوظة: من الممكن ان هذا السؤال
بالكثير من طريقتين والوصول اليه
النتيجة نفسها.

$$Q = 2 \text{ kVAR} = 2000 \text{ VAR} \\ = I^2 X_{LT} = (15.03)^2 X_{LT}$$

$$\therefore X_{LT} = \frac{2000}{(15.03)^2} = 8.85 \Omega$$

$$X_{LT} = X_A + X_B \Rightarrow X_A = 8.85 - X_B \\ = 8.85 - (2\pi f L_B) \\ = 8.85 - (2\pi \times 50 \times 0.015) \\ = 8.85 - 4.713 = 4.13 \Omega$$

$$\therefore \bar{Z}_A = R_A + jX_A = 5 + j4.13 = 6.48 \angle 39.57^\circ$$

$$\text{and } \bar{Z}_B = R_B + jX_B = 8.3 + j4.713 = 9.54 \angle 29.59^\circ \quad X_B = 2\pi f L_B \\ = 2\pi \times 50 \times 0.015$$

$$\therefore \bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 = 5 + j4.13 + 8.3 + j4.713 \\ =$$

$$\therefore \bar{V}_A = \bar{I} \bar{Z}_A = \checkmark$$

$$\bar{V}_B = \bar{I} \bar{Z}_B = \checkmark$$

$$\text{or } \bar{V}_A = \frac{\bar{V} \bar{Z}_A}{\bar{Z}_A + \bar{Z}_B} = \checkmark$$

The results must be the same.

and

$$\bar{V}_B = \frac{\bar{V} \bar{Z}_B}{\bar{Z}_A + \bar{Z}_B} = \checkmark$$

Example

A 240 V, 50 Hz series R-C circuit takes an rms current of 20 A. The maximum value for the current occurs 1/900 seconds before the maximum value of the voltage. Calculate:
(a). The power factor.
(b). Average power.
(c). The parameters of the circuit.

Solution

The time duration of the voltage (T) = 0.02 = 0.02 sec.

$$\therefore 0.05 \text{ sec.} \Rightarrow 360^\circ, \text{ then}$$

$$(1/900) \text{ sec} \Rightarrow \left[\frac{360^\circ (1/900)}{0.02} \right]^\circ = \text{The phase shift angle } (\phi)$$


$$\therefore \phi = 20^\circ$$

$$(a). \therefore p.f = \cos \phi = \cos 20^\circ \\ = 0.9397 \quad (\text{leading})$$

$$(b). \text{Average power} = P = VI \cos \phi \\ = 240(20) \cos 20^\circ \\ = 4510 \text{ W} \\ = 4.510 \text{ kW}$$

$$(c). \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{240 \angle 0^\circ}{20 \angle 20^\circ} = 12 \angle -20^\circ \\ = 20 \cos(-20) + j 12 \sin(-20) \\ = 11.28 - j 4.1$$

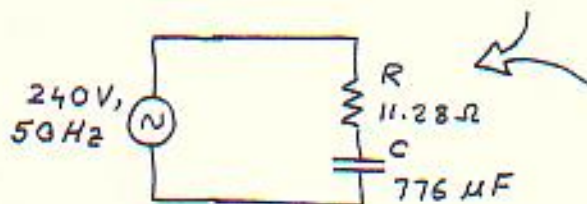$\therefore \bar{Z}$ is composed of $R = 11.28 \Omega$, and $X_c = 4.1 \Omega$




$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} \\ \therefore C = \frac{1}{2\pi f X_c} = 7.76 \times 10^{-4} \text{ F} \\ = 776 \mu\text{F}$$

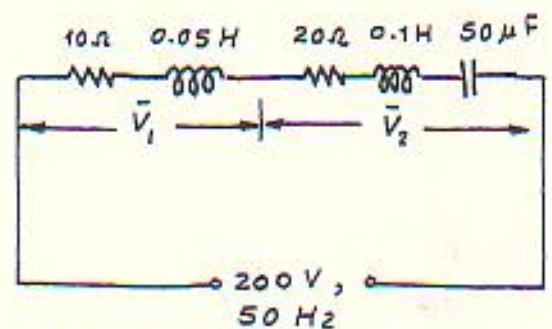Example

Draw the phasor diagram for the circuit shown, indicating the resistance and the reactance drop, the terminal voltages \bar{V}_1 and \bar{V}_2 and the current. Find the values of:

- The current \bar{I} .
- \bar{V}_1
- \bar{V}_2
- The power factor



Solution

$$R_T = 10 + 20 = 30 \Omega \\ L_T = 0.05 + 0.1 = 0.15 \text{ H} \\ \Rightarrow X_L = \omega L = 2\pi f L_T = 2\pi(50)(0.15) \\ = 47.1 \Omega$$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi(50)(50 \times 10^{-6})} = 63.7 \Omega$$

$$\therefore \bar{Z}_T = \sqrt{R^2 + (X_L - X_c)^2} = \sqrt{(30)^2 + (47.1 - 63.7)^2} \\ = 34.3 \angle -28.96^\circ$$

$$(a). \therefore \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{200 \angle 0^\circ}{34.3 \angle -28.96^\circ} = 5.83 \angle 28.96^\circ \quad \text{leading}$$

(b). $\bar{V}_1 = ?$

T57

$$\bar{V}_1 = \bar{I} \bar{Z}_1$$

$$\Rightarrow \bar{Z}_1 = 10 + jX_{L1}$$

$$= 10 + j(2\pi fL_1)$$

$$= 10 + j(2\pi(50)0.05)$$

$$= 10 + j15.7$$

$$\therefore \bar{V}_1 = (5.83 \angle 28.96^\circ)(18.6 \angle 57.5^\circ)$$

$$= 108.4 \angle 86.46^\circ$$

$$\therefore \bar{Z}_1 = 18.6 \angle 57.5^\circ$$

(c). $\bar{V}_2 = ?$

$$\bar{V}_2 = \bar{I} \bar{Z}_2$$

$$\Rightarrow \bar{Z}_2 = 20 + jX_{L2} - jX_{C2}$$

$$= 20 + j(2\pi fL_2) - \frac{1}{2\pi fC_2}$$

$$= 20 + j31.4 - j63.7$$

$$= 20 - j32.3$$

$$\therefore \bar{V}_2 = \bar{I} \bar{Z}_2 = (5.83 \angle 28.96^\circ)(37.74 \angle -58.2^\circ)$$


$$= 220.1 \angle -52.37^\circ$$

(d). The combined (overall) power factor of the circuit :

- from part (a) \Rightarrow p.f = $\cos \phi = \cos 28.96^\circ$
 $= 0.87$ leading

- or p.f = $\frac{R}{Z_T} = \frac{30}{34.3} = 0.87$ (leading)

The phasor diagram

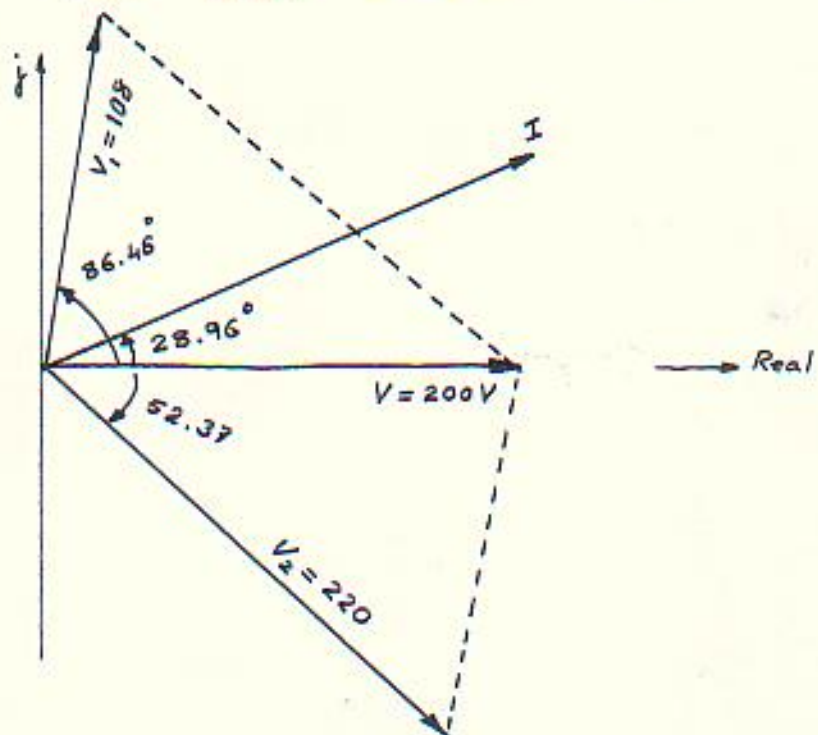

T57

Example

_____ : In a circuit it is found that the applied voltage is to lag the current by 30° .


- (a). Is the power factor lagging or leading?
- (b). What is the value of the power factor?
- (c). Is the circuit inductive or capacitive?

Solution

- (a). The power factor is leading, since the current leads the voltage.
- (b). The power factor is $p.f = \cos \phi$
 $= \cos 30$
 $= 0.866$ (lead)
- (c) The circuit is capacitive.

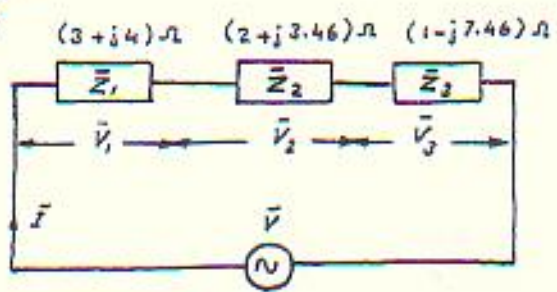Example

_____ : In the circuit diagram of the Fig. shown, the voltage drop across \bar{Z}_1 is $(10 + j0)$ volts. Find out:



- (a). The current in the circuit.
- (b). The voltage drop across \bar{Z}_2 and \bar{Z}_3
- (c). The voltage of the source.

Solution

_____ : (a). $\bar{I} = \frac{\bar{V}}{\bar{Z}_T} \Rightarrow \bar{Z}_T = \frac{\bar{V}}{\bar{I}}$

or $I = \frac{\bar{V}_1}{\bar{Z}_1} = \frac{10 + j0}{3 + j4} = \frac{10 \angle 0^\circ}{5 \angle 53.1^\circ} = 2 \angle -53.1^\circ$
 $= 2(\cos 53.1^\circ - j \sin 53.1^\circ) = 1.2 - j1.6$

(b). $\bar{V}_2 = \bar{I} \bar{Z}_2 = (1.2 - j1.6)(2 + j3.46) = 7.936 + j0.952$ volts


$\bar{V}_3 = \bar{I} \bar{Z}_3 = (1.2 - j1.6)(1 - j7.46) = -10.74 - j10.55$ volts

(c). $\bar{V} = \bar{V}_1 + \bar{V}_2 + \bar{V}_3$
 $= (10 + j0) + (7.936 + j0.952) + (-10.74 - j10.55)$
 $= 7.2 - j9.6 = 12 \angle -53.1^\circ$ volts

لذلك ان العولنية الكلية والتيار المار في الدارة كلاهما بنفس الطور والسبب في ذلك ان \bar{Z}_T في هذه الدارة لا تمثل عددا مركبا بل قيمة حقيقية فقط (real part) اي انها تمثل مقاومة فقط والتي بدورها لا تؤثر في الطور بين العولنية والتيار.

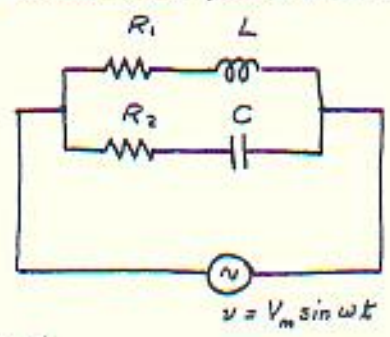Example

Derive an expression for the equivalent impedance for the circuit in the Fig. shown, in terms of the circuit parameters



Solution

Let $\bar{Z}_1 = R_1 + jX_L = R_1 + j\omega L$
 $\bar{Z}_2 = R_2 - jX_C = R_2 - j\frac{1}{\omega C}$

$$\therefore \bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$$

$$= \frac{(R_1 + j\omega L)(R_2 - j\frac{1}{\omega C})}{(R_1 + j\omega L) + (R_2 - j\frac{1}{\omega C})}$$

$$= \frac{R_1 R_2 + j\omega L R_2 - j\frac{R_1}{\omega C} + \frac{L}{C}}{(R_1 + R_2) + j(\omega L - \frac{1}{\omega C})}$$

$$\Rightarrow \frac{(R_1 R_2 + j\omega L R_2 - j\frac{R_1}{\omega C} + \frac{L}{C})(R_1 + R_2)}{(R_1 + R_2)^2 + (\omega L - \frac{1}{\omega C})^2} - j \frac{(R_1 R_2 + j\omega L R_2 - j\frac{R_1}{\omega C} + \frac{L}{C})(\omega L - \frac{1}{\omega C})}{(R_1 + R_2)^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \frac{(R_1 R_2 + \frac{L}{C})(R_1 + R_2) + (\omega L R_2 - \frac{R_1}{\omega C})(\omega L - \frac{1}{\omega C})}{(R_1 + R_2)^2 + (\omega L - \frac{1}{\omega C})^2} - j \frac{(R_1 + R_2)(\frac{R_1}{\omega C} - \omega L R_2) + (R_1 R_2 - \frac{L}{C})(\omega L - \frac{1}{\omega C})}{(R_1 + R_2)^2 + (\omega L - \frac{1}{\omega C})^2}$$

Simplifying further, then:

$$\bar{Z}_T = \frac{R_1 R_2 (R_1 + R_2) + \omega^2 L^2 R_2 + \frac{R_1}{\omega^2 C^2}}{(R_1 + R_2)^2 + (\omega L - \frac{1}{\omega C})^2} + j \frac{\omega L R_2^2 - \frac{R_1^2}{\omega C} - \frac{L}{C}(\omega - \frac{1}{\omega C})}{(R_1 + R_2)^2 + (\omega L - \frac{1}{\omega C})^2}$$

You can also derive an expression for the admittance of the circuit Y_T , and the result will be as:


$$\bar{Y}_T = \frac{R_1 + \omega^2 C^2 R_1 R_2 (R_1 + R_2) + \omega^4 L^2 C^2 R_2^2}{(R_1 + \omega^2 L^2) + (1 + \omega^2 C^2 R_2^2)} + j\omega \left[\frac{C R_1^2 - L + \omega^2 L C (L - C R_2^2)}{(R_1 + \omega^2 L^2) + (1 + \omega^2 C^2 R_2^2)} \right]$$

ملاحظة : ربما يعتقد الطالب انه قد افكرة خاصة في هذا المثال عما اجره الذي يتطلبه الحل وهو ليس بالتفصيل . ان الفكرة من هذا المثال سوف توضح خلال دراسته موضوع الرنين (Resonance) الذي يتطلب منهم مسأله استغناء تردد الرنين ومعالجه اخرى منه خلال استنتاجه \bar{Z}_T او Y_T

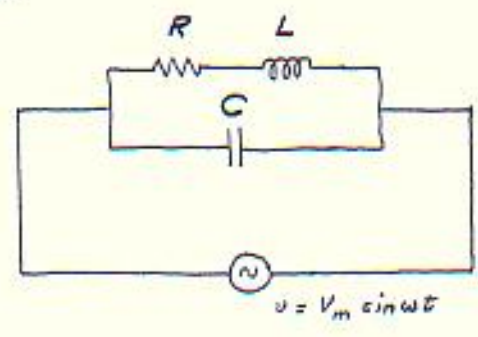Example (HW)

TST

Derive expressions for the equivalent impedance and (or) the admittance for the circuit shown.



Answer:

$$\bar{Z}_T = \frac{R + j\omega [L(1 - \omega^2 LC^2) - CR^2]}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2}$$

and


$$\bar{Y}_T = \frac{R - j\omega [L(1 - \omega^2 LC) - CR^2]}{R^2 + \omega^2 L^2}$$

* Please check the answers.

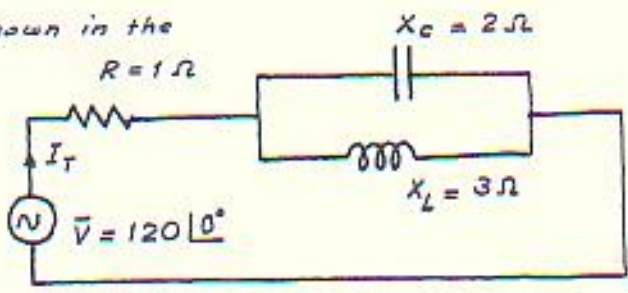Example

For the circuit shown in the Fig., determine:

- (a). \bar{Z}_T
- (b). \bar{I}_T
- (c). I_C
- (d). \bar{V}_R
- (e). \bar{V}_C
- (f). Average power
- (g). The power factor of the circuit.




Solution

Redraw the circuit (option):

Let $\bar{Z}_1 = R = 1 \angle 0^\circ \Omega$
 & $Z_2 = X_C \parallel X_L$
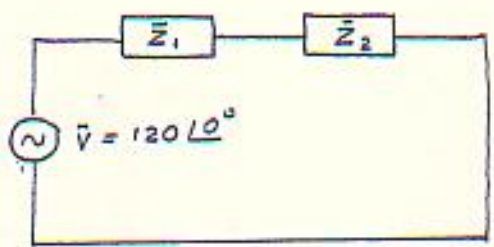
$$\begin{aligned} &= \frac{X_C X_L}{X_C + X_L} = \frac{(-j2)(j3)}{-j2 + j3} \\ &= \frac{6 \angle 0^\circ}{j1} = \frac{6 \angle 0^\circ}{1 \angle 90^\circ} \\ &= 6 \angle -90^\circ = -j6 \Omega \end{aligned}$$



(a). $\therefore \bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 = 1 - j6 = 6.08 \angle -80.54^\circ \ \Omega$ T57

(b). $\bar{I}_T = \frac{\bar{V}}{\bar{Z}} = \frac{120 \angle 0^\circ}{6.08 \angle -80.54^\circ} = 19.74 \angle 80.54^\circ \ \text{A}$

(c). $I_c = ?$
Using the current divider rule, I_c can be calculated as:

$$\bar{I}_c = I_T \frac{X_L}{X_L + X_C} = 19.74 \angle 80.54^\circ \cdot \frac{3 \angle 90^\circ}{1 \angle 90^\circ}$$

$$= 59.22 \angle 80.54^\circ \ \text{A}$$

(d). $\bar{V}_R = ?$

$$\bar{V}_R = \bar{I}_T \bar{Z}_1 = (19.74 \angle 80.54^\circ)(1 \angle 0^\circ)$$

$$= 19.74 \angle 80.54^\circ \ \text{V}$$

(e) $\bar{V}_C = ?$

$$\bar{V}_C = \bar{I}_T \bar{Z}_2 = (19.74 \angle 80.54^\circ)(6 \angle -90^\circ)$$

$$= 118.44 \angle -9.46^\circ \ \text{V}$$

OR $\bar{V}_C = \bar{I}_c \bar{X}_C = (59.22 \angle 80.54^\circ)(2 \angle -90^\circ)$

$$= 118.44 \angle -9.46^\circ$$

(f). Average power = Active power

$$P = I_T^2 R = (19.74)^2 \times 1 = 389.67 \ \text{W}$$

or $P = VI \cos \phi = 389.67 \ \text{W}$


(g). Power factor = $\cos \phi$ $\phi = 80.54^\circ$

$$\therefore \text{p.f} = \cos 80.54^\circ$$

$$= 0.164 \ \text{leading}$$

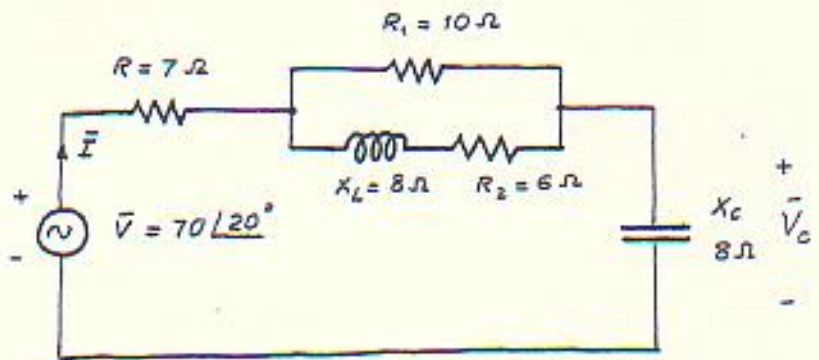Example (HW)

- (a). Calculate the voltage V_c using the voltage divider rule.
- (b). Calculate the current I




Answer

(a). $\bar{V}_c = 42.42 \angle -45.38^\circ \ \text{volts}$

(b). $\bar{I} = 5.3 \angle 44.62^\circ \ \text{A}$

Example

Find the current I in the circuit shown.

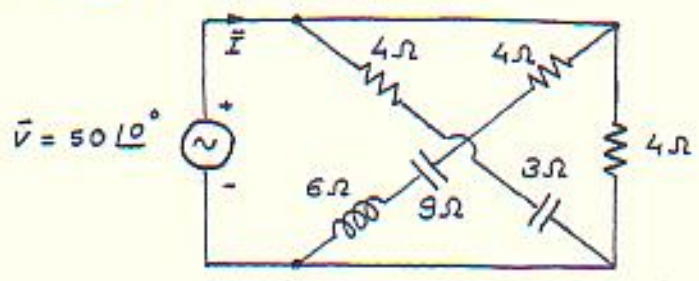

Solution

Let $\bar{Z}_1 = 4 - j3$

$$\bar{Z}_2 = 4 + j6 - j9 = 4 - j3$$

and

$$\bar{Z}_3 = 4 + j0 = 4 \Omega$$

دفعان $\bar{Z}_1, \bar{Z}_2, \bar{Z}_3$ مربوطة على التوازي

$\bar{Z}_1 = \bar{Z}_2$ دفعان

$$\bar{Z}_T = \bar{Z}_1 // \bar{Z}_2 // \bar{Z}_3$$

since $\bar{Z}_1 = \bar{Z}_2 \Rightarrow \bar{Z}_{12} = \frac{\bar{Z}_1}{2} = \frac{4-j3}{2}$

$$\therefore \bar{Z}_T = \frac{\bar{Z}_{12} // \bar{Z}_3}{\bar{Z}_{12} + \bar{Z}_3} = \frac{\bar{Z}_{12} \bar{Z}_3}{\bar{Z}_{12} + \bar{Z}_3} = \frac{4(2-j1.5)}{4+2-j1.5}$$

$$\therefore \bar{Z}_T = \frac{8-j6}{6-j1.5} = \frac{10 \angle -36.87^\circ}{6.18 \angle -14.04^\circ} = 1.62 \angle -22.83^\circ$$

$$\therefore \bar{I}_T = \frac{\bar{V}}{\bar{Z}_T} = \frac{50 \angle 0^\circ}{1.62 \angle -22.83^\circ} = 30.86 \angle 22.83^\circ$$

Note

Z_T can be calculated from:

$$\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2 \bar{Z}_3}{\bar{Z}_1 \bar{Z}_2 + \bar{Z}_2 \bar{Z}_3 + \bar{Z}_1 \bar{Z}_3}$$

or $\bar{Z}_T = \frac{1}{\bar{Y}_T}$

where $\bar{Y}_T = Y_1 + Y_2 + Y_3$

$$\bar{Y}_1 = \frac{1}{\bar{Z}_1}, \bar{Y}_2 = \frac{1}{\bar{Z}_2}, \bar{Y}_3 = \frac{1}{\bar{Z}_3}$$

بالصك على النتيجة نفسها


T57

Example

For the circuit shown,

- Compute \bar{I} .
- Find \bar{I}_1 , \bar{I}_2 and \bar{I}_3 .
- Verify Kirchhoff's Current law by showing that:

$$\bar{I} = \bar{I}_1 + \bar{I}_2 + \bar{I}_3$$
- Find the total impedance of the circuit.

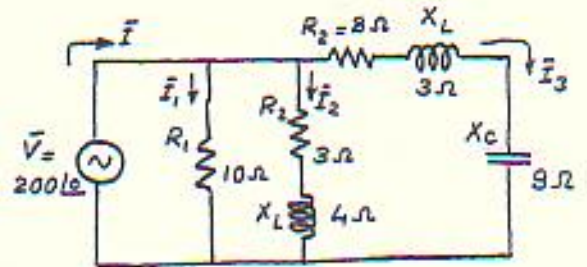**Solution**


Redraw the circuit as shown in the Fig. below;

where;

$$\bar{Z}_1 = 10 \angle 0^\circ = 10 \Omega$$

$$\bar{Z}_2 = 3 + j4$$
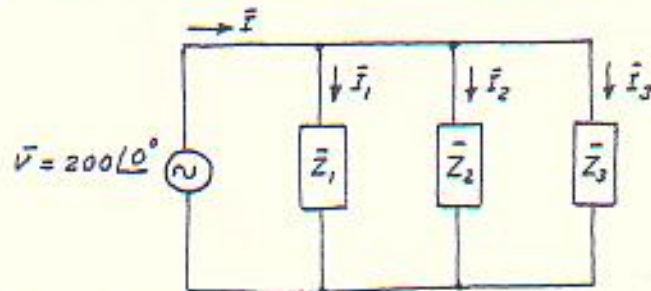
$$\begin{aligned} \bar{Z}_3 &= 8 + j3 - j9 \\ &= 8 - j6 \end{aligned}$$



$$\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3}$$

$$= \frac{1}{10} + \frac{1}{3+j4} + \frac{1}{8-j6}$$

$$= \left(\frac{1}{10}\right) + \frac{3}{9+16} - j \frac{4}{9+16} + \frac{8}{64+36} + j \frac{6}{64+36}$$

$$= \frac{1}{10} + \frac{3}{25} + \frac{8}{100} - j \frac{4}{25} + j \frac{6}{100}$$

$$\therefore \bar{Y}_T = 0.3 - j0.1 \quad (\text{S})$$

(a). $\bar{I} = ?$

$$\begin{aligned} \bar{I} &= \bar{V} \cdot \bar{Y}_T = 200 \angle 0^\circ (0.3 - j0.1) \\ &= \underline{60 - j20} \end{aligned}$$

(b).

$$\bar{I}_1 = \frac{\bar{V}}{\bar{Z}_1} = \frac{200 \angle 0^\circ}{10 \angle 0^\circ} = 20 \angle 0^\circ \quad \text{A}$$

$$\bar{I}_2 = \frac{\bar{V}}{\bar{Z}_2} = \frac{200 \angle 0^\circ}{5 \angle 53.13^\circ} = 40 \angle -53.13^\circ \quad \text{A}$$

and

$$\bar{I}_3 = \frac{\bar{V}}{\bar{Z}_3} = \frac{200 \angle 0^\circ}{10 \angle -36.87^\circ} = 20 \angle 36.87^\circ$$

(c)

$$\begin{aligned} \bar{I} &= \bar{I}_1 + \bar{I}_2 + \bar{I}_3 \\ 60 - j20 &= 20 \angle 0^\circ + 40 \angle -53.13^\circ + 20 \angle 36.87^\circ \\ &= (20 + j0) + (24 - j32) + (16 + j12) \end{aligned}$$

$$\therefore \underline{60 - j20} = \underline{60 - j20}$$

(d). $\bar{Z}_T = ?$

TS7

$$\bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.3 - j0.1} = \frac{0.3}{(0.3)^2 + (0.1)^2} + j \frac{0.1}{(0.3)^2 + (0.1)^2}$$

$$\therefore \bar{Z}_T = 3 + j1$$

For check

$$\bar{V} = \bar{I} \bar{Z}_T$$


$$= (60 - j20)(3 + j1)$$

$$= 180 - j60 + j60 + 20$$

$$= 200 + j0 = 200 \angle 0^\circ$$

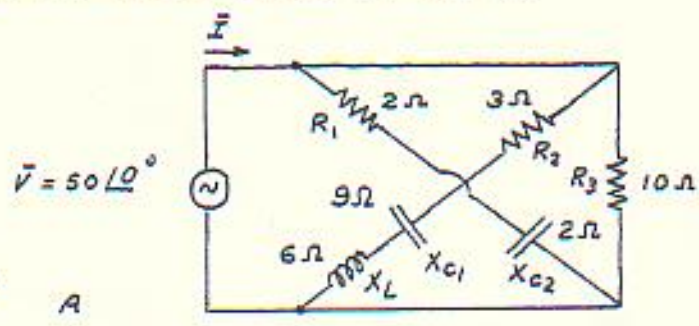Example (HW)

: Find the current I in the circuit shown in the Fig.



Answer

$$\bar{I} = 33.201 \angle 38.89^\circ \text{ A}$$

Example

: The load taken from a supply consists of: (a). lamp load of 10 kW at unity power factor, (b). motor load of 80 kVA at 0.8 power factor (lag), and (c). motor load of 40 kVA at 0.7 power factor leading.

Calculate the total load taken from the supply in kW and in kVA and the power factor of the combined load.

Solution

ملاحظة: عند حسابها لمن هذا المثال اذا يكون بشكل جدول يضم انواع القدرة المختلفة بدهمات التوتية ركما يأتي:

Load	kVA	cos φ	sin φ	kW	kVAR
(a)	10	1	0	10	0 (p.f = 1)
(b)	80	0.8	0.6	64	- 48 (p.f lag)
(c)	40	0.7	0.714	28	+ 28.6 (p.f lead)
TOTAL →				102	- 19.4



∴ Total kW = 102 ⇒ P_T
 Total kVAR = -19.4 (lagging) ⇒ Q_T

∴ Total kVA taken from the supply S_T

$$S_T = \sqrt{P_T^2 + Q_T^2}$$

$$= \sqrt{(102)^2 + (-19.4)^2} = 103.9 \text{ kVA}$$



and the power factor = $\cos \phi = \frac{P_T}{S_T} = \frac{102}{103.9} = 0.982$

وبما أن القدرة على الجهد أكبر، فمضاراً كما يأتي

$$S_T = S_1 + S_2 + S_3$$

$$= P_1 + jQ_1 + P_2 + jQ_2 + P_3 + jQ_3$$

$$= [10 \cos 0 + j0 + 80 \cos \phi_2 + j80 \sin \phi_2 + 40 \cos \phi_3 + j40 \sin \phi_3] \times 10^3$$

$$= [(10 + 64 + 28) + j(0 - 48 + 28.6)] \times 10^3$$


∴ $\vec{S}_T = 102 - j19.4 \text{ kVA}$

$$= 103.9 \angle -10.77 \text{ kVA}$$

∴ S = 103.9 kVA
 p.f = $\cos(-10.77)$
 = 0.982 (lagging)

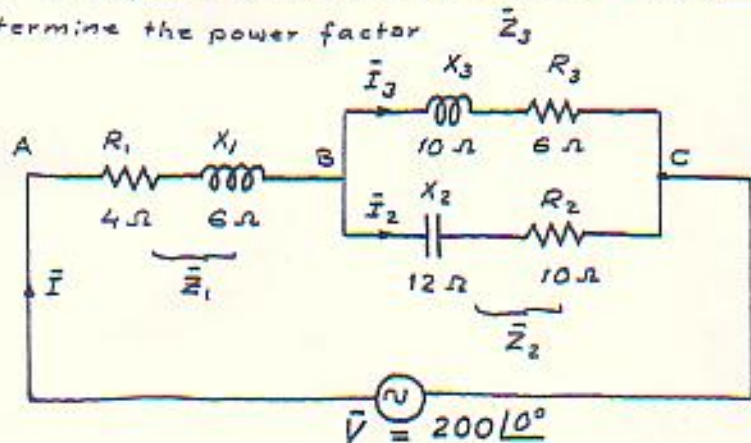Example

—: Determine the current drawn by the following circuit, where a voltage of 200 V is applied across its terminals. Draw the phasor diagram, and determine the power factor of the circuit.



Solution

—: $\vec{Z}_1 = 4 + j6 = 7.2 \angle 56.3^\circ \Omega$

$\vec{Z}_2 = 10 - j12 = 15.6 \angle -50.2^\circ \Omega$

$\vec{Z}_3 = 6 + j10 = 11.7 \angle 58^\circ \Omega$

$\therefore \bar{Z}_T = \bar{Z}_1 + \bar{Z}_{23}$

$\bar{Z}_{23} = \frac{\bar{Z}_2 \bar{Z}_3}{\bar{Z}_2 + \bar{Z}_3}$

$= \frac{(10-j12)(6+j10)}{(16-j2)} = 10.9+j3.1$

$\Rightarrow \bar{Z}_T = (4+j6) + (10.9+j3.1) = 14.9+j9.1 = 17.5 \angle 31.4^\circ \Omega$

* Now, finding $\bar{I} = ?!$

$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{200 \angle 0^\circ}{17.5 \angle 31.4^\circ} = 11.4 \angle -31.4^\circ \text{ A}$


* To draw the phasor diagram, we have (till now) \bar{V} and \bar{I} , then we have to find the following quantities:

* $\bar{V}_{AB} = \bar{I} \bar{Z}_1 = (11.4 \angle -31.4^\circ)(7.2 \angle 56.3^\circ) = 82.2 \angle 24.9^\circ \text{ volts}$

* $\bar{V}_{BC} = \bar{I} \bar{Z}_{23} = (11.4 \angle -31.4^\circ)(11.3 \angle 15.9^\circ) = 128.8 \angle -15.5^\circ \text{ volts}$

* $\bar{I}_2 = \frac{\bar{V}_{BC}}{\bar{Z}_2} = \frac{128.8 \angle -15.5^\circ}{15.6 \angle -50.2^\circ} = 8.25 \angle 34.7^\circ \text{ A}$

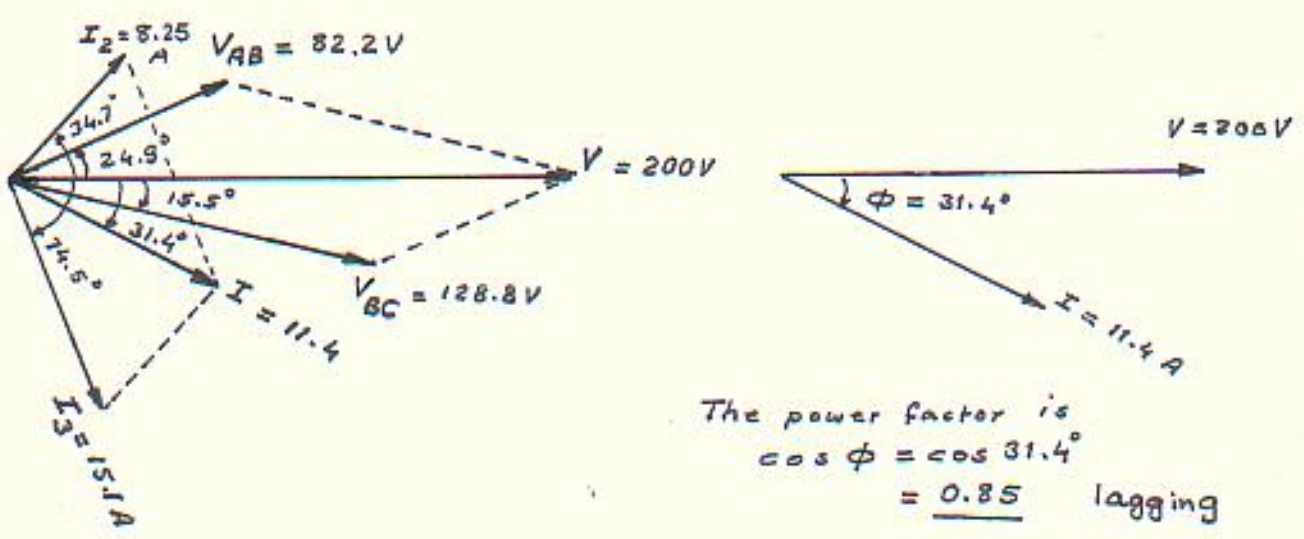* $\bar{I}_3 = \frac{128.8 \angle -15.5^\circ}{11.7 \angle 58^\circ} = 15.1 \angle -74.5^\circ \text{ A}$



The power factor is $\cos \phi = \cos 31.4^\circ = 0.85$ lagging

8. Resonance in AC Circuits


EEB

8.1 Resonance in Series AC Circuits

_____ : Consider the circuit shown;

* we have;

$$\bar{Z}_T = R + jX_L - jX_C$$

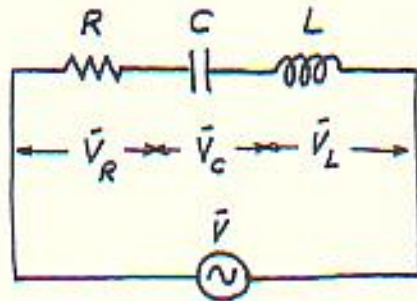


* At certain frequency (f_0), in the frequency response, we have:

$$X_L = X_C$$

* This frequency (f_0) is called the resonance frequency. Then, at this frequency:

$$\bar{Z}_T = R \Rightarrow \text{and hence;}$$

$$\bar{V} = \bar{V}_R = \bar{I}R$$

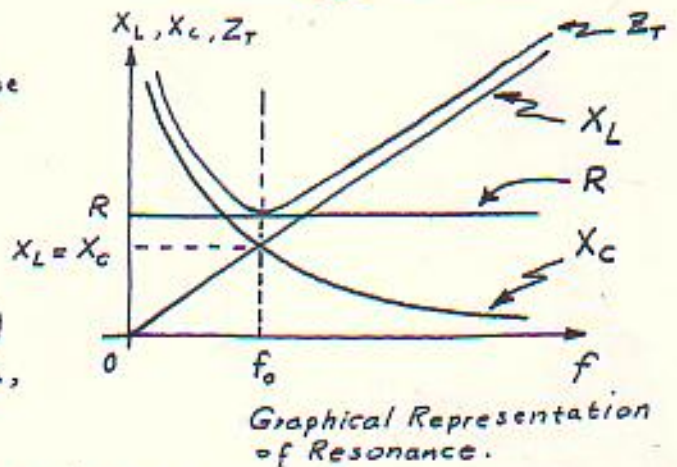

* The frequency at which resonance takes place, can be obtained as:

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C} \Rightarrow \omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\therefore f_0 = \frac{1}{2\pi\sqrt{LC}}$$

f_0 is in (Hz) if L is in Henry and C in Farad.


* Some points to remember (when an R-L-C circuit in resonance):

ي نفاط لوب س
تنكرها

- The overall (total) reactance of the circuit is zero (ie, $X_L - X_C = 0$).
- The circuit impedance is minimum (ie, $Z_T = R$).
- Circuit current is maximum, ($I_o = \frac{V}{Z} = \frac{V}{R}$).
- Circuit power factor angle is $0^\circ \Rightarrow Z_o$ ie, the power factor = 1.
- At resonance $\omega^2 LC = 1$.
- The quality factor Q_o (at resonance) = $\tan \phi = \frac{\omega_o L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$

* The Resonance Curve (Frequency Response):

Current at Resonance

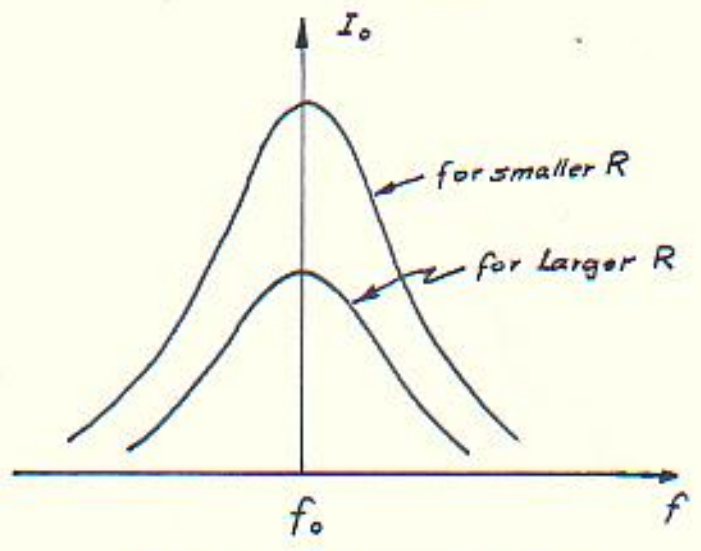


Typical Frequency Response (Resonance Curve) for a series R-L-C circuit in Resonance.

Bandwidth = $\Delta \omega = \omega_2 - \omega_1 \Rightarrow \Delta f = f_2 - f_1$

The narrower the bandwidth, the higher the selectivity of the circuit and vice-versa.

$$P_A = P_B = \left(\frac{I_o}{\sqrt{2}}\right)^2 R$$

$$= \frac{I_o^2 R}{2} = \frac{P}{2}$$

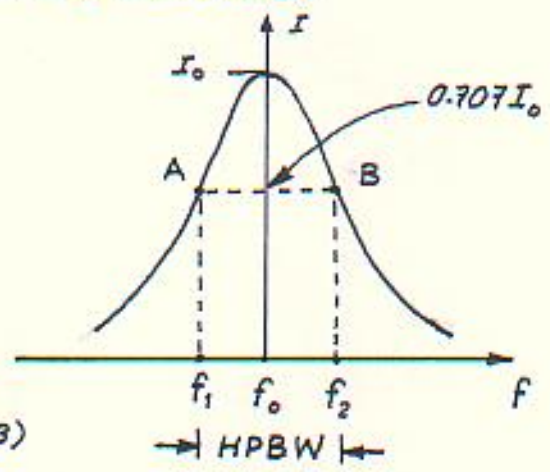

* Bandwidth is often called (HPBW) to denote the bandwidth at which half the power takes place.

* Also this bandwidth is called (-3dB) bandwidth for the same reason but in a logarithmic scale. (-3dB comes from $10 \log 0.5$).

In Summary

For an R-L-C circuit in resonance, the following remarks regarding the points A and B in the frequency response:

- Current is $\frac{I_0}{\sqrt{2}} = 0.707 I_0$
- Impedance is $\sqrt{2} R$ or $\sqrt{2} Z_0$
- $P_A = P_B = \frac{P_0}{2}$
- The circuit phase angle is $\phi = \pm 45^\circ$
- The quality factor = $Q = \tan \phi = \tan 45^\circ = 1$
- HPBW = $f_2 - f_1$

* How to find f_2 and f_1

* At lower half power frequencies; $\omega_1 < \omega_0 \Rightarrow \omega_1 L < \frac{1}{\omega_1 C}$
and $\phi = 45^\circ$.

$$\therefore \frac{1}{\omega_1 C} - \omega_1 L = R \Rightarrow \omega_1^2 + \frac{R}{L} \omega_1 - \frac{1}{LC} = 0$$

putting $\frac{\omega_0}{Q_0} = \frac{R}{L}$ and $\omega_0^2 = \frac{1}{LC}$ in the last equation, then

$$\therefore \omega_1^2 + \frac{\omega_0}{Q_0} \omega_1 - \omega_0^2 = 0$$

The positive solution of the above equation is

$$\omega_1 = \omega_0 \left[\sqrt{1 + \frac{1}{4Q_0^2}} - \frac{1}{2Q_0} \right]$$

* Similarly at the upper half power frequencies $\omega_2 > \omega_0$, the positive solution for ω_2 will be as:

$$\omega_2 = \omega_0 \left[\sqrt{1 + \frac{1}{4Q_0^2}} + \frac{1}{2Q_0} \right]$$

* for larger values of Q_0 (typically greater than 10), the factor $\frac{1}{4Q_0^2}$ becomes negligible compared to 1, then:

دعنا نبدأ

$$\begin{aligned} \omega_1 &= \omega_0 \left(1 - \frac{1}{2Q_0} \right) \\ &= \omega_0 \left(1 - \frac{1}{2 \frac{\omega_0 L}{R}} \right) \\ &= \omega_0 - \frac{\omega_0 R}{2\omega_0 L} \\ \therefore \omega_1 &= \omega_0 - \frac{R}{2L} \end{aligned}$$

$$\omega_1 = \omega_0 \left(1 - \frac{1}{2Q_0} \right)$$

the lower frequency limit.

$$\Rightarrow f_1 = f_0 - \frac{R}{4\pi L}$$

and:

$$\omega_2 = \omega_0 \left(1 + \frac{1}{2Q_0} \right)$$

the upper frequency limit.

Similarly

$$f_2 = f_0 + \frac{R}{4\pi L}$$

$$\therefore \text{HPBW} = f_2 - f_1 = \frac{R}{2\pi L}$$

$$\Rightarrow \text{HPBW} = f_0 / Q_0$$

Q - Factor of a resonant series circuit

: There are different ways to derive (or to define) the quality factor Q_0 of a series resonant circuit.

* It is given by the voltage magnification produced in the circuit at resonance ;

we have : $\bar{I}_0 = \frac{\bar{V}}{R}$ at resonance

$\therefore Q_0 \Rightarrow$ voltage magnification is $= \frac{V_{L0}}{V}$

$$\begin{aligned} \Rightarrow \frac{V_{L0}}{V} &= \frac{I_0 X_{L0}}{I_0 R} = \frac{\text{Reactive Power}}{\text{Active Power}} = \frac{X_{L0}}{R} = \frac{\omega_0 L}{R} \\ &= \frac{\text{Reactance}}{\text{Resistance}} \end{aligned}$$

OR

$$\begin{aligned} Q_0 &= \text{voltage magnification} = \frac{V_{C0}}{V} = \frac{I_0 X_{C0}}{I_0 R} = \frac{X_{C0}}{R} \\ &= \frac{\text{Reactive Power}}{\text{Active Power}} = \frac{1}{\omega_0 CR} \end{aligned}$$

** The quality factor can also be defined as:

الطاقة المخزنة في الملف $\frac{1}{2} LI^2$

$$\begin{aligned} Q_0 &= 2\pi \frac{\text{Maximum Energy stored}}{\text{Energy dissipated per cycle}} \\ &= 2\pi \cdot \frac{\frac{1}{2} L I^2}{I_0^2 R \cdot T_0} = 2\pi \left[\frac{\frac{1}{2} L (\sqrt{2} I_0)^2}{I_0^2 R \left(\frac{1}{f_0} \right)} \right] \end{aligned}$$

$$\therefore Q_0 = \frac{I_0^2 (2\pi f_0) L}{I_0^2 R} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR}$$

*** OR, the quality factor (Q_0 at resonance), can be obtained as:

$$\text{we have: } f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{and } Q_0 = \frac{\omega_0 L}{R} = \frac{\frac{1}{\sqrt{LC}} \cdot L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\therefore Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}}$$

NOTE: Higher values of the Q -factor mean not only higher voltage magnification but also mean high selectivity of the tuning circuit (resonant circuit).

\therefore In Summary

$$\begin{aligned} Q_0 &= \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = \frac{1}{R} \sqrt{\frac{L}{C}} = \sqrt{\frac{X_{L0} X_{C0}}{R}} \\ &= \frac{f_0}{\text{HPBW}} = \frac{f_0}{f_2 - f_1} \end{aligned}$$

Example

A 20Ω resistor is connected in series with an inductor, a capacitor and an ammeter across a 25 V supply with variable frequency. When the frequency is 400 Hz , the current is at its maximum value of 0.5 A , and the potential difference across the capacitor is 150 V . Calculate:

- the capacitance of the capacitor.
- the resistance and the inductance of the inductor.


Solution

\therefore the current is maximum $\Rightarrow \therefore$ the cct is in resonance

$$\therefore X_C = V_C / I_0 = 150 / 0.5 = 300 \Omega$$

$$(a). X_C = \frac{1}{2\pi f_0 C} \Rightarrow C = \frac{1}{2\pi f X_C}$$
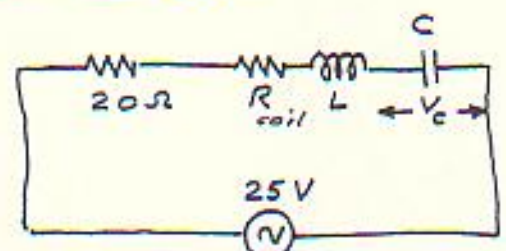
$$\therefore C = \frac{1}{2\pi(400)(300)} = 1.3 \mu\text{F}$$



$$(b). X_L = X_C = 300 \Omega = 2\pi f_0 L \Rightarrow L = \frac{300}{2\pi(400)} = 0.119 \text{ H}$$

* Now $R_{\text{coil}}?$ \Rightarrow

at resonance $Z_T = \text{Resistance of the circuit}$

$$\therefore \frac{V}{I_0} = R_T$$

$$\therefore \frac{25}{0.5} = 20 + R_{\text{coil}}$$

$$\therefore R_{\text{coil}} = 50 - 20 = \underline{30 \Omega}$$

Example

_____: An RLC circuit consists of a series resistance of $1 \text{ k}\Omega$, an inductance of 100 mH , and a capacitor of 10 pF . If a voltage of 100 V is applied across the combination, find:

- (a). the resonance frequency.
- (b). Q-factor of the circuit.
- (c). the half-power points.
- (d). The half-power bandwidth of the resonance frequency response.

Solution

_____:

(a). The resonance frequency $f_0 = ?$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{100 \times 10^{-3} \times 10 \times 10^{-12}}}$$

$$= \underline{159 \text{ kHz}}$$

(b). The quality factor of the circuit $Q_0 = ?$

$$Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{1000} \sqrt{\frac{100 \times 10^{-3}}{10 \times 10^{-12}}}$$

$$\therefore Q_0 = \underline{100}$$

(c). The half-power points $\Rightarrow f_1 = ?$ & $f_2 = ?$

$$* f_1 = f_0 - \frac{R}{4\pi L} = (159 \times 10^3) - \frac{1000}{4\pi \times 100 \times 10^{-3}}$$

$$\therefore f_1 = \underline{158.2 \text{ kHz}}$$

$$* f_2 = f_0 + \frac{R}{4\pi L} = (159 \times 10^3) + \frac{1000}{4\pi \times 100 \times 10^{-3}}$$

$$\therefore f_2 = \underline{159.8 \text{ kHz}}$$

(d). The half power bandwidth HPBW = ?

$$\text{HPBW} = f_2 - f_1 = 159.8 - 158.2 = \underline{1.6 \text{ kHz}}$$

OR \longleftrightarrow

بدراسة المسألة السابقة
كانت في:

$$\text{HPBW} = f_2 - f_1$$

$$= f_0 + \frac{R}{4\pi L} - f_0 + \frac{R}{4\pi L}$$


$$\therefore \text{HPBW} = \frac{R}{2\pi L}$$

حازك وبقول عنك
النسبة نفسها..

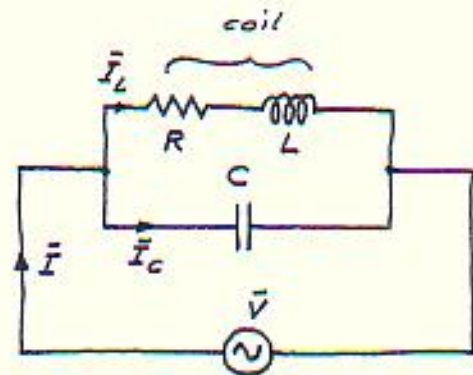8.2 Resonance in Parallel Circuits

Consider the parallel RLC circuit shown;


- For this circuit, the resulting phasor diagram can be obtained as shown in the Fig. below



- The **CONDITION** of resonance for this circuit takes place, when the two reactive components of the line current are **EQUAL**. This means that:

$$\bar{I}_C = \bar{I}_L \sin \phi_L$$
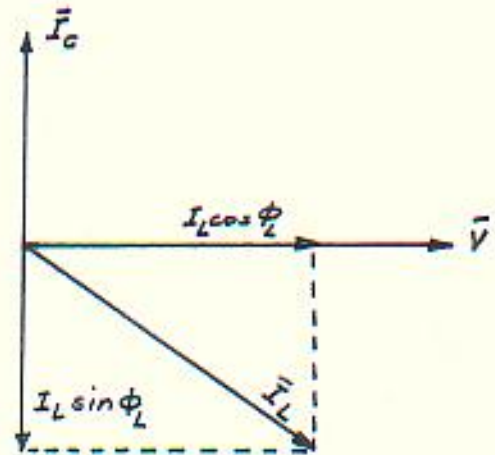
$$\text{or } \bar{I}_C - I_L \sin \phi_L = 0$$



- In terms of impedance, at resonance:


$$Z \sin \phi_L = X_L = X_C$$

$$\Rightarrow X_L = X_C \Rightarrow X_L \cdot X_C = Z^2$$

$$\omega_0 L \cdot \frac{1}{\omega_0 C} = Z^2$$

$$\frac{\omega_0 L}{\omega_0 C} = Z^2$$
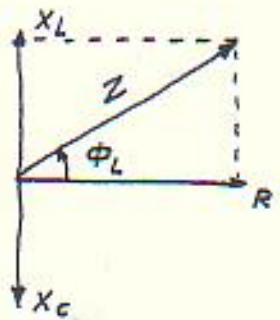
$$\text{But } \bar{Z} = R + jX_L \Rightarrow Z^2 = R^2 + X_L^2 \Rightarrow \frac{\omega_0 L}{\omega_0 C} = R^2 + X_L^2$$



$$\therefore \frac{L}{C} = R^2 + (2\pi f_0)^2 L^2 \Rightarrow (2\pi f_0)^2 L^2 = \frac{L}{C} - R^2$$

$$\therefore f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

* ملاحظة عند تكون المقاومة R صغيرة جداً

فإن: $f_0 = \frac{1}{2\pi\sqrt{LC}}$ كما في حالة رنين دوائر التوالي.

* Current at Resonance

Since the net reactive components of the current, at resonance, is zero, then;

$$\bar{I}_o - \bar{I}_L \sin \phi_L = 0$$

Thus the resultant current at resonance is only the real component (see the phasor diagram) which is:

$$\boxed{I_o = I_L \cos \phi_L}$$

$$\Rightarrow \bar{I}_L = \frac{\bar{V}}{Z}$$


$$\phi \cos \phi_L = \frac{R}{Z}$$

$$\therefore I_o = I_L \cos \phi_L = \frac{VR}{Z^2}$$

$$\text{but } Z^2 = \frac{L}{C} \Rightarrow I_o = \frac{VR}{L/C} = \frac{V}{L/CR}$$

$$\boxed{\therefore I_o = \frac{V}{L/CR}}$$

current at resonance

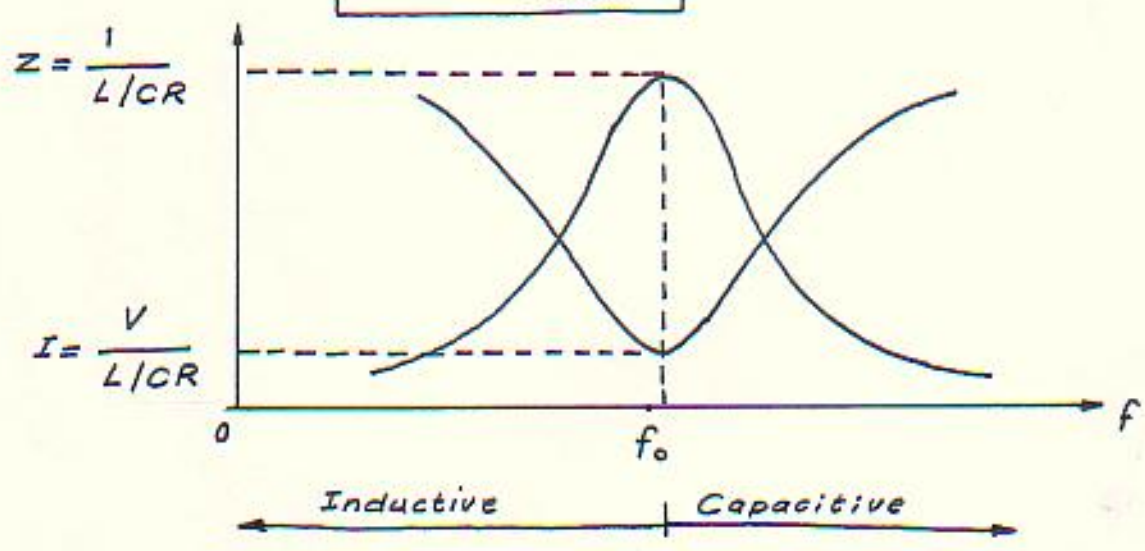


The impedance $[Z = \frac{1}{L/CR}]$ is called sometimes the effective impedance OR "the dynamic impedance".

*

طريقة اخرى
لإستنتاج هـ
وهي الطريقة
العامة

Alternative Method

using the admittance ;

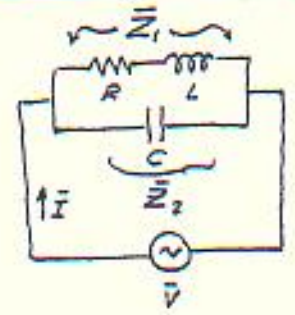

$$\bar{Y}_T = G + jB$$

$$\bar{Y}_1 = \frac{1}{\bar{Z}_1} = \frac{1}{R + jX_L} = \frac{R}{R^2 + X_L^2} - j \frac{X_L}{R^2 + X_L^2}$$

$$\bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{-jX_C} = j \frac{1}{X_C}$$

$$\therefore \bar{Y}_T = \bar{Y}_1 + \bar{Y}_2$$

$$\therefore \bar{Y}_T = \frac{R}{R^2 + X_L^2} + j \left(\frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} \right)$$

* In general, any circuit to be in resonance, the imaginary part (j-component) of the circuit impedance or admittance is zero.

Thus ; for our circuit mentioned earlier ;

$$\frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} = 0$$

$$\Rightarrow \frac{X_L}{R^2 + X_L^2} = \frac{1}{X_C} \Rightarrow X_L \cdot X_C = R^2 + X_L^2 = Z^2$$

وهي نفس النتيجة التي تم الحصول عليها سابقاً.

* Talking in terms of susceptance for parallel circuits, the net susceptance is zero at resonance condition. ($B = 0$).

It may be noted that at resonance, the admittance is equal to the conductance (G)

Points to Remember

The following points about parallel resonance should be noted and compared with those about series resonance. At resonance :

- Net susceptance is zero ($B_T = 0$).
- The admittance equal to the conductance.
- Reactive component of the line current is zero.
- Dynamic impedance = L/CR
- Line current at resonance is minimum and equal $\frac{V}{L/CR}$ but it is phase with the applied voltage.
- Power factor of the circuit is unity.

Bandwidth of the Parallel Resonant Circuit

Bandwidth: The bandwidth of a parallel circuit is defined in the same way as that for a series circuit. This circuit also has upper and lower half-power frequencies where power dissipated is half of that at resonant frequency.

Quality Factor of a Parallel Circuit

Quality Factor: It is defined as the current magnification (in the C-branch or in the coil branch) with respect to the line current drawn from the supply. This means that:

$$Q\text{-factor at resonance} \Rightarrow Q_0 = \frac{\bar{I}_C}{\bar{I}}$$

$$\bar{I}_C = \frac{\bar{V}}{X_C} = \frac{\bar{V}}{1/\omega C}$$

$$= \omega C \bar{V}$$

and

$$\bar{I} = \frac{\bar{V}}{L/CR}$$

$$\therefore Q_0 = \frac{\omega C \bar{V}}{\frac{\bar{V}}{L/CR}} = \omega C \bar{V} \times \frac{L/CR}{\bar{V}}$$

$$\therefore Q_0 = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R}$$

which is the same as that for series circuits.

$$\therefore Q_0 = \tan \phi$$

Other expressions relating Q_0 can be used in parallel circuits as had been used for series circuits.

Example

Example: A capacitor is connected in parallel with a coil having $L = 5.52 \text{ mH}$ and $R = 10 \Omega$, to a 100 V , 50 Hz supply. Calculate the value of the capacitance for which the current taken from the supply is in phase with the applied voltage.

Solution

Solution: Since the current taken from the supply is in phase with the applied voltage \Rightarrow The circuit is in resonance.

Then, at resonance;

$$Z^2 = \frac{L}{C} \quad \text{or} \quad C = L/Z^2$$

$$X_L = 2\pi fL = 2\pi(50) 5.52 \times 10^{-3} = 1.734 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} \Rightarrow$$

$$\therefore Z^2 = 10^2 + 1.734^2 \Rightarrow Z = 10.1 \Omega$$

$$\therefore C = \frac{L}{Z^2} = \frac{5.52 \times 10^{-3}}{(10.1)^2} = 54.6 \mu\text{F}$$

Example

Calculate the impedance of the parallel-tuned circuit shown at a frequency of 500 kHz and fo a bandwidth of operation equal to 20 kHz. The resistance of the coil is 5Ω.

Solution

HPBW = R / (2πL) = 20 x 10^3 Hz

L = 5 / (2π(20 x 10^3)) = 39 μH



f0 = 500 x 10^3 Hz = 1 / (2π * sqrt(1/LC - R^2/L^2)) = 1 / (2π * sqrt(1/(39 x 10^-6 C) - (5^2 / (39 x 10^-6)^2)))

C = 2.6 x 10^-9 F = 2.6 nF

Z = L / CR = (39 x 10^-6) / (2.6 x 10^-9 * 5) = 3 kΩ

ملاحظة: في حال اضناة اي عنصر الى الدارة المذكورة في المثال ، فلا بد من استشارة الملائمة الخاصة بـ (f0) كما تعلمنا سابقاً.

Example

For a series R.L.C circuit, the inductor is variable. The source voltage is $(\sqrt{2} 200 \sin 100\pi t)$. Maximum current obtained by varying the inductance is 0.314 A and the voltage across the capacitor is 300 V. Find the circuit elements.

Solution

Max. current \Rightarrow Resonant conditions, then:

$I_m = I_0 = \frac{V}{R}$ and also $V_L = V_C$

$\therefore R = \frac{V}{I_m} = \frac{200}{0.314} = 637 \Omega$

$V_C = I_0 X_C = \frac{I_0}{\omega_0 C}$ $\omega_0 = 100\pi$

$\therefore C = \frac{I_0}{\omega_0 V_C} = \frac{0.314}{(100\pi)(300)} = 3.33 \mu F$

$V_L = I_0 X_L = I_0 (2\pi f_0) L = I_0 \omega_0 L$

$\therefore L = \frac{V_L}{\omega_0 I_0} = \frac{300}{(100\pi)(0.314)} = 3.03 H$

دقتاً
 $V_L = V_C$
at Resonance

Example

A coil having an inductance of 50 mH and a resistance of 10 Ω is connected in series with a 25 μF capacitor across a 200 V ac supply. Calculate:

- (a). resonance frequency of the circuit.
- (b). current flowing at resonance.
- (c). the value of Q_0 using different expressions.

Solution

(a). $f_0 = \frac{1}{2\pi\sqrt{LC}}$

$= \frac{1}{2\pi\sqrt{50 \times 10^{-3} \times 25 \times 10^{-6}}}$

$= 142.3 Hz.$

TSB

(b). $I_0 = \frac{V}{R} = \frac{200}{10} = 20 \text{ A}$

(c). $Q_0 = \frac{\omega_0 L}{R} = \frac{2\pi \times 142.3 \times 50 \times 10^{-3}}{10} = 4.47$

or

$Q_0 = \frac{1}{\omega_0 CR} = \frac{1}{2\pi \times 142.3 \times 25 \times 10^{-6} \times 10} = 4.47$

or

$Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{50 \times 10^{-3}}{25 \times 10^{-6}}} = 4.47$

ملاحظة: في هذا المثال
 ان Q_0 (معامل جودة
 دائرة الرنين) هو نفسه
 Q (معامل جودة الملف)
 وذلك لتوجه مقادير
 اضافة اخرى بما مقادير
 الملف؛ لهذا ذلك
 مستبعداً حيث ان اية مقارنة
 اضافية (عند سعة توليد
 تيار في سعة Q_0).

Example

A series R-L-C circuit consists of $R = 1000 \Omega$, $L = 100 \text{ mH}$ and $C = 10 \text{ pF}$. The applied voltage across the circuit is 100 V . Then;

- (a). Find the resonant frequency of the circuit.
- (b). Find the quality factor of the circuit at the resonant freq.
- (c). At what angular frequencies do the half power points occur?
- (d). Calculate the HPBW of the resonance curve.

Solution

ملاحظة: الوصول في اطلق
 ان تسمى (f_0) !

(a). $f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{100 \times 10^{-3} \times 10 \times 10^{-12}}} = 159.15 \text{ kHz}$

(b). $Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{1000} \times \sqrt{\frac{1000 \times 10^{-3}}{10 \times 10^{-12}}} = 100$

(c). $HPBW = \frac{R}{2\pi L} = \frac{1000}{2\pi \times 100 \times 10^{-3}} = 1591.5 \text{ Hz}$

more general relation

$HPBW = f_0 / Q_0 = \frac{159.15 \times 10^3}{100} = 1591.5 \text{ Hz}$

(d). $\omega_1 = \omega_0 \left(1 - \frac{1}{2Q_0}\right) = 2\pi \times 159.15 \times 10^3 \left(1 - \frac{1}{2 \times 100}\right)$
 $= 994.464 \times 10^3 \text{ rad/sec.}$

& $\omega_2 = \omega_0 \left(1 + \frac{1}{2Q_0}\right) = 2\pi \times 159.15 \times 10^3 \left(1 + \frac{1}{2 \times 100}\right)$
 $= 1004.459 \times 10^3 \text{ rad/sec.}$

اد بملامسة اخرى انك محوسبة
 تستخدم جميع انواع دوائر
 الرنين.

⊕ ملاحظة: من يمكنه استخدام الملامسة الاكثر محوسبة:

$\omega_1 = \omega_0 - \frac{HPBW}{2}$

& $\omega_2 = \omega_0 + \frac{HPBW}{2}$