

## Architecture, Programming, and Interfacing

# Barry B. Brey

# Chapter 11: Basic I/O Interface

# Introduction

- This chapter outlines some of the basic methods of communications, both serial and parallel, between humans or machines and the microprocessor.
- We first introduce the basic I/O interface and discuss decoding for I/O devices.
- Then, we provide detail on parallel and serial interfacing, both of which have a variety of applications.

# Chapter Objectives

**Upon completion of this chapter, you will be able to:**

- Explain the operation of the basic input and output interfaces.
- Decode an 8-, 16-, and 32-bit I/O device so that they can be used at any I/O port address.
- Define handshaking and explain how to use it with I/O devices.
- Interface and program the 82C55 programmable parallel interface.

# Chapter Objectives

(*cont.*)

**Upon completion of this chapter, you will be able to:**

- Interface LCD displays, LED displays, keyboards, ADC, DAC, and various other devices to the 82C55.
- Interface and program the 16550 serial communications interface adapter.
- Interface and program the 8254 programmable interval timer.

# Chapter Objectives

(*cont.*)

**Upon completion of this chapter, you will be able to:**

- Interface an analog-to-digital converter and a digital-to-analog converter to the microprocessor.
- Interface both DC and stepper motors to the microprocessor.

# 11–1 INTRO TO I/O INTERFACE

- I/O instructions (IN, INS, OUT, and OUTS) are explained.
- Also isolated (direct or I/O mapped I/O) and memory-mapped I/O, the basic input and output interfaces, and handshaking.
- Knowledge of these topics makes it easier to understand the connection and operation of the programmable interface components and I/O techniques.

# The I/O Instructions

- One type of instruction transfers information to an I/O device (OUT).
- Another reads from an I/O device (IN).
- Instructions are also provided to transfer strings of data between memory and I/O.
  - INS and OUTS, found except the 8086/8088



- Instructions that transfer data between an I/O device and the microprocessor's accumulator (AL, AX, or EAX) are called **IN** and **OUT**.
- The I/O address is stored in register DX as a 16-bit address or in the byte (p8) immediately following the opcode as an 8-bit address.
  - Intel calls the 8-bit form (p8) a **fixed address** because it is stored with the instruction, usually in a ROM
- The 16-bit address is called a **variable address** because it is stored in a DX, and then used to address the I/O device.



- Other instructions that use DX to address I/O are the INS and OUTS instructions.
- I/O ports are 8 bits in width.
  - a 16-bit port is actually two consecutive 8-bit ports being addressed
  - a 32-bit I/O port is actually four 8-bit ports

- When data are transferred using IN or OUT, the I/O address, (**port number** or simply port), appears on the address bus.
- External I/O interface decodes the port number in the same manner as a memory address.
  - the 8-bit fixed port number (p8) appears on address bus connections  $A_7$ – $A_0$  with bits  $A_{15}$ – $A_8$  equal to  $00000000_2$
  - connections above  $A_{15}$  are undefined for I/O instruction

- The 16-bit variable port number (DX) appears on address connections  $A_{15}$ – $A_0$ .
- The first 256 I/O port addresses (00H–FFH) are accessed by both fixed and variable I/O instructions.
  - any I/O address from 0100H to FFFFH is only accessed by the variable I/O address
- In a PC computer, all 16 address bus bits are decoded with locations 0000H–03FFH.
  - used for I/O inside the PC on the ISA (**industry standard architecture**) bus

- INS and OUTS instructions address an I/O device using the DX register.
  - but do not transfer data between accumulator and I/O device as do the IN/OUT instructions
  - Instead, they transfer data between memory and the I/O device
- Pentium 4 and Core2 operating in the 64-bit mode have the same I/O instructions.
- There are no 64-bit I/O instructions in the 64-bit mode.
  - most I/O is still 8 bits and likely will remain so

# Isolated and Memory-Mapped I/O

- Two different methods of interfacing I/O: **isolated I/O** and **memory-mapped I/O**.
- In isolated I/O, the IN, INS, OUT, and OUTS transfer data between the microprocessor's accumulator or memory and the I/O device.
- In memory-mapped I/O, any instruction that references memory can accomplish the transfer.
- The PC does not use memory-mapped I/O.




# *Isolated I/O*

- The most common I/O transfer technique used in the Intel-based system is isolated I/O.
  - *isolated* describes how I/O locations are isolated from memory in a separate I/O address space
- Addresses for isolated I/O devices, called ports, are separate from memory.
- Because the ports are separate, the user can expand the memory to its full size without using any of memory space for I/O devices.

- A disadvantage of isolated I/O is that data transferred between I/O and microprocessor must be accessed by the IN, INS, OUT, and OUTS instructions.
- Separate control signals for the I/O space are developed (using  $M/\overline{IO}$  and  $W/\overline{R}$  ), which indicate an I/O read ( $\overline{IORC}$ ) or an I/O write ( $\overline{RD}$ ) operation.
- These signals indicate an I/O port address, which appears on the address bus, is used to select the I/O device.



**Figure 11–1** The memory and I/O maps for the 8086/8088 microprocessors. (a) Isolated I/O. (b) Memory-mapped I/O.

   


- in the PC, isolated I/O ports are used to control peripheral devices
- an 8-bit port address is used to access devices located on the system board, such as the timer and keyboard interface
- a 16-bit port is used to access serial and parallel ports, video and disk drive systems

# ***Memory-Mapped I/O***

- Memory-mapped I/O does not use the IN, INS, OUT, or OUTS instructions.
- It uses any instruction that transfers data between the microprocessor and memory.
  - treated as a memory location in memory map
- Advantage is any memory transfer instruction can access the I/O device.
- Disadvantage is a portion of memory system is used as the I/O map.
  - reduces memory available to applications

# Personal Computer I/O Map

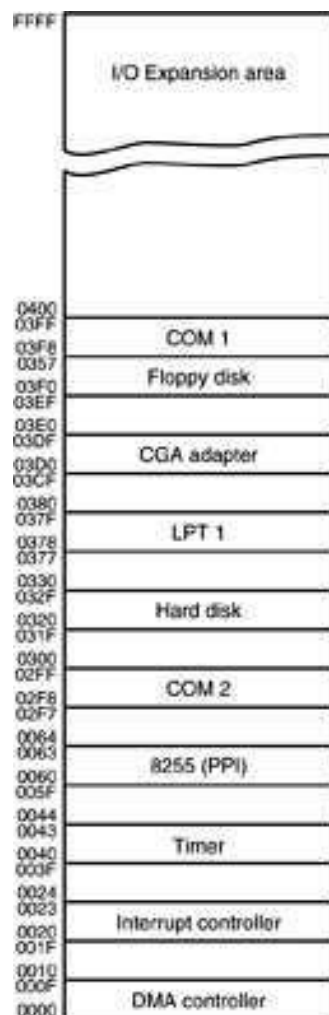

- the PC uses part of I/O map for dedicated functions, as shown here
- I/O space between ports 0000H and 03FFH is normally reserved for the system and ISA bus
- ports at 0400H–FFFFH are generally available for user applications, main-board functions, and the PCI bus
- 80287 coprocessor uses 00F8H–00FFH, so Intel reserves I/O ports 00F0H–00FFH

**Figure 11–2** I/O map of a personal computer illustrating many of the fixed I/O areas.


# Basic Input and Output Interfaces

- The basic input device is a set of three-state buffers.
- The basic output device is a set of data latches.
- The term IN refers to moving data *from* the I/O device *into* the microprocessor and
- The term OUT refers to moving data *out* of the microprocessor *to* the I/O device.

# ***The Basic Input Interface***

- Three-state buffers are used to construct the 8-bit input port depicted in Figure 11–3.
- External TTL data are connected to the inputs of the buffers.
  - buffer outputs connect to the data bus
- The circuit of allows the processor to read the contents of the eight switches that connect to any 8-bit section of the data bus when the select signal becomes a logic 0.

**Figure 11–3** The basic input interface illustrating the connection of eight switches. Note that the 74ALS244 is a three-state buffer that controls the application of the switch data to the data bus.

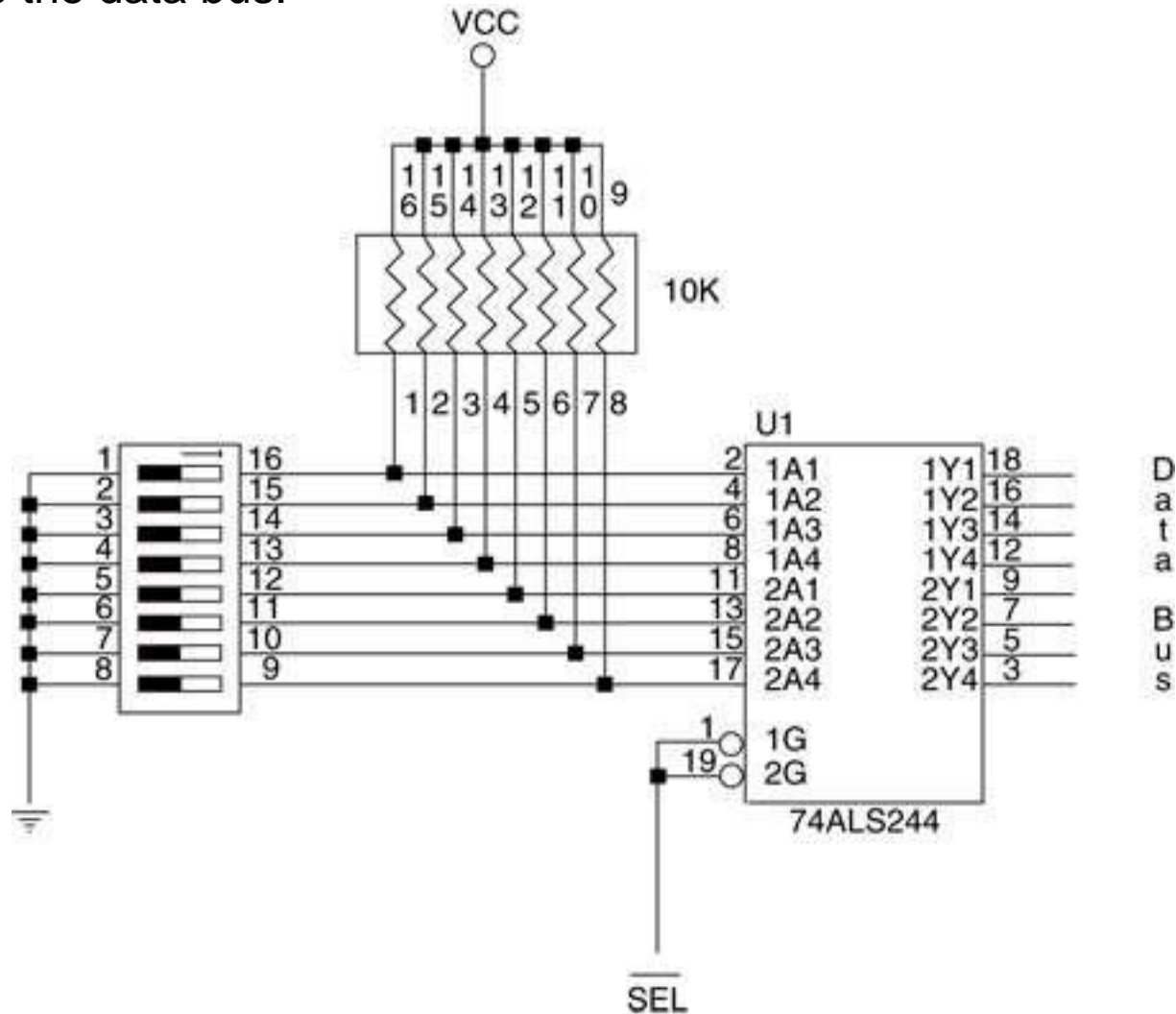


- When the IN instruction executes, contents of the switches copy to the AL register.
- This basic input circuit is not optional and must appear any time input data are interfaced to the microprocessor.
- Sometimes it appears as a discrete part of the circuit, as shown in Figure 11–3.
  - also built into a programmable I/O devices
- Sixteen- or 32-bit data can also be interfaced but is not nearly as common as 8-bit data.



# ***The Basic Output Interface***

- Receives data from the processor and usually must hold it for some external device.
  - latches or flip-flops, like buffers in the input device, are often built into the I/O device
- Fig 11–4 shows how eight light-emitting diodes (LEDs) connect to the processor through a set of eight data latches.
- The latch stores the number output by the microprocessor from the data bus so that the LEDs can be lit with any 8-bit binary number.

**Figure 11–4** The basic output interface connected to a set of LED displays.

 


- Latches hold the data because when the processor executes an OUT, data are only present on the data bus for less than  $1.0\ \mu\text{s}$ .
  - the viewer would never see the LEDs illuminate
- When the OUT executes, data from AL, AX, or EAX transfer to the latch via the data bus.
- Each time the OUT executes, the  $\overline{\text{SEL}}$  signal activates, capturing data to the latch.
  - data are held until the next OUT
- When the output instruction is executed, data from the AL register appear on the LEDs.

# Handshaking

- Many I/O devices accept or release information slower than the microprocessor.
- A method of I/O control called **handshaking** or **polling**, synchronizes the I/O device with the microprocessor.
- An example is a parallel printer that prints a few hundred characters per second (CPS).
- The processor can send data much faster.
  - a way to slow the microprocessor down to match speeds with the printer must be developed

- Fig 11–5 illustrates typical input and output connections found on a printer.
  - data transfers via data connections ( $D_7$ – $D_0$ )
- ASCII data are placed on  $D_7$ – $D_0$ , and a pulse is then applied to the  $\overline{STB}$  connection.
  - BUSY indicates the printer is busy
  - $\overline{STB}$  is a clock pulse used to send data to printer
- The strobe signal sends or clocks the data into the printer so that they can be printed.
  - as the printer receives data, it places logic 1 on the BUSY pin, indicating it is printing data

**Figure 11–5** The DB25 connector found on computers and the Centronics 36-pin connector found on printers for the Centronics parallel printer interface.

 

DB25 Pin number	CENT36 Pin number	Function	DB25 Pin number	CENT36 Pin number	Function
1	1	Data Strobe	12	12	Paper empty
2	2	Data 0 (D0)	13	13	Select
3	3	Data 1 (D1)	14	14	Afd
4	4	Data 2 (D2)	15	32	Error
5	5	Data 3 (D3)	16	—	RESET
6	6	Data 4 (D4)	17	31	Select in
7	7	Data 5 (D5)	18–25	19–30	Ground
8	8	Data 6 (D6)	—	17	Frame ground
9	9	Data 7 (D7)	—	16	Ground
10	10	Ack	—	33	Ground
11	11	Busy			

- The software polls or tests the BUSY pin to decide whether the printer is busy.
  - If the printer is busy, the processor waits
  - if not, the next ASCII character goes to the printer
- This process of interrogating the printer, or any asynchronous device like a printer, is called handshaking or polling.




# ***Input Devices***

- Input devices are already TTL and compatible, and can be connected to the microprocessor and its interfacing components.
  - or they are switch-based
- Switch-based devices are either open or connected; These are not TTL levels.
  - TTL levels are a logic 0 (0.0 V–0.8 V)
  - or a logic 1 (2.0 V–5.0 V)
- Using switch-based device as TTL-compatible input requires conditioning applied.


- Fig 11–6 shows a toggle switch properly connected to function as an input device.
- A pull-up resistor ensures when the switch is open, the output signal is a logic 1.
  - when the switch is closed, it connects to ground, producing a valid logic 0 level
- A standard range of values for pull-up resistors is between 1K Ohm and 10K Ohm.

**Figure 11–6** A single-pole, single-throw switch interfaced as a TTL device.

 


- Mechanical switch contacts physically bounce when they are closed,
  - which can create a problem if a switch is used as a clocking signal for a digital circuit
- To prevent problems with bounces, one of the circuits shown in Fig 11–7 can be used.
  - the first is a classic textbook bounce eliminator
  - second is a more practical version of the same
- The first version costs more to construct
  - the second costs requires no pull-up resistors and two inverters instead of two NAND gates

**Figure 11–7** Debouncing switch contacts: (a) conventional debouncing and (b) practical debouncing.

 

(a)

 

(b)

- as the Q input from the switch becomes a logic 0, it changes the state of the flip-flop
- if the contact bounces away from the Q input, the flip-flop remembers, no change occurs, and thus no bounce


# ***Output Devices***

- Output devices are more diverse than input devices, but many are interfaced in a uniform manner.
- Before an output device can be interfaced, we must understand voltages and currents from the microprocessor or TTL interface.
- Voltages are TTL-compatible from the microprocessor of the interfacing element.
  - logic 0 = 0.0 V to 0.4 V
  - logic 1 = 2.4 V to 5.0 V


- Currents for a processor and many interfacing components are less than for standard TTL.
  - Logic 0 = 0.0 to 2.0 mA
  - logic 1 = 0.0 to 400  $\mu$ A
- Fig 11–8 shows how to interface a simple LED to a microprocessor peripheral pin.
  - a transistor driver is used in 11–8(a)
  - a TTL inverter is used in 11–8(b)
- The TTL inverter (standard version) provides up to 16 mA of current at a logic 0 level
  - more than enough to drive a standard LED



**Figure 11–8** Interfacing an LED: (a) using a transistor and (b) using an inverter.

 

(a)

 

(b)

- TTL input signal has minimum value of 2.4 V
- Drop across emitter-base junction is 0.7 V.
- The difference is 1.7 V
  - the voltage drop across the resistor
- The value of the resistor is  $1.7\text{ V} \div 0.1\text{ mA}$  or 17K  $\Omega$ .
  - as 17K  $\Omega$  is not a standard value, an 18K  $\Omega$  resistor is chosen


- In 11–8(a), we elected to use a switching transistor in place of the TTL buffer.
  - 2N2222 is a good low-cost, general-purpose switching transistor with a minimum gain of 100
  - collector current is 10 mA; so base current will be 1/100 of collector current of 0.1 mA
- To determine the value of the base current–limiting resistor, use the 0.1 mA base current and a voltage drop of 1.7 V across the base current–limiting resistor.

- Suppose we need to interface a 12 V DC 1A motor to the microprocessor.
- We cannot use a TTL inverter:
  - 12 V signal would burn out the inverter
  - current far exceeds 16 mA inverter maximum
- We cannot use a 2N2222 transistor:
  - maximum current is 250 mA to 500 mA, depending on the package style chosen
- The solution is to use a Darlington-pair, such as a TIP120.
  - costs 25¢, can handle 4A current with heat sink

- Fig 11–9 illustrates a motor connected to the Darlington-pair with a minimum current gain of 7000 and a maximum current of 4A.
- Value of the bias resistor is calculated exactly the same as the one used in the LED driver.
- The current through the resistor is  $1.0 \text{ A} \div 7000$ , or about 0.143 mA.
- Voltage drop is 0.9 V because of the two diode drops (base/emitter junctions).
- The value of the bias resistor is  $0.9 \text{ V} \div 0.143 \text{ mA}$  or 6.29K  $\Omega$ .

**Figure 11–9** A DC motor interfaced to a system by using a Darlington-pair.

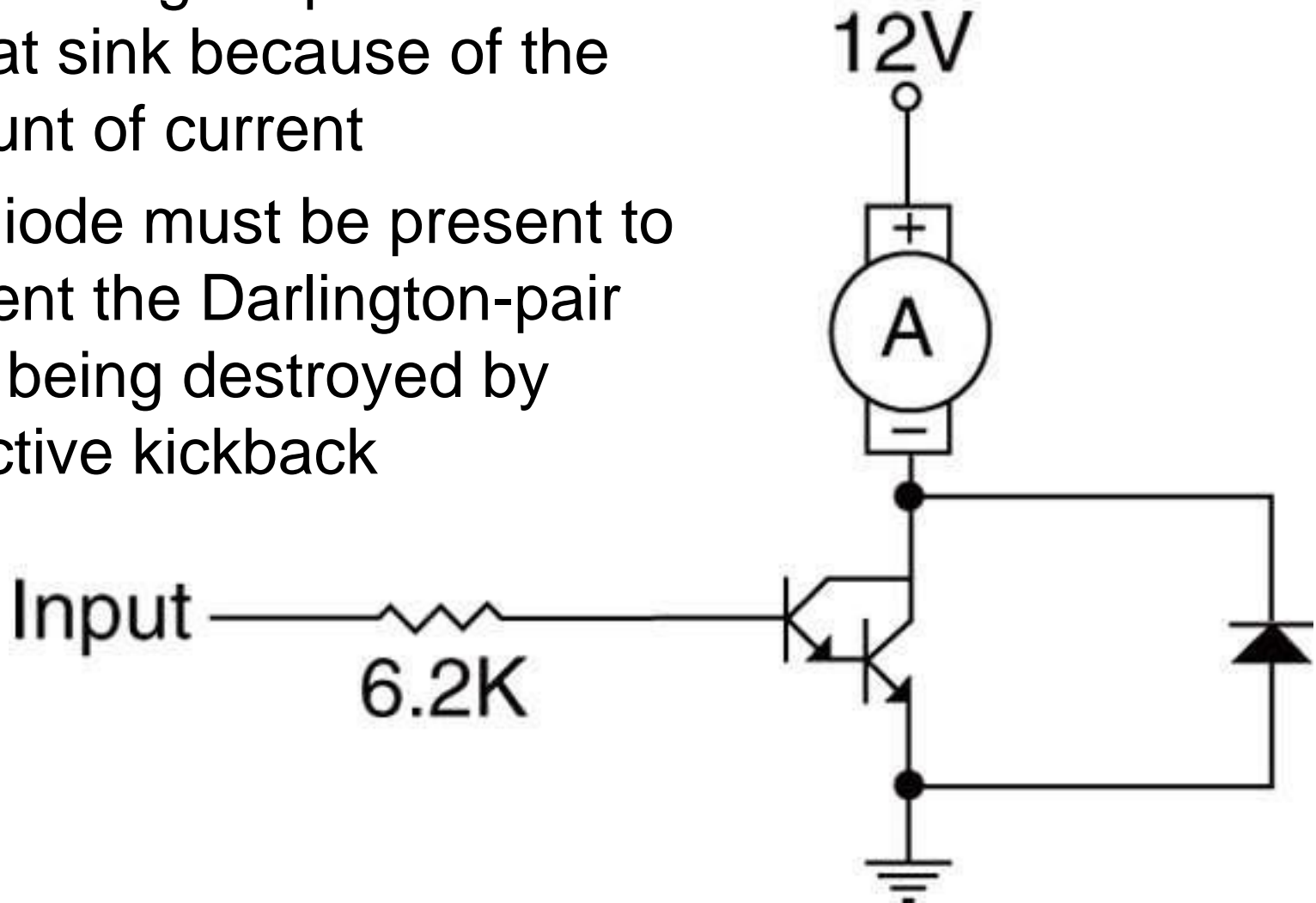- The Darlington-pair must use a heat sink because of the amount of current
- the diode must be present to prevent the Darlington-pair from being destroyed by inductive kickback



# 11–2 I/O PORT ADDRESS DECODING

- Very similar to memory address decoding, especially for memory-mapped I/O devices.
- The difference between memory decoding and isolated I/O decoding is the number of address pins connected to the decoder.
- In the personal computer system, we always decode all 16 bits of the I/O port address.


# Decoding 8-Bit I/O Port Addresses

- Fixed I/O instruction uses an 8-bit I/O port address that on  $A_{15}-A_0$  as 0000H–00FFH.
  - we often decode only address connections  $A_7-A_0$  for an 8-bit I/O port address
- The DX register can also address I/O ports 00H–FFH.
- If the address is decoded as an 8-bit address, we can never include I/O devices using a 16-bit address.
  - the PC never uses or decodes an 8-bit address




- Figure 11–10 shows a 74ALS138 decoder that decodes 8-bit I/O ports F0H - F7H.
  - identical to a memory address decoder except we only connect address bits  $A_7$ – $A_0$  to the inputs of the decoder
- Figure 11–11 shows the PLD version, using a GAL22V10 (a low-cost device) for this decoder.
- The PLD is a better decoder circuit because the number of integrated circuits has been reduced to one device.

**Figure 11–10** A port decoder that decodes 8-bit I/O ports. This decoder generates active low outputs for ports F0H–F7H.

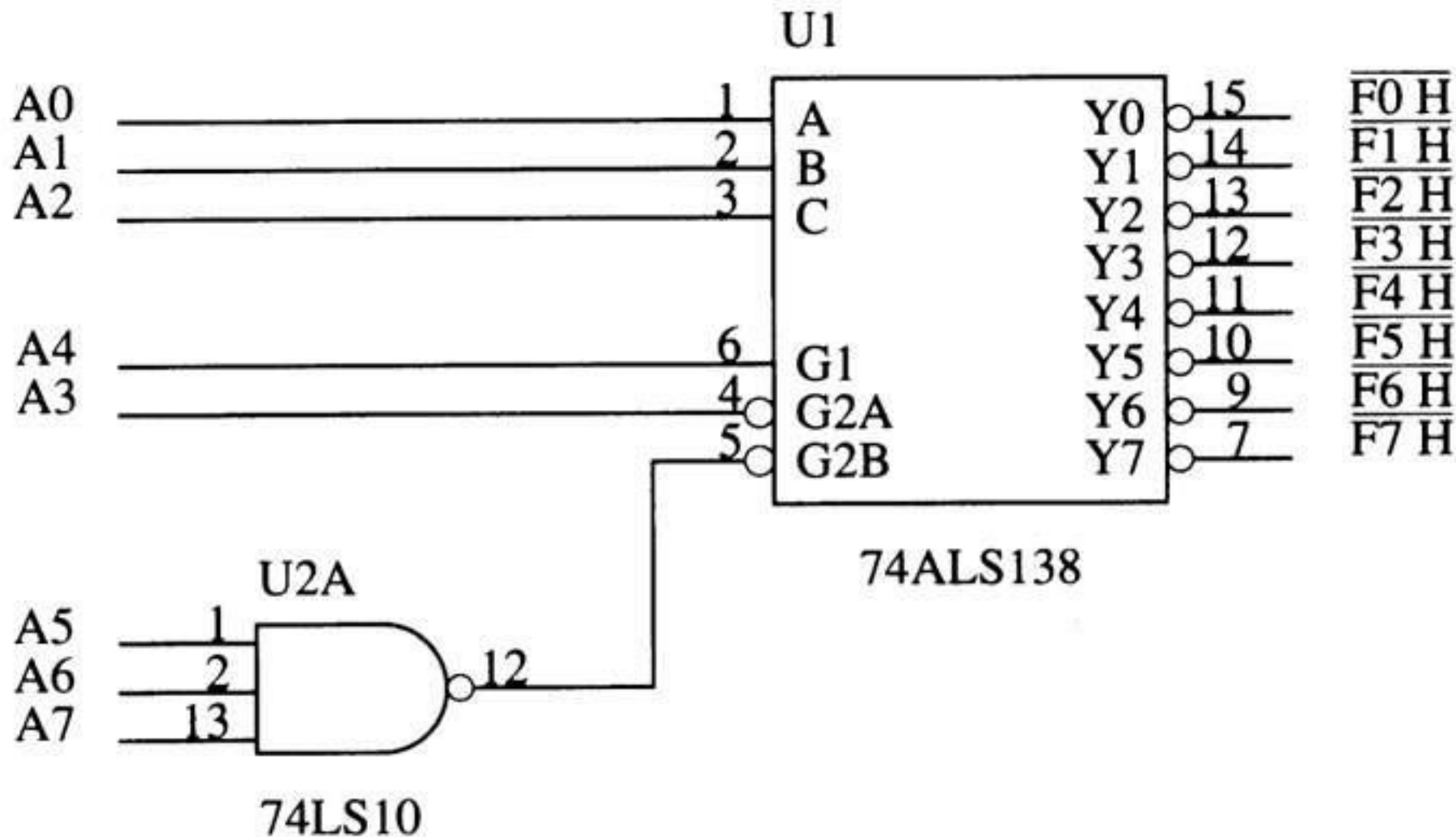


**Figure 11–11** A PLD that generates part selection signals

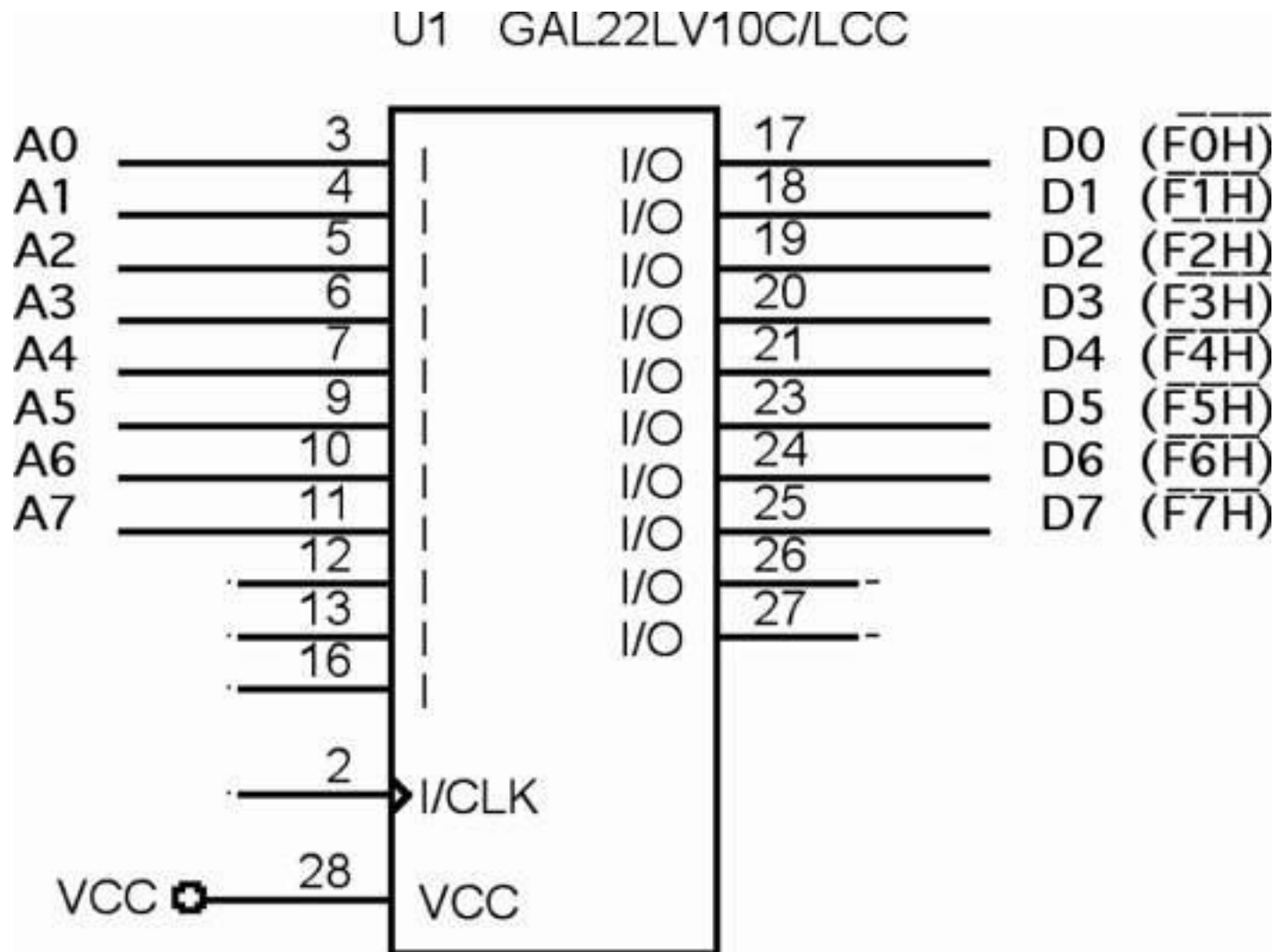

# Decoding 16-Bit I/O Port Addresses

- PC systems typically use 16-bit I/O addresses.
  - 16-bit addresses rare in embedded systems
- The difference between decoding an 8-bit and a 16-bit I/O address is that eight additional address lines ( $A_{15}$ – $A_8$ ) must be decoded.
- Figure 11–12 illustrates a circuit that contains a PLD and a 4-input NAND gate used to decode I/O ports EFF8H–EFFFH.
- PLD generates address strobes for I/O ports


**Figure 11–12** A PLD that decodes 16-bit I/O ports EFF8H through EFFFH.

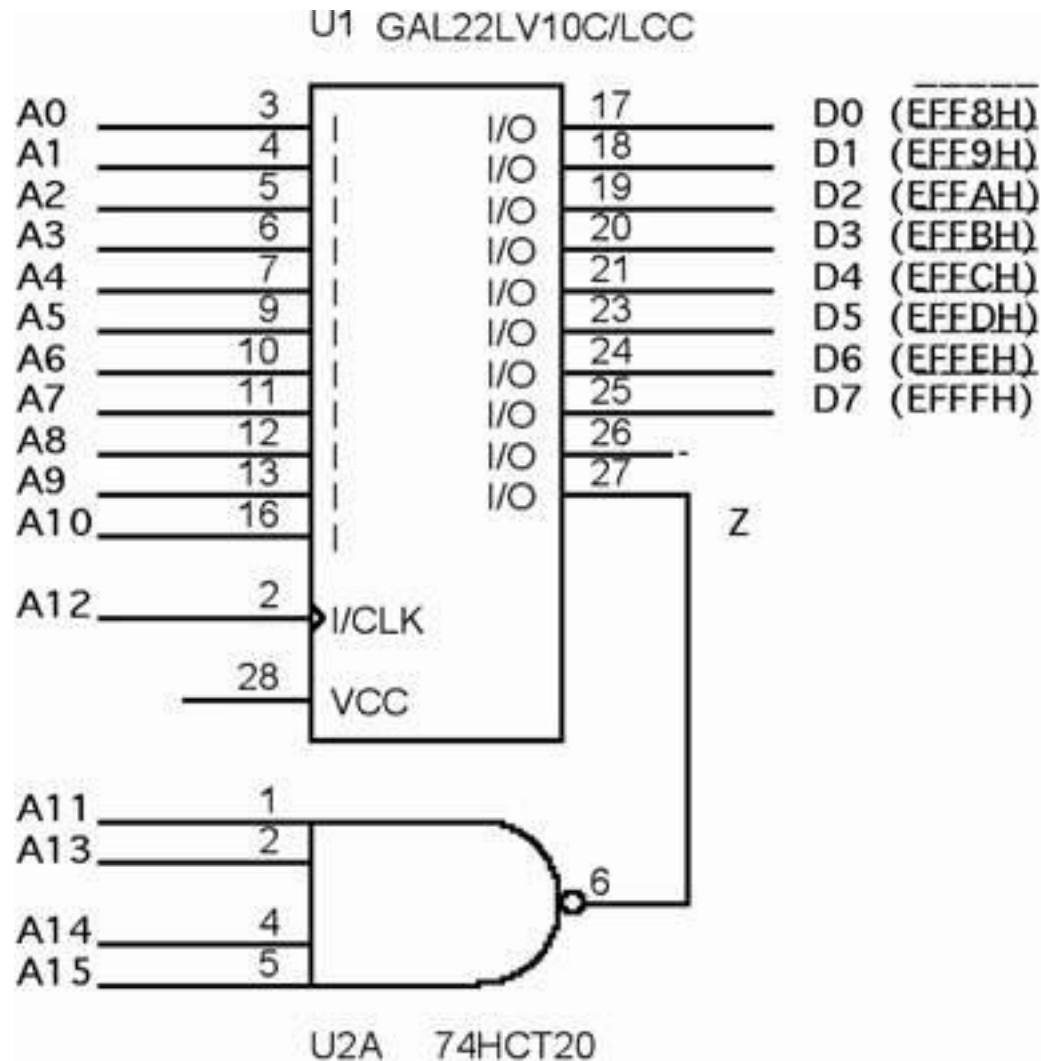

# 8- and 16-Bit Wide I/O Ports

- Data transferred to an 8-bit I/O device exist in one of the I/O banks in a 16-bit processor such as 80386SX.
- The I/O system on such a microprocessor contains two 8-bit memory banks.
- Fig 11–13 shows separate I/O banks for a 16-bit system such as 80386SX.
- Because two I/O banks exist, any 8-bit I/O write requires a separate write.


**Figure 11–13** The I/O banks found in the 8086, 80186, 80286, and 80386SX.

 

- I/O reads don't require separate strobes.
  - as with memory, the processor reads only the byte it expects and ignores the other byte
  - a read can cause problems when an I/O device responds incorrectly to a read operation
- Fig 11–14 shows a system with two different 8-bit output devices, located at 40H and 41H.
- These are 8-bit devices and appear in different I/O banks.
  - thus, separate I/O write signals are generated to clock a pair of latches that capture port data




**Figure 11–14** An I/O port decoder that selects ports 40H and 41H for output data.

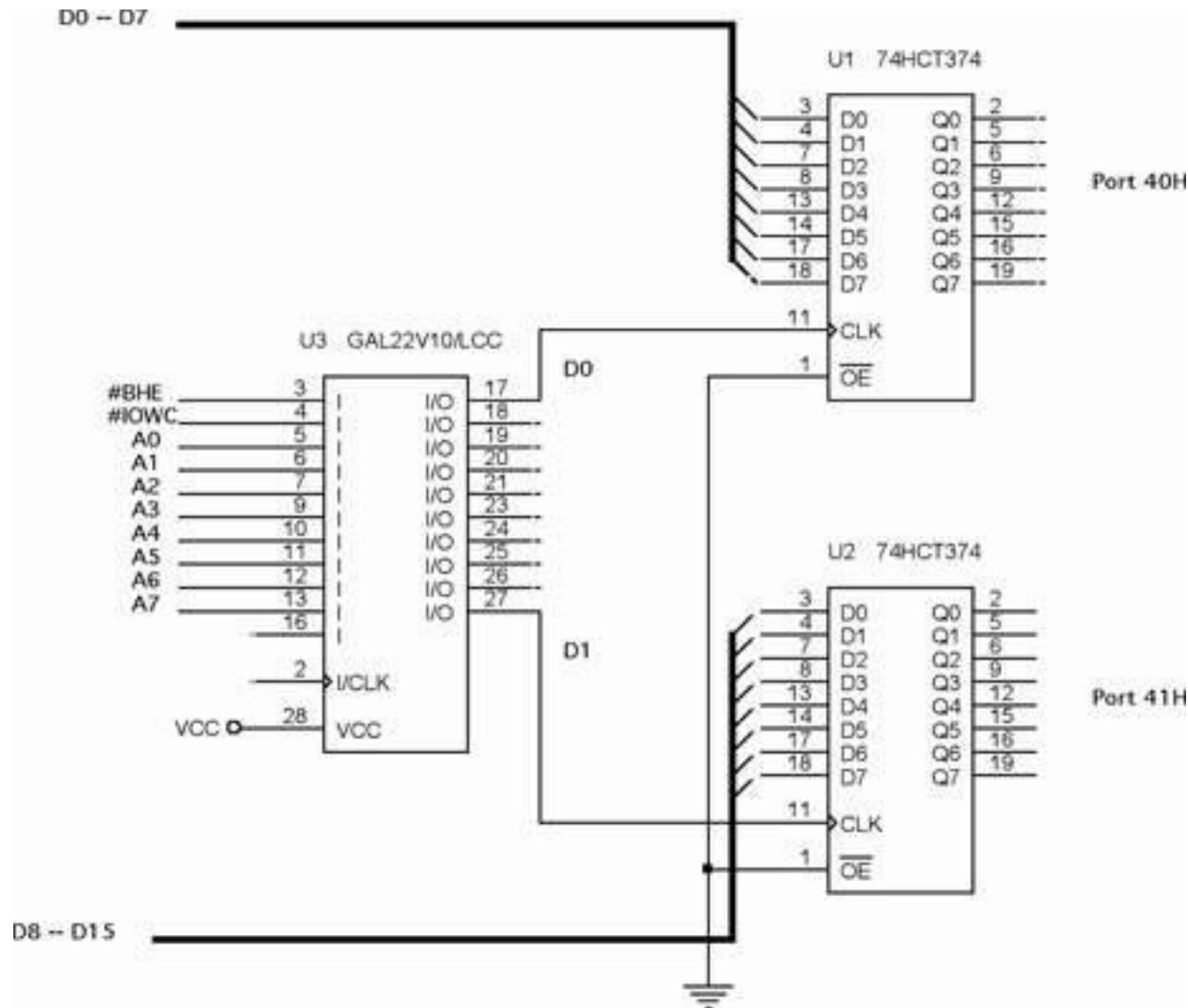

- all I/O ports use 8-bit addresses
- ports 40H & 41H can be addressed as separate 8-bit ports
- or as one 16-bit port

- Fig 11–15 shows a 16-bit device connected to function at 8-bit addresses 64H & 65H.
- The PLD decoder does not have a connection for address bits  $\overline{\text{BLE}}$  ( $A_0$ ) and  $\overline{\text{BHE}}$  because the signals don't apply to 16-bit-wide devices.
- The program for the PLD, illustrated in Example 11–5, shows how the enable signals are generated for the three-state buffers (74HCT244) used as input devices.


**Figure 11–15** A 16-bit-wide port decoded at I/O addresses 64H and 65H.

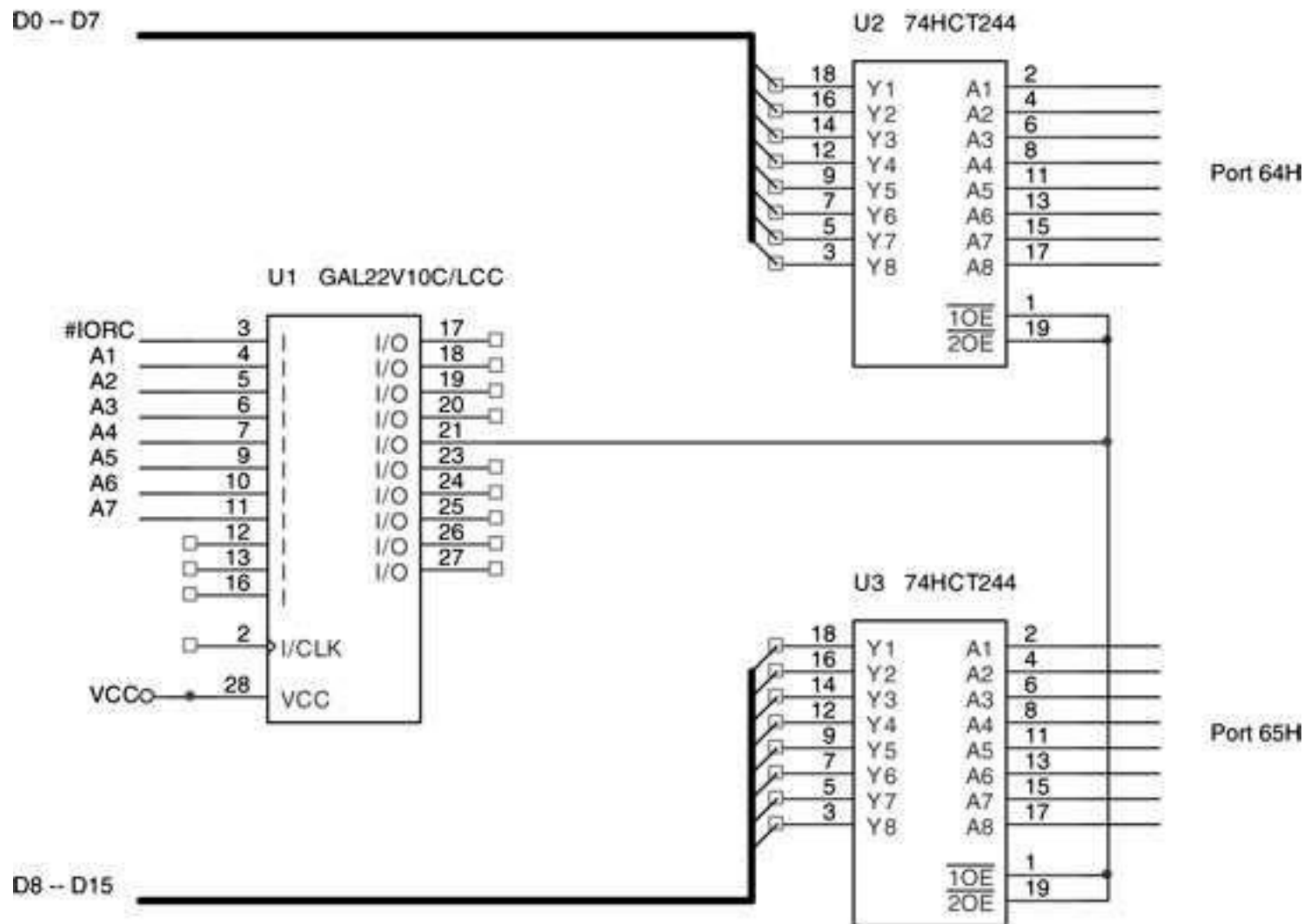

# 32-Bit-Wide I/O Ports

- May eventually become common because of newer buses found in computer systems.
- The EISA system bus supports 32-bit I/O as well as the VESA local and current PCI bus.
  - not many I/O devices are 32 bits in width
- Fig 11–16 shows a 32-bit input port for 80386DX - 80486DX microprocessor.
- The circuit uses a single PLD to decode the I/O ports and four 74HCT244 buffers to connect the I/O data to the data bus.

**Figure 11–16** A 32-bit-wide port decoded at 70H through 73H for the 80486DX microprocessor.

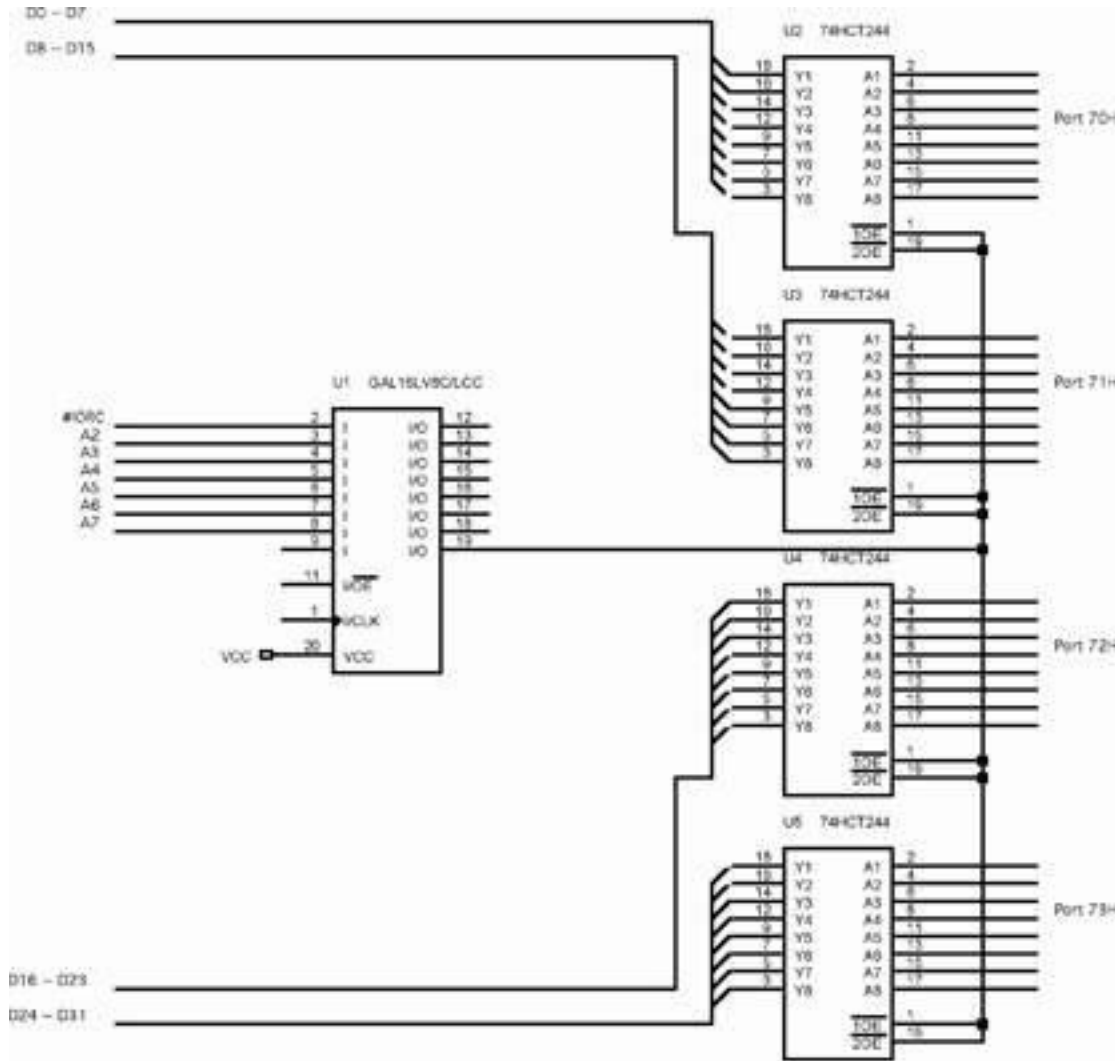


- I/O ports decoded by this interface are the 8-bit ports 70H–73H
- When writing to access this port, it is crucial to use the address 70H for 32-bit input
- as instruction  
IN EAX, 70H

- With the Pentium–Core2 and their 64-bit data buses, I/O ports appear in various banks, as determined by the I/O port address.
- A 32-bit I/O access in the Pentium system can appear in any four consecutive I/O banks.
  - 32-bit ports 0100H–0103H appear in banks 0–3
- I/O address range must begin at a location where the rightmost two bits are zeros.
  - 0100H–0103H is allowable
  - 0101H–0104H is not

- Widest I/O transfers are 32 bits, and there are no I/O instructions to support 64-bit transfers.
  - true for Pentium 4 or Core2 in the 64-bit mode
- Suppose we need to interface a 16-bit-wide output port at I/O address 2000H and 2001H.
  - interface is illustrated in Figure 11–17
  - PLD program is listed in Example 11–7
- The problem that can arise is when the I/O port spans across a 64-bit boundary.
  - example, a 16-bit- port at 2007H and 2008H

**Figure 11–17** A Pentium 4 interfaced to a 16-bit-wide I/O port at port addresses 2000H and 2001H.

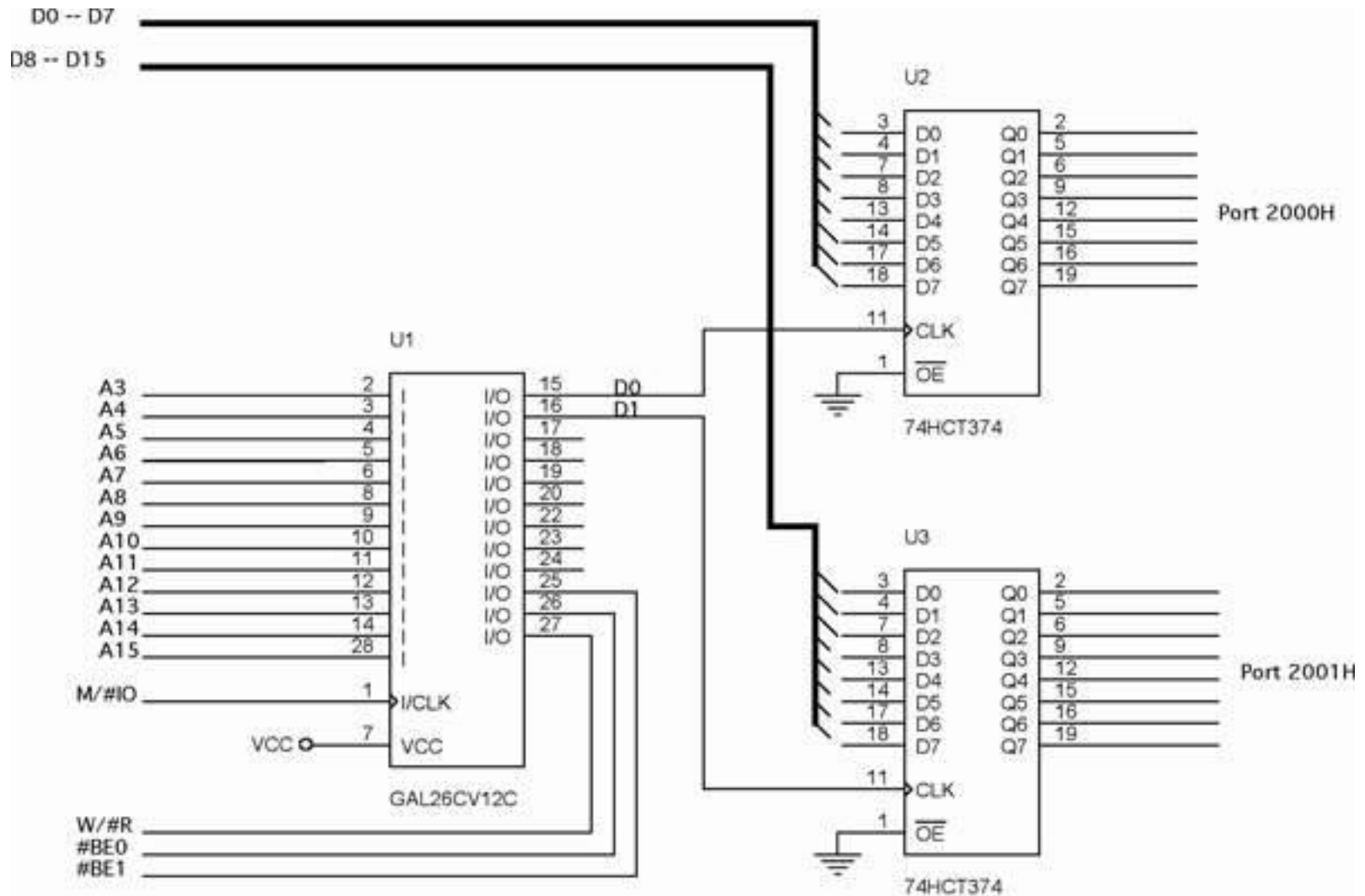



# 11–3 THE PROGRAMMABLE PERIPHERAL

- **82C55 programmable peripheral interface (PPI)** is a popular, low-cost interface component found in many applications.
- The PPI has 24 pins for I/O, programmable in groups of 12 pins and groups that operate in three distinct modes of operation.
- 82C55 can interface any TTL-compatible I/O device to the microprocessor.


- The 82C55 (CMOS version) requires wait states if operated with a processor using higher than an 8 MHz clock.
  - also provides at least 2.5 mA of sink (logic 0) current at each output, a maximum of 4.0 mA
- Because I/O devices are inherently slow, wait states used during I/O transfers do not impact significantly upon the speed of the system.
- The 82C55 still finds application even in the latest Core2-based computer system.

- 82C55 is used for interface to the keyboard and parallel printer port in many PCs.
  - found as a function within an interfacing chip set
  - also controls the timer and reads data from the keyboard interface
- An experimentation board is available that plugs into the parallel port of a PC, to allow access to an 8255 located on the board.
- The 8255 is programmed in either assembly language or Visual C++ through drivers available with the board.

# Basic Description of the 82C55

- Fig 11–18 shows pin-outs of the 82C55 in DIP and surface mount (flat pack) format.
- The three I/O ports (labeled A, B, and C) are programmed as groups.
  - group A connections consist of port A ( $PA_7$ – $PA_0$ ) and the upper half of port C ( $PC_7$ – $PC_4$ )
  - group B consists of port B ( $PB_7$ – $PB_0$ ) and the lower half of port C ( $PC_3$ – $PC_0$ )
- 82C55 is selected by its  $\overline{CS}$  pin for programming and reading/writing to a port.


**Figure 11–18** The pin-out of the 82C55 peripheral interface adapter (PPI).

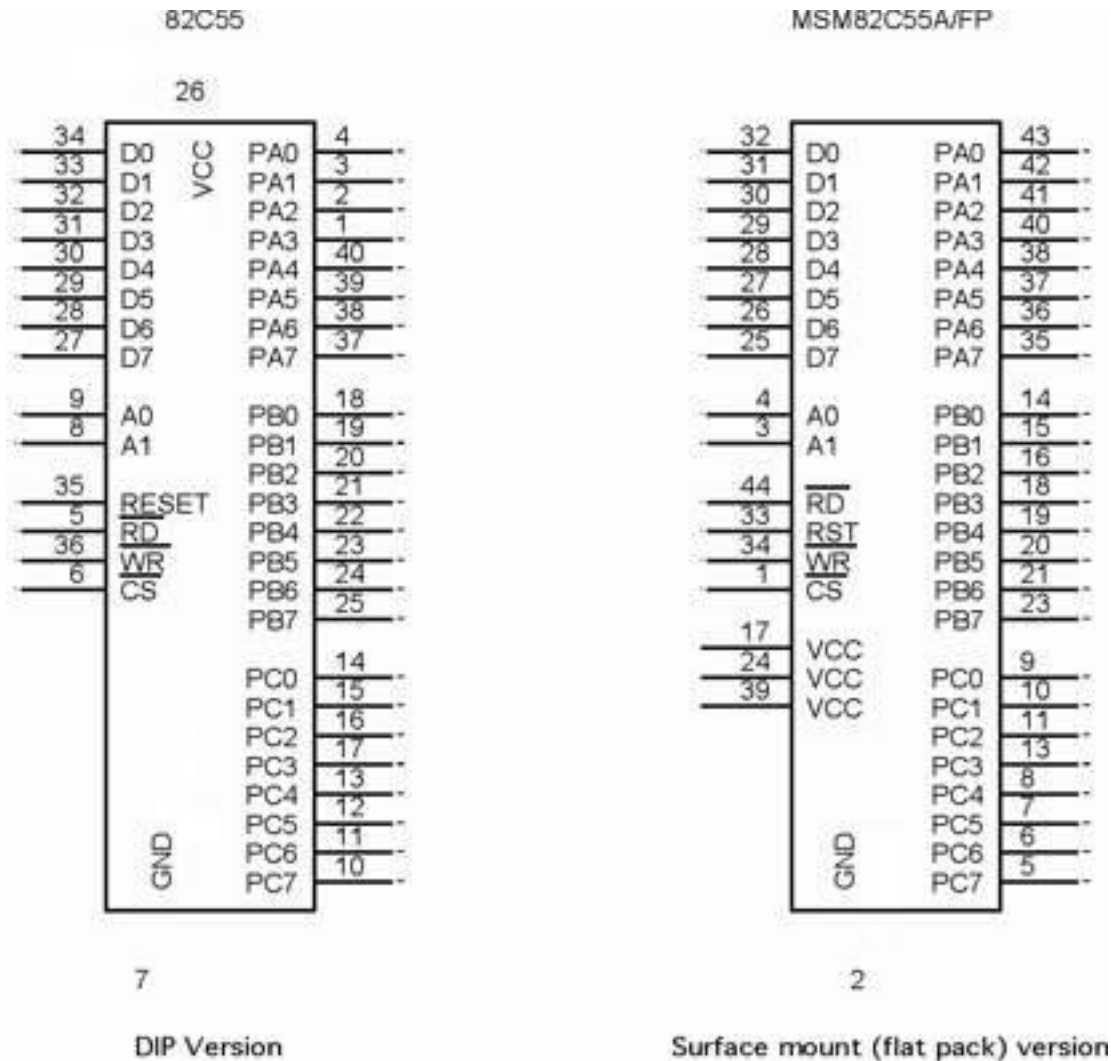

- Table 11–2 shows I/O port assignments used for programming and access to the I/O ports.
- In the PC, a pair of 82C55s, or equivalents, are decoded at I/O ports 60H–63H and also at ports 378H–37BH.
- The 82C55 is a fairly simple device to interface to the microprocessor and program.
- For 82C55 to be read or written, the  $\overline{CS}$  input must be logic 0 and the correct I/O address must be applied to the  $A_1$  and  $A_0$  pins.
- Remaining port address pins are *don't cares*.

- Fig 11–19 shows an 82C55 connected to the 80386SX so it functions at 8-bit addresses C0H (port A), C2H (port B), C4H (port C), and C6H (command register).
  - this interface uses the low bank of the I/O map
- All 82C55 pins are direct connections to the 80386SX, except the  $\overline{CS}$  pin. The pin is decoded/selected by a 74ALS138 decoder.
- A RESET to 82C55 sets up all ports as simple input ports using mode 0 operation.
  - initializes the device when the processor is reset

**Figure 11–19** The 82C55 interfaced to the low bank of the 80386SX microprocessor.

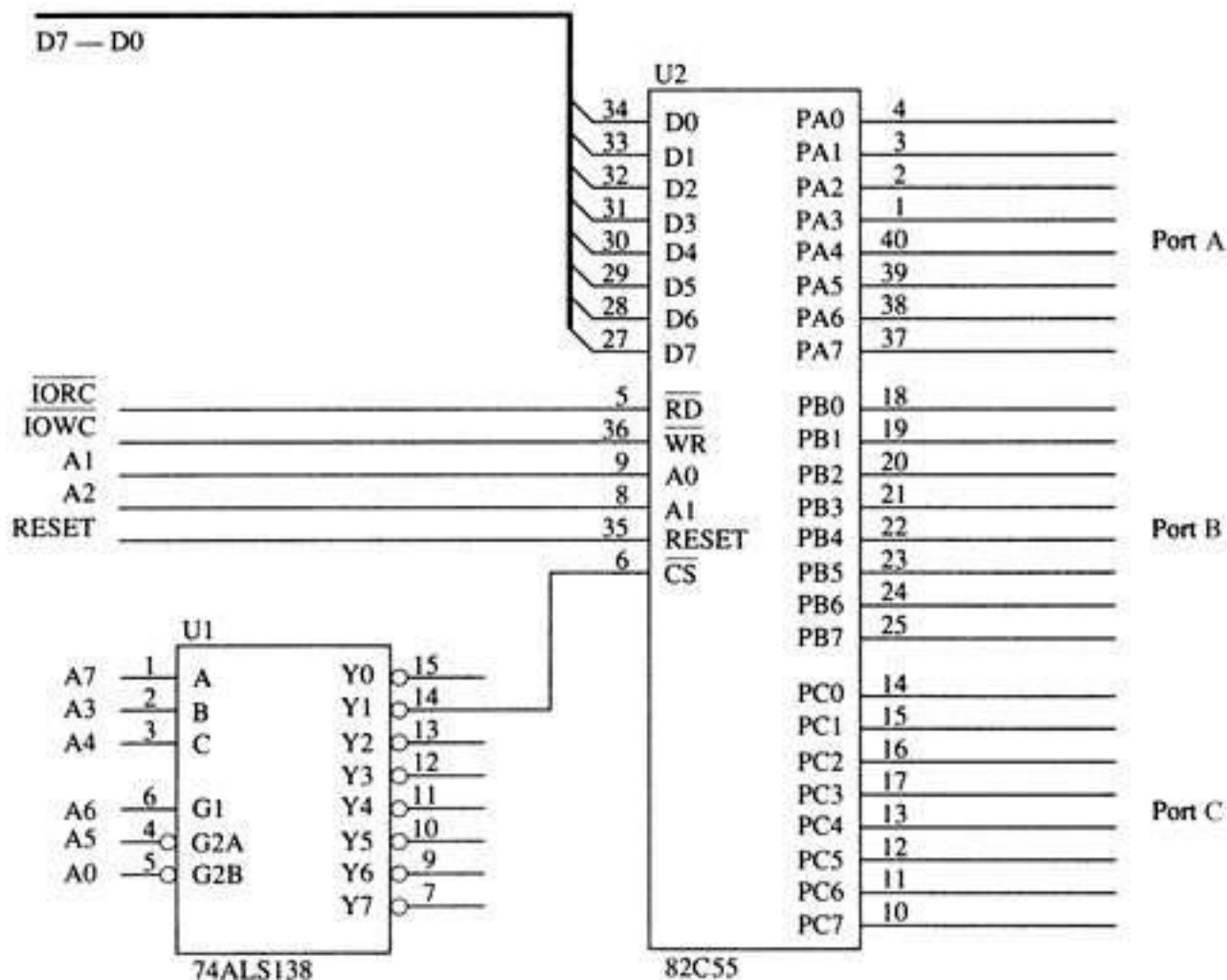




- After a RESET, no other commands are needed, as long as it is used as an input device for all three ports.
- 82C55 is interfaced to the PC at port addresses 60H–63H for keyboard control.
  - also for controlling the speaker, timer, and other internal devices such as memory expansion
- It is also used for the parallel printer port at I/O ports 378H–37BH.

# Programming the 82C55

- 82C55 is programmed through two internal command registers shown in Figure 11–20.
- Bit position 7 selects either command byte A or command byte B.
  - command byte A programs functions of group A and B
  - byte B sets (1) or resets (0) bits of port C only if the 82C55 is programmed in mode 1 or 2
- Group B (port B and the lower part of port C) are programmed as input or output pins.

**Figure 11–20** The command byte of the command register in the 82C55. (a) Programs ports A, B, and C. (b) Sets or resets the bit indicated in the select a bit field.

 


- group B operates in mode 0 or mode 1
- mode 0 is basic input/output mode that allows the pins of group B to be programmed as simple input and latched output connections
- Mode 1 operation is the strobed operation for group B connections
- data are transferred through port B
- handshaking signals are provided by port C

- Group A (port A and the upper part of port C) are programmed as input or output pins.
- Group A can operate in modes 0, 1, and 2.
  - mode 2 operation is a bidirectional mode of operation for port A
- If a 0 is placed in bit position 7 of the command byte, command byte B is selected
- This allows any bit of port C to be set (1) or reset (0), if the 82C55 is operated in either mode 1 or 2.
  - otherwise, this byte is not used for programming

# Mode 0 Operation

- Mode 0 operation causes 82C55 to function:
  - as a buffered input device
  - as a latched output device
- Fig 11–21 shows 82C55 connected to a set of eight seven-segment LED displays.
- These are standard LEDs.
  - the interface can be modified with a change in resistor values for an organic LED (OLED) display or high-brightness LEDs

**Figure 11–21** An 8-digit LED display interfaced to the 8088 microprocessor through an 82C55 PIA.

 

- ports A & B are programmed as (mode 0) simple latched output ports
- port A provides segment data inputs  
port B provides a means of selecting one display position at a time for multiplexing the displays
- the 82C55 is interfaced to an 8088 through a PLD so it functions at I/O port numbers 0700H–0703H
- PLD decodes the I/O address and develops the write strobe for the  $\overline{\text{WR}}$  pin of the 82C55

- Resistor values in Fig 11–21 are chosen so the segment current is 80 mA.
  - required to produce average 10 mA current per segment as the displays are multiplexed
- A six-digit display uses a segment current of 60 mA for an average of 10 mA per segment.
- Peak anode current in an eight-digit display is 560 mA (seven segments  $\times$  80 mA).
  - average anode current is 80 mA
- In a six-digit display, peak current would be 420 mA (seven segments  $\times$  60 mA).


- In this display, the segment load resistor passes 80 mA current and has approximately 3.0 V across it.
- The value of the resistor is  $3.0 \text{ V} \div 180 \text{ mA} = 37.5 \text{ Ohm}$ . The closest standard resistor value of 39 Ohm is used in Fig11–21.
- Programming the 82C55 is accomplished by the short sequence of instructions listed in Example 11–9.
- Ports A and B are programmed as outputs.



# An LCD Display Interfaced to the 82C55

- LCDs (**liquid crystal displays**) have replaced LED displays in many applications.
- Fig 11–22 shows an Optrex DMC-20481 LCD display interfaced to an 82C55.
  - DMC-20481 is a 4-line by 20-characters-per-line display that accepts ASCII code as input data
- It also accepts commands that initialize it and control its application.

**Figure 11–22** The DMC-20481 LCD display interfaced to the 82C55.

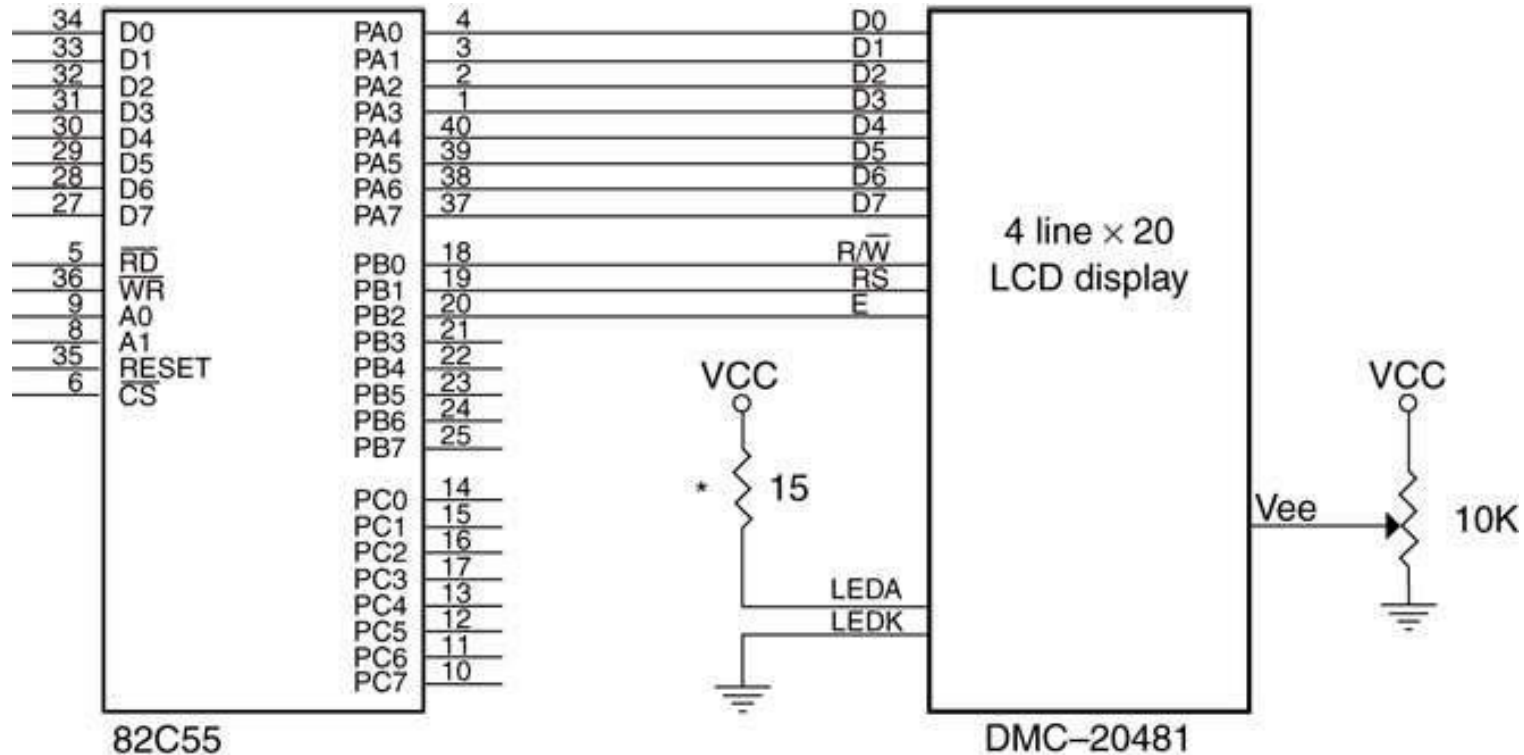

\*Current max is 480 mA, nominal 260 mA.

- The data connections, which are attached to the 82C55 port A, are used to input display data and to read information from the display.
- For a 4-bit interface,  $D_4$ – $D_7$  pins are used where the data must be formatted with the high nibble first, followed by the low nibble.
- A few newer OLED devices contain a serial interface that uses a single pin for the data.

- To program DMC-20481 it must first be initialized.
- This applies to any display using the HD44780 (Hitachi) display driver IC.
- The entire line of small display panels from Optrex and most other manufacturers is programmed in the same manner.
- To program DMC-20481 it must first be initialized.
  - this applies to any display using the HD44780 (Hitachi) display driver integrated circuit

- Initialization is accomplished via the following:
  - 1. Wait at least 15 ms after  $V_{CC}$  rises to 5.0 V
  - 2. Output the function set command (30H), and wait at least 4.1 ms
  - 3. Output the function set command (30H) a second time, and wait at least 100  $\mu s$
  - 4. Output the function set command (30H) a third time, and wait at least 40  $\mu s$
  - 5. Output the function set command (38H) a fourth time, and wait at least 40  $\mu s$
  - 6. Output 08H to disable the display, and wait at least 40  $\mu s$

- 7. Output a 01H to home the cursor and clear the display, and wait at least 1.64 ms
- 8. Output the enable display cursor off (0CH), and wait at least 40  $\mu$ s
- 9. Output 06H to select auto-increment, shift the cursor, and wait at least 40  $\mu$ s
- Software to accomplish the initialization of the LCD display is listed in Example 11–12.
- The time delays can also be obtained by using a timer in C++.

- After initialization, time delays are no longer needed when sending data or many commands to the display.
- The clear display command still needs a time delay as the busy flag is not used .
- Instead of a time delay, the busy flag is tested to see whether the display has completed an operation.
- The BUSY procedure tests the LCD display and only returns when the display has completed a prior instruction.

- Once the BUSY procedure is available, data can be sent to the display by writing another procedure called WRITE.
- The WRITE procedure uses BUSY to test before trying to write new data to the display.
- Example 11–14 shows the WRITE procedure, which transfers the ASCII character from the BL register to the current cursor position of the display.




- The only other procedure needed for a basic display is the clear & home cursor procedure, called CLS, shown in Example 11–15.
- This procedure uses the SEND macro from the initialization software to send the clear command to the display.
- With CLS and the procedures presented thus far, you can display any message on the display, clear it, display another message, and basically operate the display.

# ***A Stepper Motor Interfaced to the 82C55.***

- Another device often interfaced to a computer system is the **stepper motor**.
  - a digital motor because it is moved in discrete steps as it traverses through  $360^\circ$
- An inexpensive stepper motor is geared to move perhaps  $15^\circ$  per step
- A more costly, high-precision stepper motor can be geared to  $1^\circ$  per step.


- In all cases, these steps are gained through many magnetic poles and/or gearing.
- Figure 11–23 shows a four-coil stepper motor that uses an armature with a single pole.
  - two coils are energized
- If less power is required, one coil may be energized at a time, causing the motor to step at  $45^\circ$  ,  $135^\circ$  ,  $225^\circ$  , and  $315^\circ$  .
- The motor is shown with the armature rotated to four discrete places, called full stepping.
  - accomplished by energizing the coils, as shown

**Figure 11–23** The stepper motor showing full-step operation: (a)  $45^\circ$  (b)  $135^\circ$  (c)  $225^\circ$  (d)  $315^\circ$  .

 

- The motor is driven by NPN Darlington amp pairs to provide a large current to each coil.
- A circuit that can drive this stepper motor is illustrated in Fig 11–24.
  - with the four coils shown in place
- This circuit uses the 82C55 to provide drive signals used to rotate the motor armature in either the right- or left-hand direction.
- A simple procedure that drives the motor is listed in Example 11–16 in both assembly language and as a function in C++.

**Figure 11–24** A stepper motor interfaced to the 82C55. This illustration does not show the decoder.

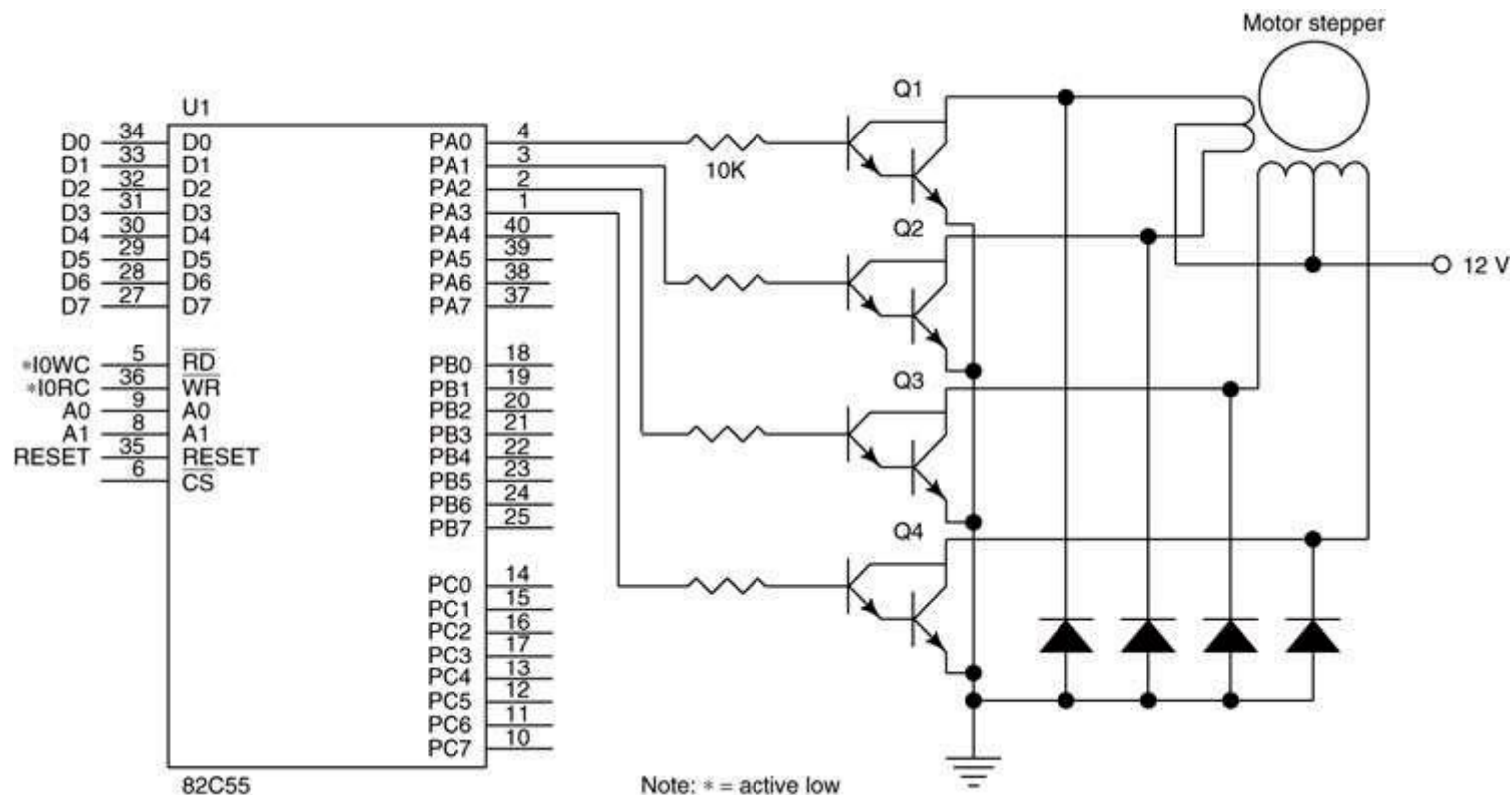


# ***Key Matrix Interface***

- Keyboards come in a variety of sizes, from standard 101-key QWERTY keyboards to special keyboards that contain 4 to 16 keys.
- Fig 11–25 is a key matrix with 16 switches interfaced to ports A and B of an 82C55.
  - the switches are formed into a  $4 \times 4$  matrix, but any matrix could be used, such as a  $2 \times 8$
- The keys are organized into four rows and columns: ( $ROW_0$ – $ROW_3$ ) ( $COL_0$ – $COL_3$ )


**Figure 11–25** A  $4 \times 4$  keyboard matrix connected to an 8088 microprocessor through the 82C55 PIA.

- the 82C55 is decoded at I/O ports 50H–53H for an 8088
- port A is programmed as an input port to read the rows
- port B is programmed as an output port to select a column
- a flowchart of the software required to read a key from the keyboard matrix and debounce the key is illustrated in Fig 11–26

 



**Figure 11–26** The flowchart of a keyboard-scanning procedure.

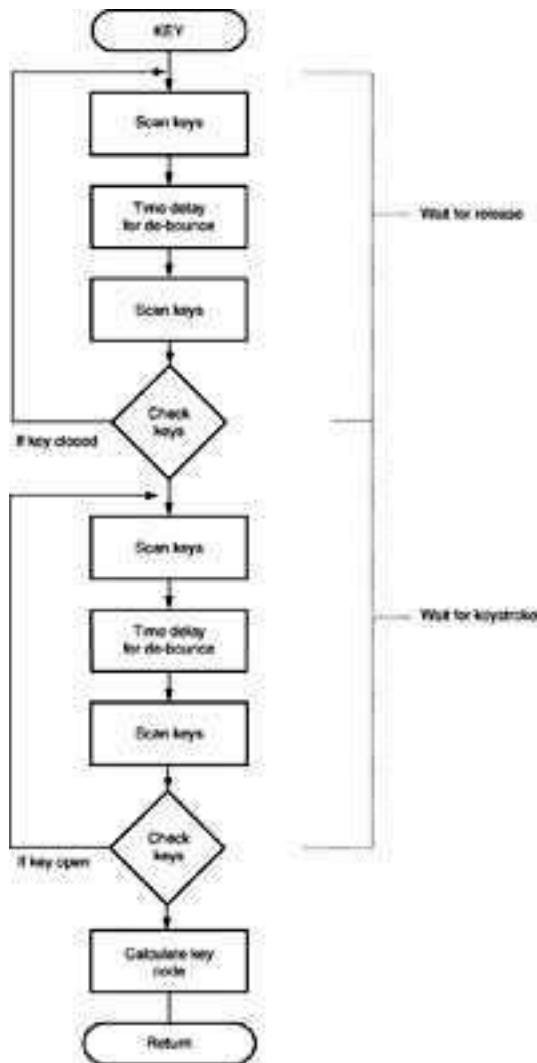


- keys must be debounced, normally with a time delay of 10–20 ms
- the software uses a procedure called SCAN to scan the keys and another called DELAY10 to waste 10 ms of time for debouncing
- the main keyboard procedure is called KEY and appears in Example 11–17
- the KEY procedure is generic, and can handle any configuration from a  $1 \times 1$  matrix to an  $8 \times 8$  matrix.

- The ShortDelay procedure is needed as the computer changes port B at a very high rate .
  - the time delay allows the data sent to port B to settle to their final state
- This is not needed if scan rate (time between output instructions) does not exceed 30 KHz.
  - if the scanning frequency is higher, the device generates radio interference
- If so, the FCC will not approve application in any accepted system
  - without certification the system cannot be sold

# Mode 1 Strobed Input

- Causes port A and/or port B to function as latching input devices.
  - allows external data to be stored to the port until the microprocessor is ready to retrieve it
- Port C is used in mode 1 operation—not for data, but for control or handshaking signals.
  - to help operate either or both port A and B as strobed input ports
- Fig 11–27 shows how both ports are structured for mode 1 strobed input operation.

**Figure 11–27** Strobed input operation (mode 1) of the 82C55. (a) Internal structure and (b) timing diagram.

 

# Signal Definitions for Mode 1

## Strobed Input

---

### STB

- The **strobe** input loads data to the port latch, which holds the information until it is input to the microprocessor via the IN instruction.

### IBF

- **Input buffer full** is an output indicating that the input latch contains information.

# INTR

- **Interrupt request** is an output that requests an interrupt. The INTR pin becomes a logic 1 when  $\overline{STB}$  returns to a logic 1. Cleared when data are input from the port by the processor.

# INTE

- **Interrupt enable signal** is neither input nor output; it is an internal bit programmed via port  $PC_4$  (port A) or  $PC_2$  (port B) bit position.

# PC<sub>7</sub>, PC<sub>6</sub>


- The port C pins 7 and 6 are general-purpose I/O pins that are available for any purpose.

# ***Strobed Input Example***

- An example of a strobed input device is a keyboard.
- The keyboard encoder debounces the key switches and provides a strobe signal whenever a key is depressed.
  - the data output contains ASCII-coded key code
- Figure 11–28 illustrates a keyboard connected to strobed input port A.




**Figure 11–28** Using the 82C55 for strobed input operation of a keyboard.

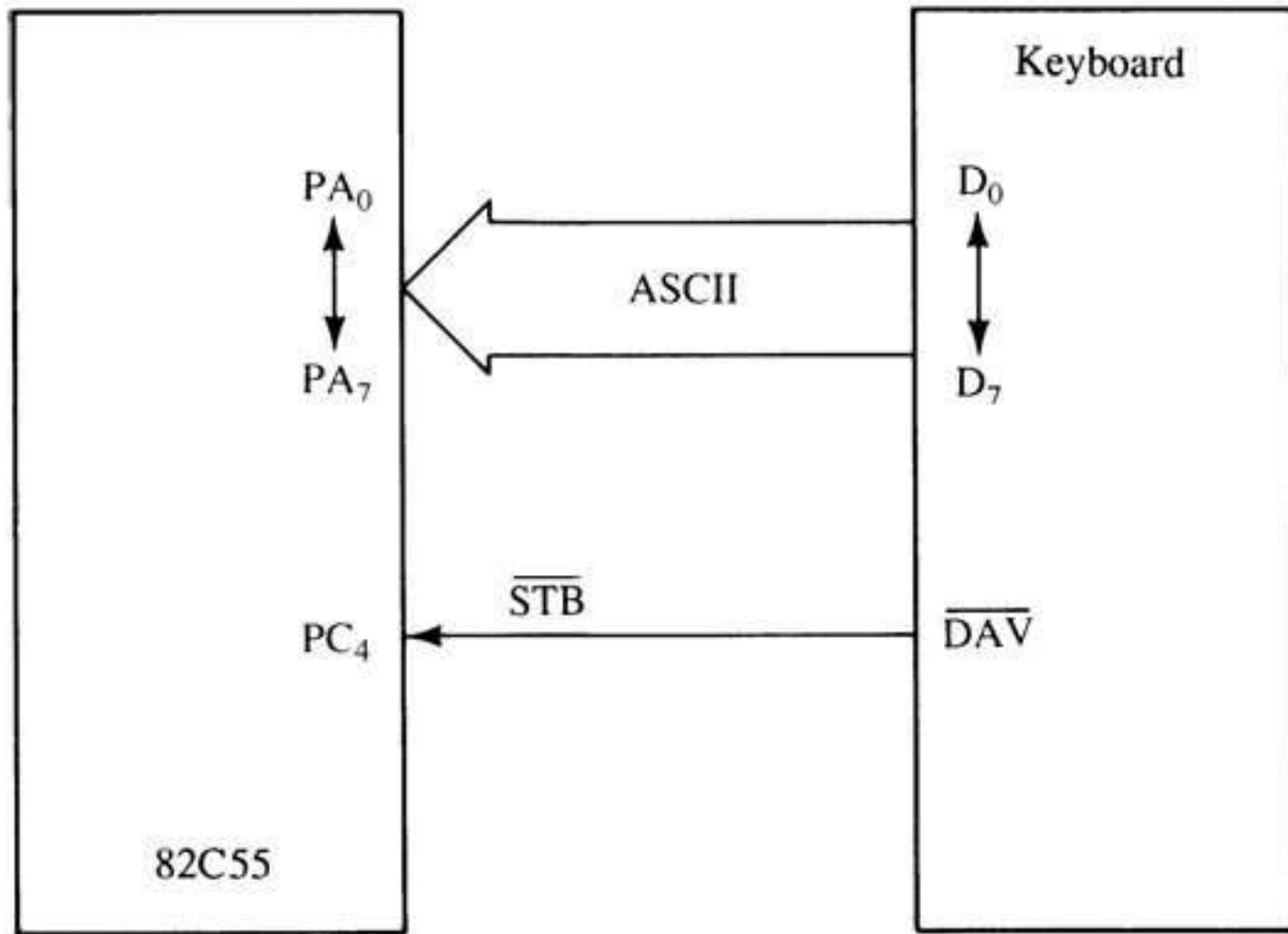

# Mode 1 Strobed Output

- Fig 11–29 shows the internal configuration and timing diagram of 82C55 when operated as a strobed output device under mode 1.
- Strobed output operation is similar to mode 0 output operation.
  - except control signals are included to provide handshaking
- When data are written to a strobed output port, the **output buffer full** signal becomes logic 0 to indicate data are present in the port latch.

**Figure 11–29** Strobed output operation (mode 1) of the 82C55. (a) Internal structure and (b) timing diagram.

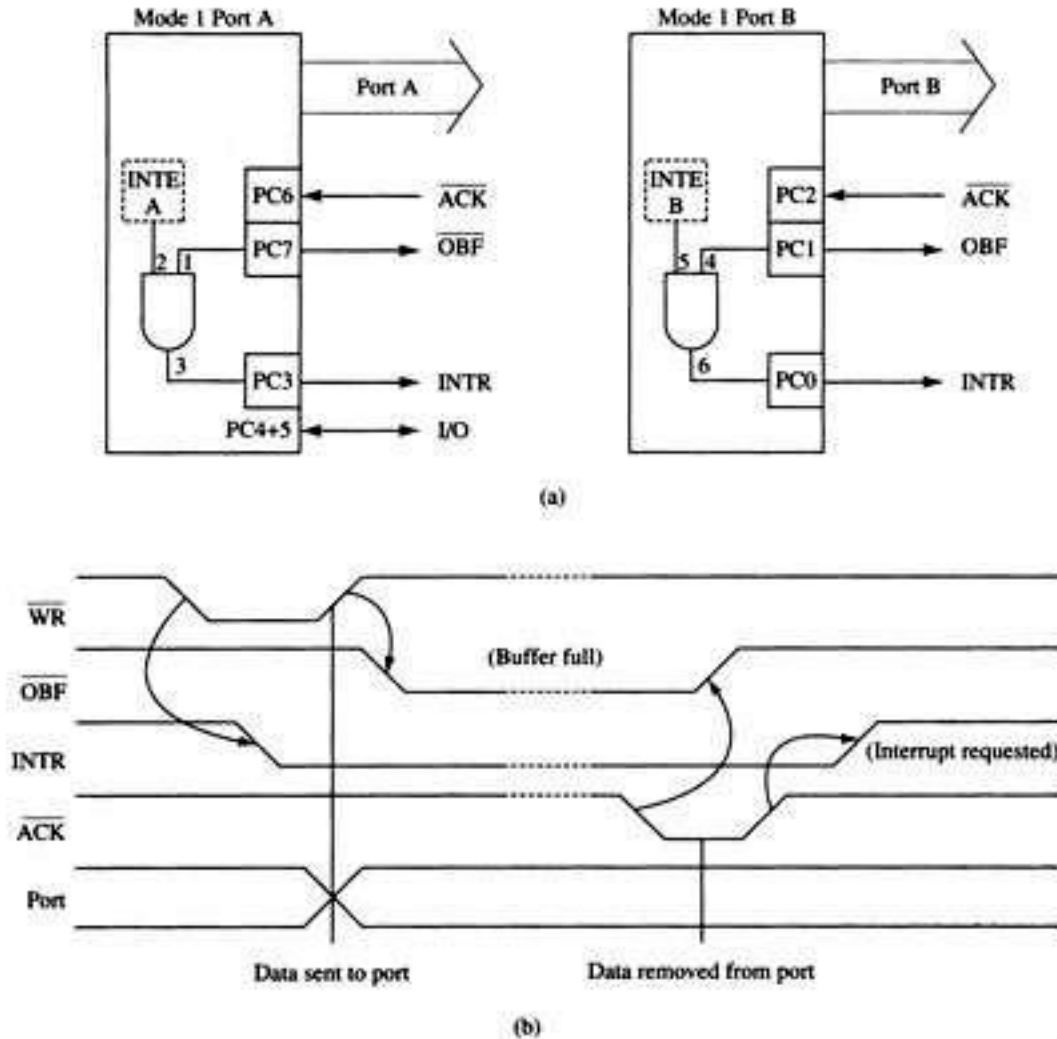

# Signal Definitions for Mode 1

## Strobed Output

### OBF

- **Output buffer full** goes low whenever data are output (OUT) to the port A or B latch. The signal is set to logic 1 when the ACK pulse returns from the external device.

# ACK

- The **acknowledge signal** causes the OBF pin to return to logic 1. The ACK signal is a response from an external device, indicating that it has received data from the 82C55 port.

# INTR

- **Interrupt request** often interrupts the processor when the external device receives the data via the ACK signal. Qualified by the internal INTE (**interrupt enable**) bit.

# INTE

- **Interrupt enable** is neither input nor output; it is an internal bit programmed to enable or disable the INTR pin. INTE A is programmed using  $PC_6$  bit. INTE B is programmed using the  $PC_2$  bit.


## $PC_4$ , $PC_5$

- Port C pins  $PC_4$  and  $PC_5$  are general-purpose I/O pins. The bit set and reset command is used to set or reset these two pins.

# ***Strobed Output Example***

- The printer interface demonstrates how to achieve strobed output synchronization between the printer and the 82C55.
- Figure 11–30 illustrates port B connected to a parallel printer, with eight data inputs for receiving ASCII-coded data, a  $\overline{DS}$  (**data strobe**) input to strobe data into the printer, and an ACK output to acknowledge the receipt of the ASCII character.

**Figure 11–30** The 82C55 connected to a parallel printer interface that illustrates the strobed output mode of operation for the 82C55.

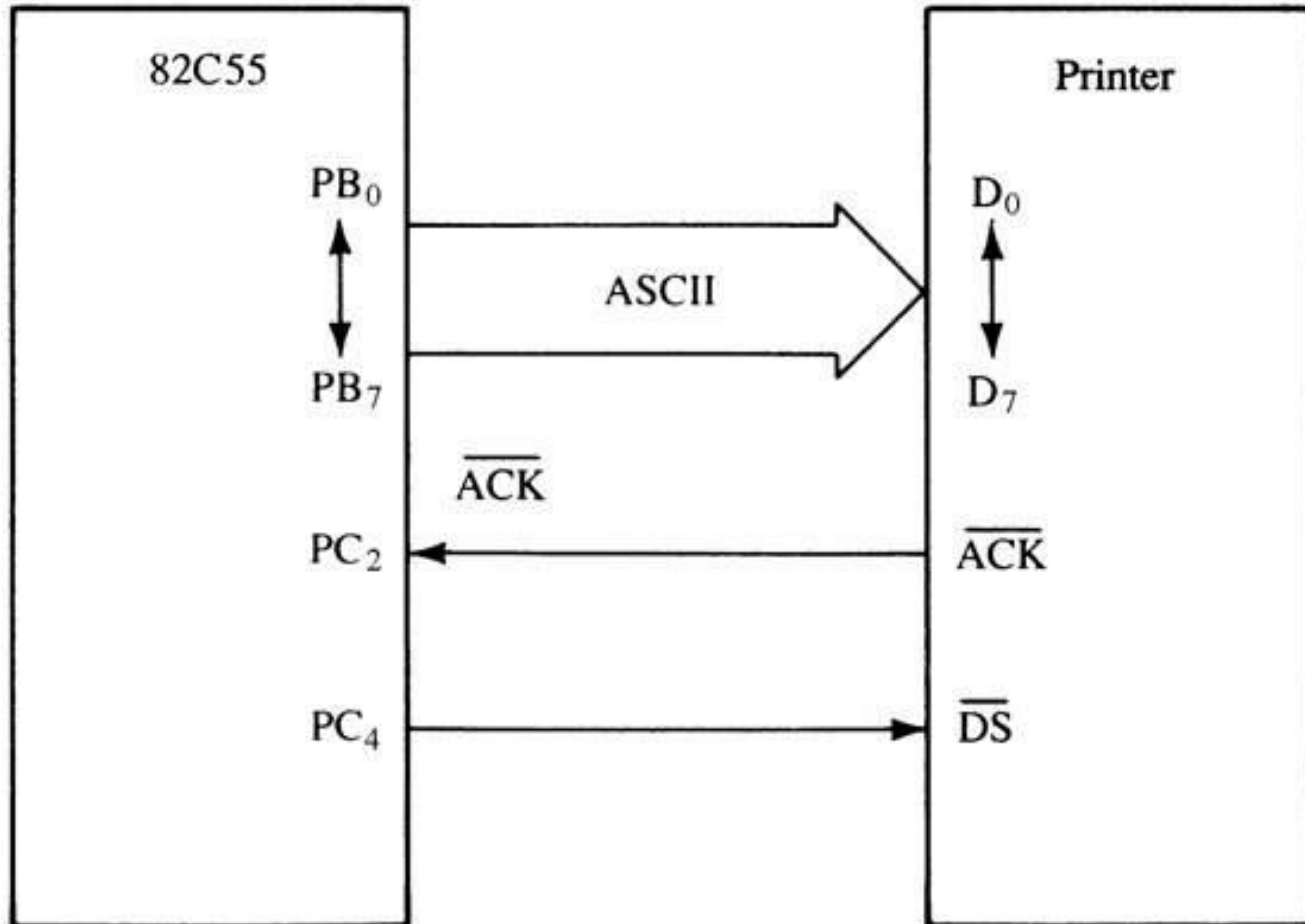




# Mode 2 Bidirectional Operation

- Mode 2 is allowed with group A only.
- Port A becomes bidirectional, allowing data transmit/receive over the same eight wires.
  - useful when interfacing two computers
- Also used for IEEE-488 parallel high-speed GPIB (**general- purpose instrumentation bus**) interface standard.
- Figure 11–31 shows internal structure and timing for mode 2 bidirectional operation.

**Figure 11–31** Mode 2 operation of the 82C55. (a) Internal structure and (b) timing diagram.

 

# Signal Definitions for Bidirectional Mode 2

## INTR

- **Interrupt request** is an output used to interrupt the microprocessor for input and output conditions.

---

## OBF

- **Output buffer full** is an output indicating the output buffer contains data for the bidirectional bus.

# ACK

- **Acknowledge** is an input that enables the three-state buffers so that data can appear on port A. If ACK is logic 1, the output buffers of port A are at their high-impedance state.

# STB

- The **strobe** input loads the port A input latch with external data from the bidirectional port A bus.

# $PC_0$ , $PC_1$ , and $PC_2$

- These pins are general-purpose I/O pins in mode 2 controlled by the bit set and reset command.

# IBF

- **Input buffer full** is an output used to signal that the input buffer contains data for the external bidirectional bus.

# INTE

- **Interrupt enable** are internal bits (INTE1 & INTE2) that enable the INTR pin. The state of the INTR pin is controlled through port C bits  $PC_6$  (INTE1) and  $PC_4$  (INTE2).

# ***The Bidirectional Bus***

- The bidirectional bus is used by referencing port A with the IN and OUT instructions.
- To transmit data through the bidirectional bus, the program first tests to determine whether the output buffer is empty.
  - if so, data are sent to the output buffer via OUT
- The external circuitry also monitors the signal to decide whether the microprocessor has sent data to the bus.

- To receive data through the bidirectional port A bus, IBF is tested with software to decide whether data have been strobed into the port.
  - if IBF = 1, data is input using IN
- The external interface sends data to the port by using the STB signal.
  - the IBF signal becomes logic 1 and data at port A are held inside the port in a latch
- When the IN executes, the IBF bit is cleared and data in the port are moved into AL.
- See Example 11–21 for a procedure.



- The INTR (**interrupt request**) pin can be activated from both directions of data flow through the bus.
- If INTR is enabled by both INTE bits, the output and input buffers both cause interrupt requests.
- This occurs when data are strobed into the buffer using STB or when data are written using OUT.

# 82C55 Mode Summary

- Figure 11–32 shows a graphical summary of the three modes of operation for the 82C55.
- Mode 0 provides simple I/O.
- Mode 1 provides strobed I/O.
- Mode 2 provides bidirectional I/O.
- These modes are selected through the command register of the 82C55.

**Figure 11–32** A summary of the port connections for the 82C55 PIA.

		Mode 0		Mode 1		Mode 2
Port A		IN	OUT	IN	OUT	I/O
Port B		IN	OUT	IN	OUT	Not used
Port C	0	IN	OUT	$\text{INTR}_B$	$\text{INTR}_B$	I/O
	1			$\text{IBF}_B$	$\overline{\text{OBF}}_B$	I/O
	2			$\overline{\text{STB}}_B$	$\overline{\text{ACK}}_B$	I/O
	3			$\text{INTR}_A$	$\text{INTR}_A$	INTR
	4			$\overline{\text{STB}}_A$	I/O	$\overline{\text{STB}}$
	5			$\text{IBF}_A$	I/O	IBF
	6			I/O	$\overline{\text{ACK}}_A$	$\overline{\text{ACK}}$
	7			I/O	$\overline{\text{OBF}}_A$	$\overline{\text{OBF}}$

# The Serial EEPROM Interface


- In Chapter 10, Figure 10–23, a serial EEPROM is illustrated, but at that point in the text, no I/O existed for an interface.
- Suppose that port C of an 82C55 is used for connection to this interface and software is needed to drive the interface.
- The  $PC_0$  pin is programmed as an output to send data and as an input to receive data from the EEPROM.

### Chapter 10, Figure 10–23 A serial EEPROM interface.

J. M. PACKAGES			
1	1-4	1	CB4
2	5-8	2	1
3	9-11	3	CB4
4	12-15	4	CB4
5	16-18	5	CB4
6	19-21	6	CB4
7	22-24	7	CB4
8	25-27	8	CB4
9	28-30	9	CB4
10	31-33	10	CB4
11	34-36	11	CB4
12	37-39	12	CB4
13	40-42	13	CB4
14	43-45	14	CB4
15	46-48	15	CB4
16	49-51	16	CB4
17	52-54	17	CB4
18	55-57	18	CB4
19	58-60	19	CB4
20	61-63	20	CB4

144

functional block diagram

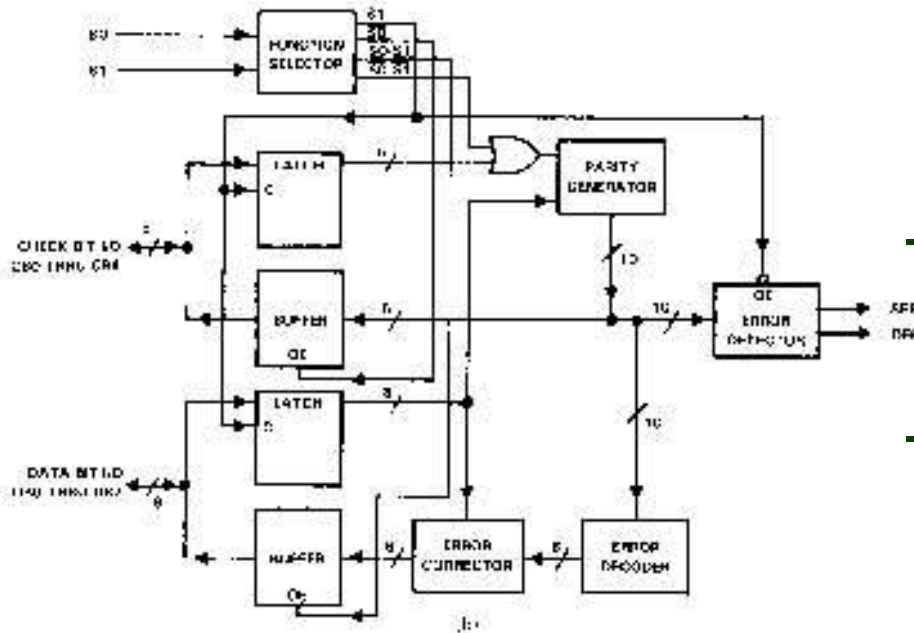


- this memory interface has two signal lines
- one is a serial clock (SCL); the other a bidirectional serial data line (SDA)
- not meant to replace system main memory
- it is fast enough for music or other low-speed data

- Refer to Figure 10–24.
- The data format for the software for reading and writing data to the EEPROM is also illustrated in Example 11–22.
- This software is written in C with some assembly language, but it can also be developed in assembly language.
- I/O port address for the command register is 0x1203, and 0x1202 for the port C register.
  - the time delay should be 1.25  $\mu$ s for a data rate of 400 KHz

**Chapter 10, Figure 10–24** Data signals to the serial EEPROM for a read or a write.

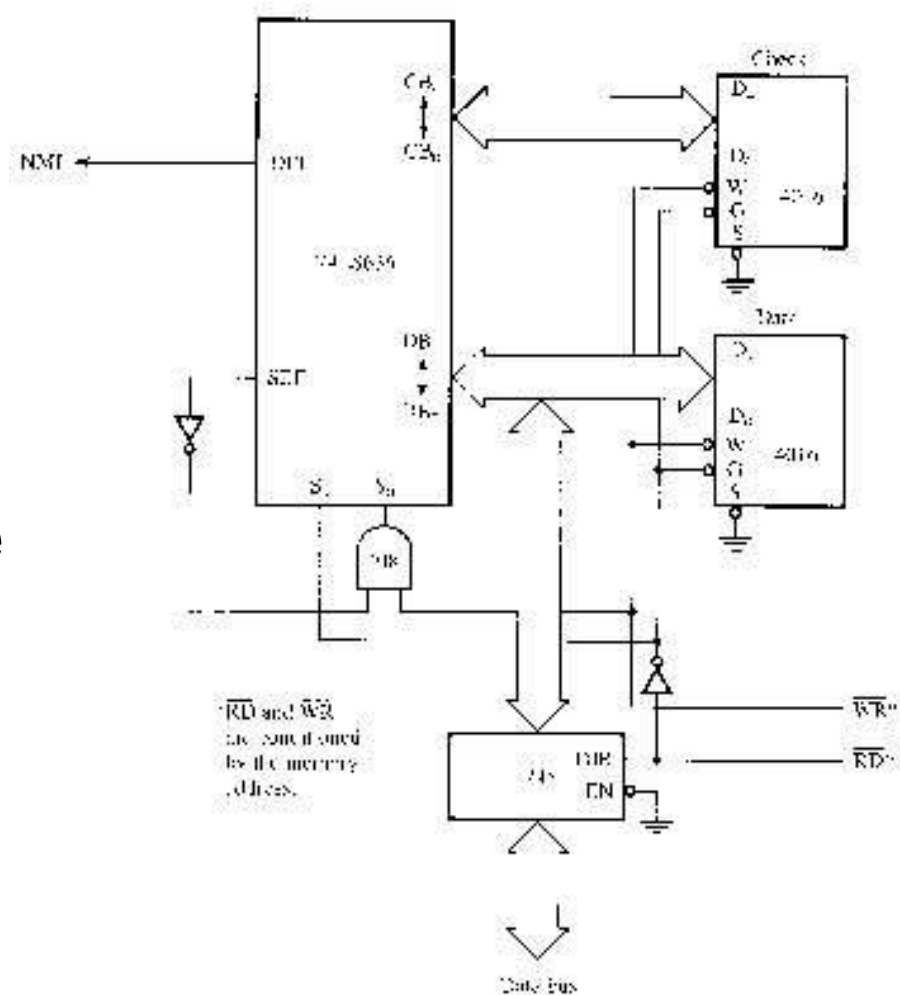- the serial data contains the address in the first byte as well as a device code of 1010, which represents the EEPROM
- other serial devices have different device codes
- this is followed by the memory location and the data in additional bytes



# 11–4 8254 PROGRAMMABLE INTERVAL TIMER

- The 8254 consists of three independent 16-bit programmable counters (**timers**).
- Each counter is capable of counting in binary or binary-coded decimal (BCD).
  - maximum allowable input frequency to any counter is 10 MHz
- Useful where the microprocessor must control real-time events.




- Usage includes real-time clocks, event counters, and motor speed/direction control.
- Timer appears in the PC decoded at ports 40H–43H to do the following:
  - 1. Generate a basic timer interrupt that occurs at approximately 18.2 Hz
  - 2. Cause the DRAM memory system to be refreshed
  - 3. Provide a timing source to the internal speaker and other devices.
- Timer in the PC is an 8253 instead of 8254.


# 8254 Functional Description

- Figure 11–33 shows the pin-out of the 8254, a higher-speed version of the 8253, and a diagram of one of the three counters.
- Each timer contains:
  - a CLK input which provides the basic operating frequency to the timer
  - a gate input pin which controls the timer in some modes
  - an output (OUT) connection to obtain the output of the timer

**Figure 11–33** The 8254 programmable interval timer. (a) Internal structure and (b) pin-out. (Courtesy of Intel Corporation.)

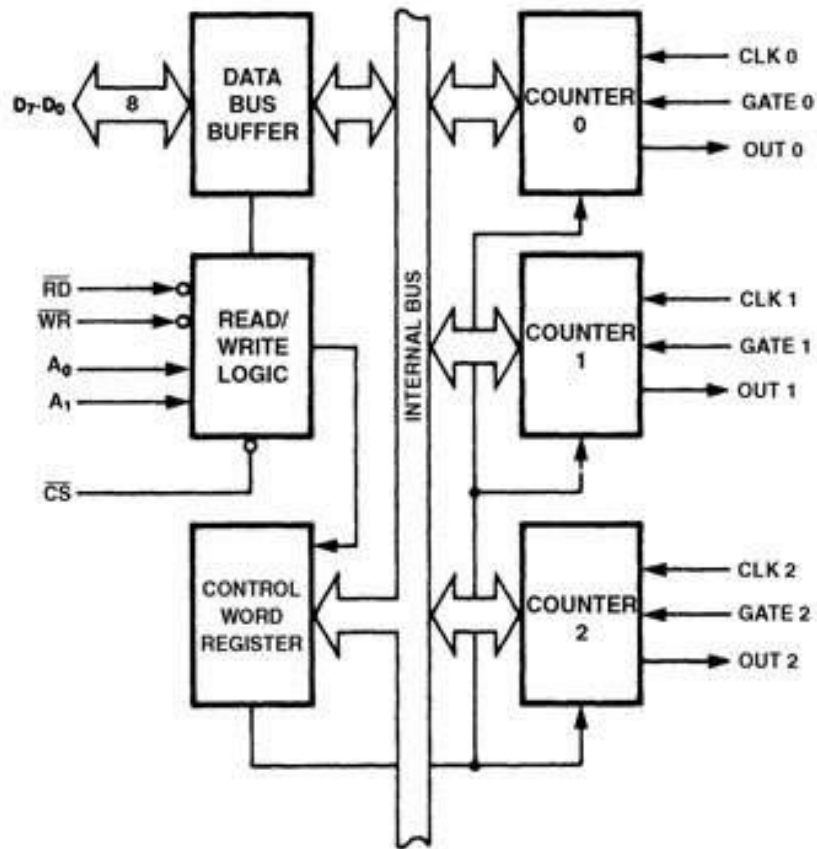

(a)

 

(b)

- The signals that connect to the processor are the data bus pins ( $D_7$ – $D_0$ ),  $\overline{RD}$ ,  $\overline{WR}$ ,  $\overline{CS}$ , and address inputs  $A_1$  and  $A_0$ .
- Address inputs are present to select any of the four internal registers.
  - used for programming, reading, or writing to a counter

- Timer zero generates an 18.2 Hz signal that interrupts the microprocessor at interrupt vector 8 for a clock tick.
  - often used to time programs and events in DOS
- Timer 1 is programmed for  $15\ \mu\text{s}$ , used on the PC to request a DMA action used to refresh the dynamic RAM.
- Timer 2 is programmed to generate a tone on the PC speaker.

# Pin Definitions for 8254

## $A_0$ , $A_1$

- The **address inputs** select one of four internal registers within the 8254. See Table 11–4 for the function of the  $A_1$  and  $A_0$  address bits.

## CLK

- The **clock** input is the timing source for each of the internal counters. This input is often connected to the PCLK signal from the microprocessor system bus controller.

# CS

- **Chip select** enables 8254 for programming and reading or writing a counter.

# G

- The **gate input** controls the operation of the counter in some modes of operation

# GND

- **Ground** connects to the system ground bus.

# OUT

- A **counter output** is where the waveform generated by the timer is available.

# $\overline{RD}$

- **Read** causes data to be read from the 8254 and often connects to the  $\overline{IORC}$  signal.

# Vcc

- **Power** connects to the +5.0 V power supply.




# WR

- **Write** causes data to be written to the 8254 and often connects to write strobe IOWC.

# Programming the 8254

- Each counter is programmed by writing a control word, followed by the initial count.
  - fig 11–34 lists the program control word structure
- The control word allows the programmer to select the counter, mode of operation, and type of operation (read/write).
  - also selects either a binary or BCD count


**Figure 11–34** The control word for the 8254-2 timer.

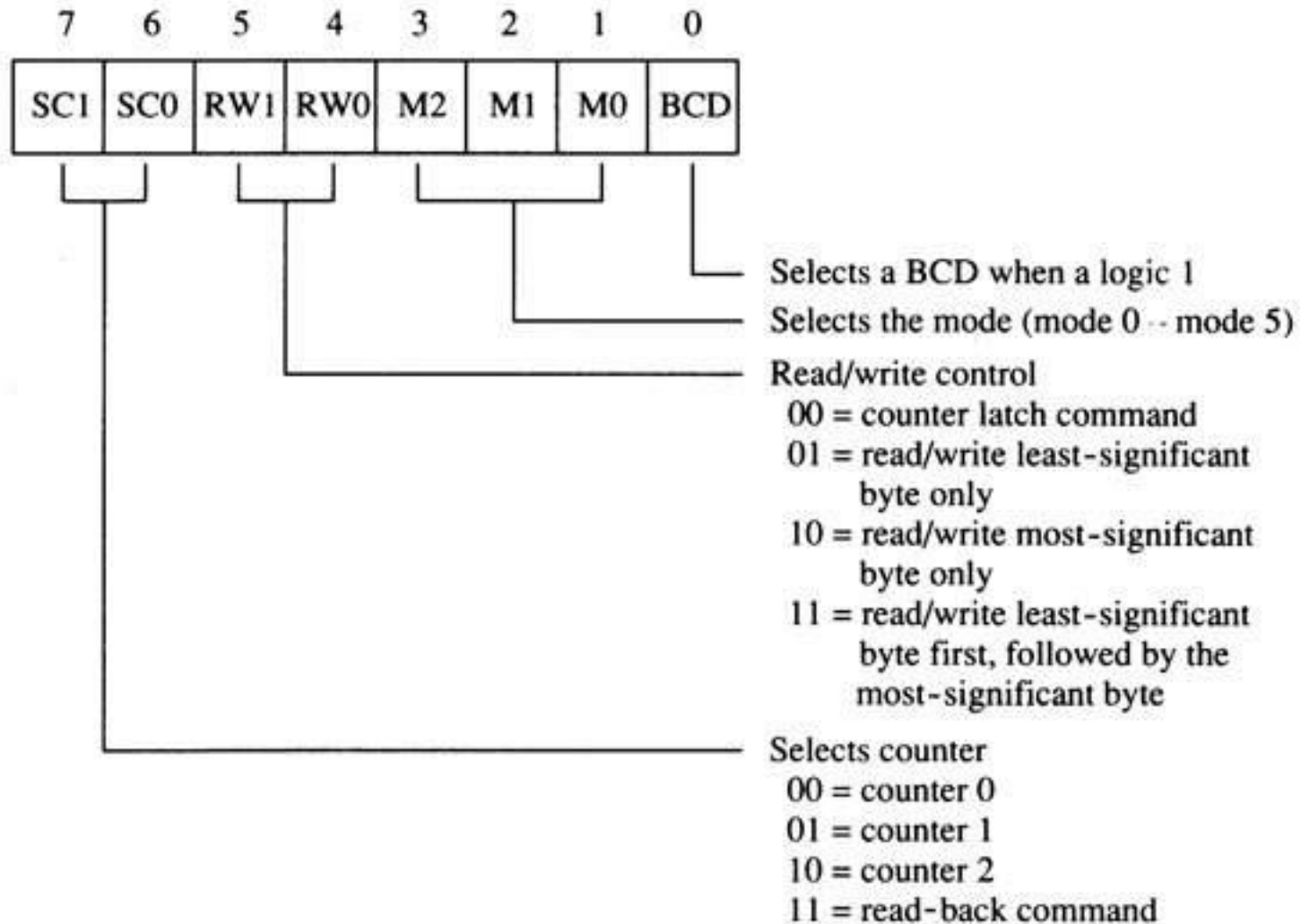

- Each counter may be programmed with a count of 1 to FFFFH; A count of 0 is equal to FFFFH+1 (65,536) or 10,000 in BCD.
- Timer 0 is used in the PC with a divide-by count of 64K (FFFFH) to generate the 18.2 Hz (18.196 Hz) interrupt clock tick.
  - timer 0 has a clock input frequency of 4.77 MHz + 4 or 1.1925 MHz
- The order of programming is important for each counter, but programming of different counters may be interleaved for better control.

# Modes of Operation

- six modes (0–5) of available to each of the 8254 counters
- each mode functions with the CLK input, the gate (G) control signal, and OUT signal

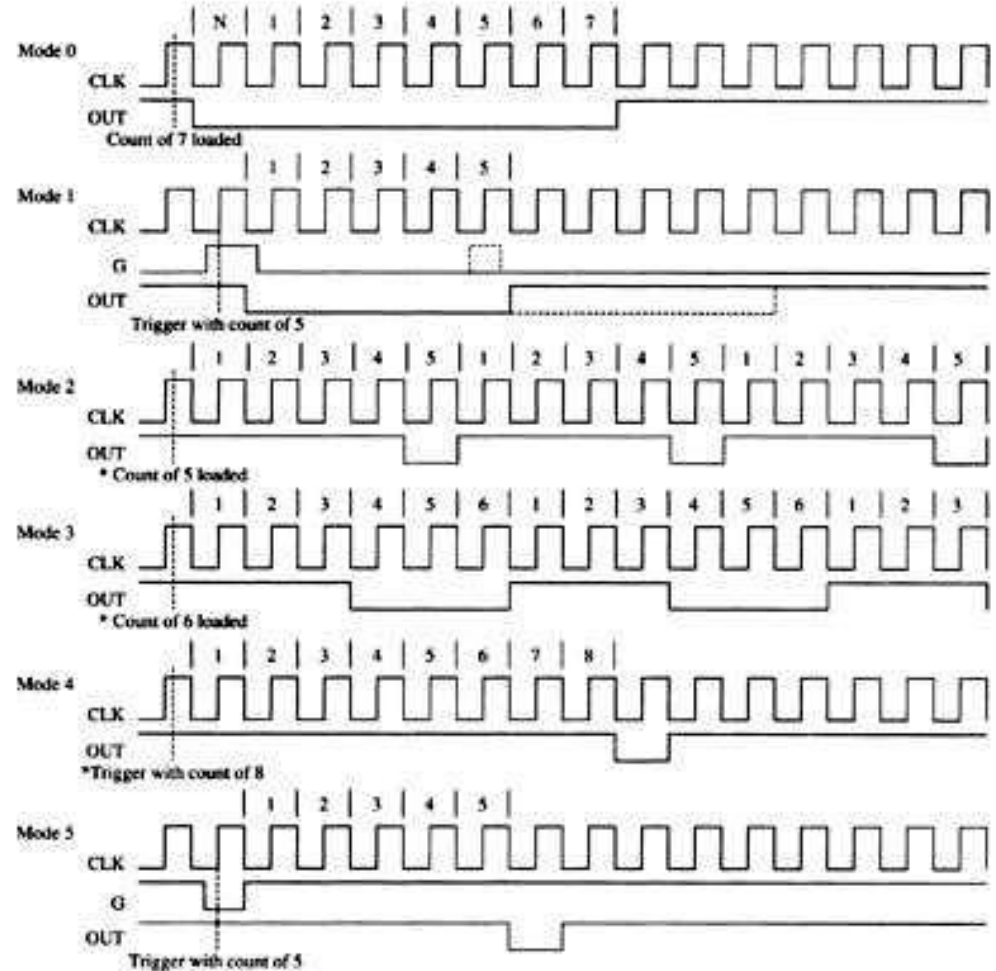

**Figure 11–35** The six modes of operation for the 8254-2 programmable interval timer. The G input stops the count when 0 in modes 2, 3, and 4.

# Mode 0

- Allows 8254 to be used as an events counter.
- Output becomes logic 0 when the control word is written and remains until N plus the number of programmed counts.
- Note that gate (G) input must be logic 1 to allow the counter to count.
- If G becomes logic 0 in the middle of the count, the counter will stop until G again becomes logic 1.

# Mode 1

- Causes function as a retriggerable, monostable multivibrator (one-shot).
- G input triggers the counter so it develops a pulse at the OUT connection that becomes logic 0 for the duration of the count.
  - if the count is 10, the OUT connection goes low for 10 clocking periods when triggered
- If G input occurs within the output pulse, the counter is reloaded and the OUT connection continues for the total length of the count.

# Mode 2

- Allows the counter to generate a series of continuous pulses one clock pulse wide.
  - pulse separation is determined by the count
- For a count of 10, output is logic 1 for nine clock periods and low for one clock period.
- The cycle is repeated until the counter is programmed with a new count or until the G pin is placed at logic 0.
  - G input must be logic 1 for this mode to generate a continuous series of pulses



# Mode 3

- Generates a continuous square wave at the OUT connection, provided the G pin is logic 1.
- If the count is even, output is high for one half of the count and low for one half of the count.
- If the count is odd, output is high for one clocking period longer than it is low.
  - if the counter is programmed for a count of 5, the output is high for three clocks and low for two clocks

# Mode 4

- Allows a single pulse at the output.
- If count is programmed as 10, output is high for 10 clocking periods and low for one period.
  - the cycle does not begin until the counter is loaded with its complete count
- Operates as a software triggered one-shot.
- As with modes 2 and 3, this mode also uses the G input to enable the counter.
  - G input must be logic 1 for the counter to operate for these three modes


# Mode 5

- A hardware triggered one-shot that functions as mode 4.
  - except it is started by a trigger pulse on the G pin instead of by software
- This mode is also similar to mode 1 because it is retriggerable.

# ***Generating a Waveform with the 8254***

- Fig 11–36 shows an 8254 connected to I/O ports 0700H, 0702H, 0704H, and 0706H of an 80386SX.
- The addresses are decoded by using a PLD that also generates a write strobe signal for the 8254, which is connected to the low-order data bus connections.

**Figure 11–36** The 8254 interfaced to an 8 MHz 8086 so that it generates a 100 KHz square wave at OUT0 and a 200 KHz continuous pulse at OUT1.

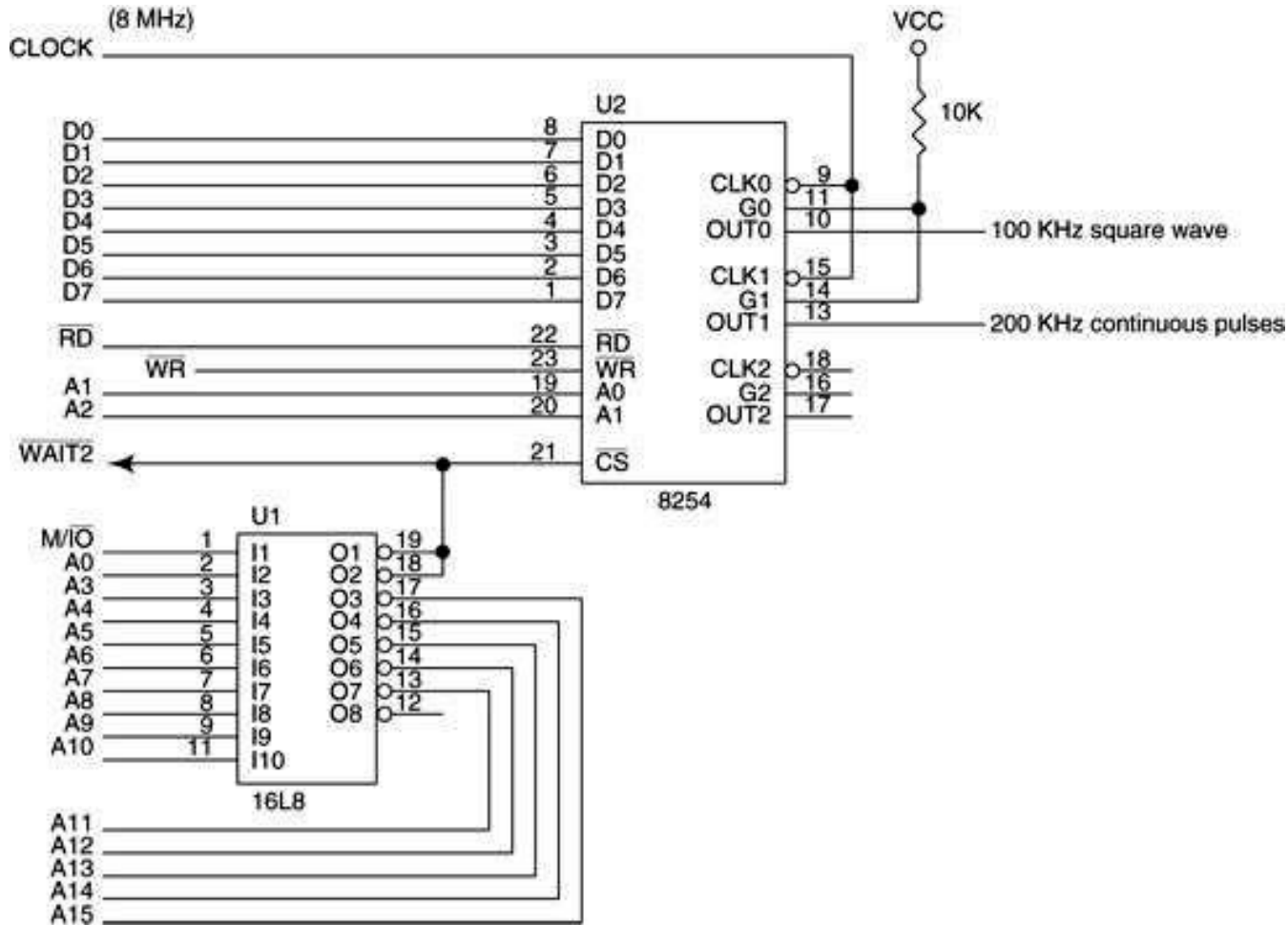


- The PLD also generates a wait signal for the microprocessor that causes two wait states when the 8254 is accessed.
- The wait state generator connected to the microprocessor actually controls the number of wait states inserted into the timing.
- Example 11–24 lists the program that generates a 100 KHz square-wave at OUT0 and a 200 KHz continuous pulse at OUT1.

# *Reading a Counter*

- Each counter has an internal latch read with the read counter port operation.
  - the latches will normally follow the count
- If counter contents are needed, the latch can remember the count by programming the counter latch control word.
- See Figure 11–37.
  - counter contents are held in a latch until read


**Figure 11–37** The 8254-2 counter latch control word.

 




- When a read from the latch or counter is programmed, the latch tracks the contents.
- When necessary for contents of more than one counter to be read at the same time, the read-back control word is used
- Illustrated in Figure 11–38.

**Figure 11–38** The 8254-2 read-back control word.

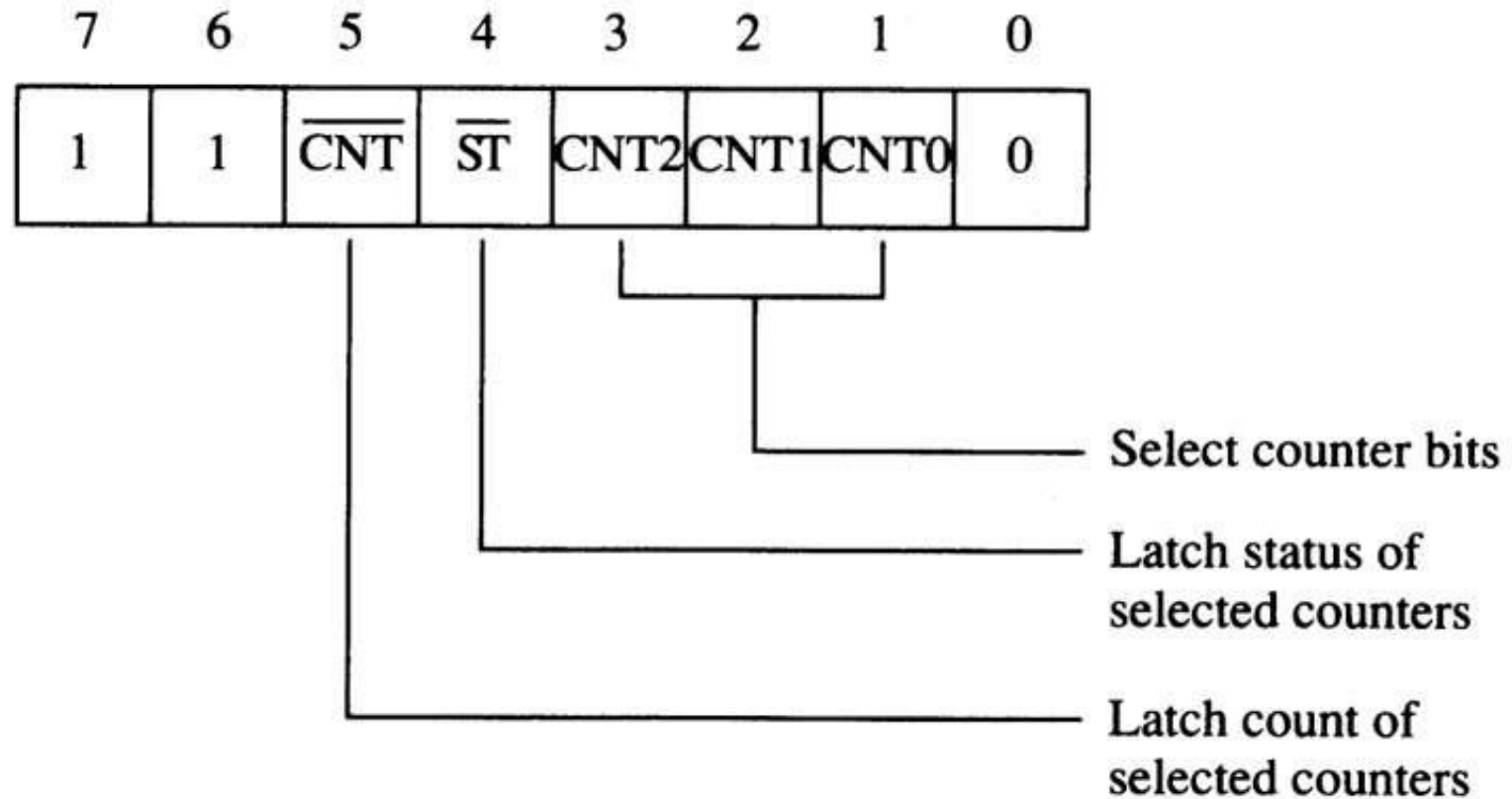

- With the read-back control word, the  $\overline{\text{CNT}}$  bit is logic 0 to cause the counters selected by CNT0, CNT1, and CNT2 to be latched.
- If the status register is to be latched, then the bit is placed at logic 0.
- Figure 11–39 shows the status register, which shows:
  - the state of the output pin
  - whether the counter is at its null state (0)
  - how the counter is programmed


**Figure 11–39** The 8254-2 status register.

 

# DC Motor Speed and Direction Control

- An application of 8254 is as a motor speed controller for a DC motor.
- Fig 11–40 shows the schematic diagram of the motor and associated driver circuitry.
- It also illustrates the interconnection of the 8254, a flip-flop, and the motor and its driver.


**Figure 11–40** Motor speed and direction control using the 8254 timer.

 

- if Q output of the 74ALS112 is logic 1, the motor spins in its forward direction
- if logic 0, the motor spins in reverse
- if flip-flop output alternates between logic 1 and 0, the motor spins in either direction at various speeds
- if the duty cycle of the Q output is 50%, the motor will not spin at all and exhibits some holding torque

- Fig 11–41 shows some timing diagrams and effects on the speed/direction of the motor.
- Each counter generates pulses at different positions to vary the duty cycle at the Q output of the flip-flop.
- This output is also called *pulse width modulation*.
- Example 11–25 lists a procedure that controls the speed and direction of the motor.

**Figure 11–41** Timing for the motor speed and direction control circuit of Figure 11–40. (a) No rotation, (b) high-speed rotation in the reverse direction, and (c) high-speed rotation in the forward direction.

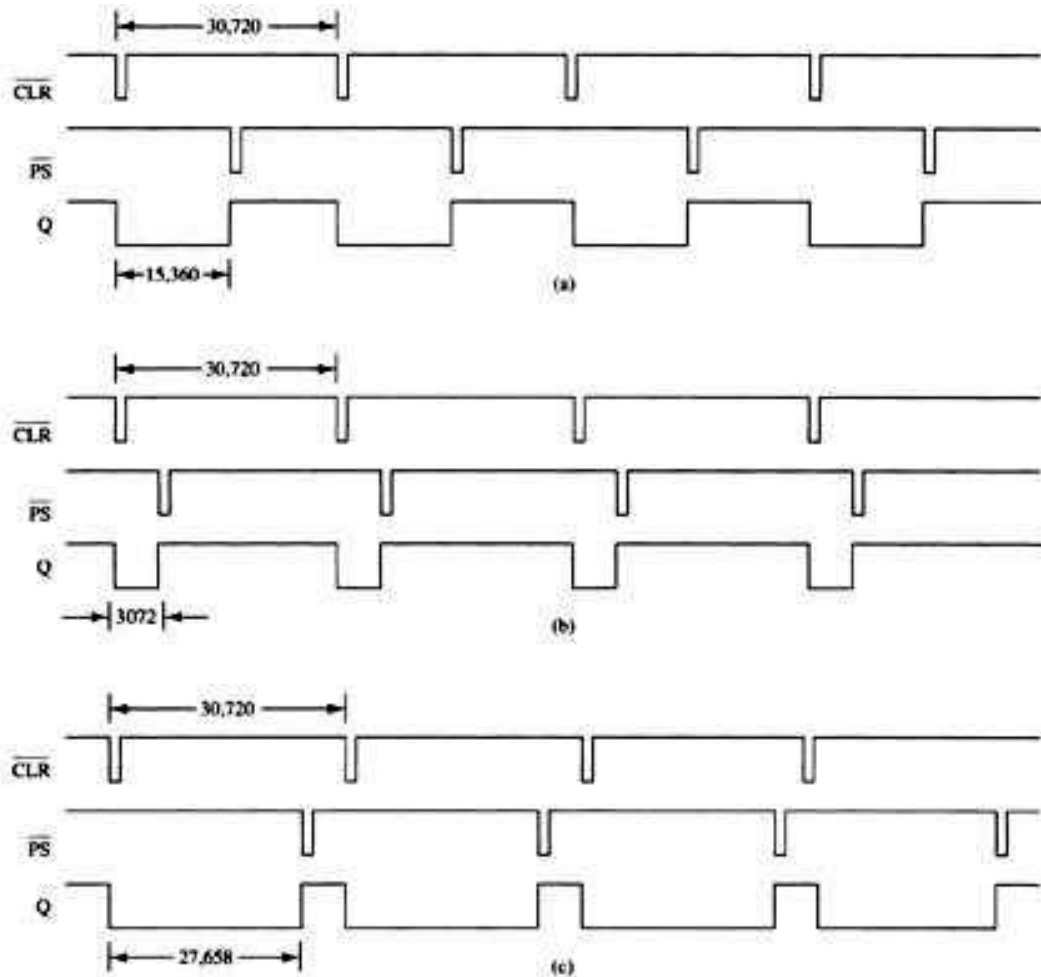




# 11–5 16550 PROGRAMMABLE COMMUNICATIONS INTERFACE

- National Semiconductor Corp's PC16550D is a programmable communications interface designed to connect to virtually any type of serial interface.
- 16550 is a universal asynchronous receiver/transmitter (UART) fully compatible with Intel microprocessors.

- 16550 operates at 0–1.5 M baud.
  - baud rate is bps (bits transferred per second) including start, stop, data, and parity
  - bps are bits per second; Bps is bytes per second
- 16550 also includes a programmable baud rate generator and separate FIFOs for input and output data to ease the load on the microprocessor.
- Each FIFO contains 16 bytes of storage.
- The most common communications interface found in the PC and many modems.

# Asynchronous Serial Data

- Asynchronous serial data are transmitted and received without a clock or timing signal.
  - shown here are two frames of asynchronous serial data
  - each frame contains a start bit, seven data bits, parity, and one stop bit

 

**Figure 11–42** Asynchronous serial data.

- Dial-up communications systems of the past, such as CompuServe, Prodigy, and America Online, used 10 bits for asynchronous serial data with even parity.
- Most Internet and BBS services use 10 bits, but normally do not use parity.
  - instead, eight data bits are transferred, replacing parity with a data bit
- This makes byte transfers of non-ASCII data much easier to accomplish.

# 16550 Functional Description

- Fig 11–43 shows pin-outs of a 16550 UART.
- The device is available as a 40-pin DIP (**dual in-line package**) or as a 44-pin PLCC (**plastic leadless chip carrier**).
- Two completely separate sections are responsible for data communications.
  - the receiver and the transmitter
- Because each sections is independent, 16550 is able to function in simplex, half-duplex, or full-duplex modes.

**Figure 11–43** The pin-out of the 16550 UART.



- A major feature of the 16550 is its internal receiver and transmitter FIFO (first-in, first-out) memories.
- Because each is 16 bytes deep, the UART requires attention from the processor only after receiving 16 bytes of data.
  - also holds 16 bytes before the processor must wait for the transmitter
- The FIFO makes this UART ideal when interfacing to high-speed systems because less time is required to service it.

- A **simplex** system is one in which the transmitter or receiver is used by itself.
  - such as in an FM (**frequency modulation**) radio station
- A **half-duplex** system is a CB (**citizens band**) radio.
  - transmit and receive, but not at the same time
- A **full-duplex** system allows transmission and reception in both directions simultaneously.
  - the telephone is a full-duplex system



- The 16550 can control a **modem (modulator/demodulator)**, a device that converts TTL serial data into audio tones that can pass through the telephone system.
- Six pins on 16650 are for modem control:  $\overline{\text{DSR}}$  (**data set ready**),  $\overline{\text{DTR}}$  (**data terminal ready**),  $\overline{\text{CTS}}$  (**clear-to-send**),  $\overline{\text{RTS}}$  (**request-to-send**),  $\overline{\text{RI}}$  (**ring indicator**), and  $\overline{\text{DCD}}$  (**data carrier detect**).
- The modem is referred to as the data set and the 16550 is referred to as the data terminal.

# 16550 Pin Functions

$A_0$ ,  $A_1$ ,  $A_2$

- The **address inputs** are used to select an internal register for programming and also data transfer.
- See Table 11–5 for a list of each combination of the address inputs and the registers selected.

# ADS

- The **address strobe** input is used to latch the address lines and chip select lines.
- If not needed (as in the Intel system), connect this pin to ground.
- The ADS pin is designed for use with Motorola microprocessors.

# BAUDOUT

- The **baud out** pin is where the clock signal generated by the baud rate generator from the transmitter section is made available.
- It is most often connected to the RCLK input to generate a receiver clock that is equal to the transmitter clock.

# $CS_0$ , $CS_1$ , $\overline{CS_2}$

- The **chip select** inputs must all be active to enable the 16550 UART.

## $\overline{CTS}$

- The **clear-to-send** (if low) indicates that the modem or data set is ready to exchange information.
- This pin is often used in a half-duplex system to turn the line around.

# $D_0-D_7$

- The **data bus** pins are connected to the microprocessor data bus.

## $\overline{DCD}$

- **Data carrier detect** input is used by the modem to signal the 16550 that a carrier is present.

# DTR

- **Data terminal ready** is an output that indicates that the data terminal (16550) is ready to function.

# INTR

- **Interrupt request** is an output to the microprocessor used to request an interrupt (INTR=1) when the 16550 has a receiver error, it has received data, and the transmitter is empty.

# DDIS

- The **disable driver** output becomes logic 0 to indicate the microprocessor is reading data from the UART.
- DDIS can be used to change the direction of data flow through a buffer.

---

# DSR

- **Data set ready** is an input to the 16550, indicating that the modem or data set is ready to operate.



# MR

- **Master reset** initializes the 16550 and should be connected to the system RESET signal.

## $\overline{\text{OUT1}}$ , $\overline{\text{OUT2}}$

- **User-defined output pins** that can provide signals to a modem or any other device as needed in a system.

# RCLK

- **Receiver clock** is the clock input to the receiver section of the UART.

# **RD, $\overline{\text{RD}}$**

- **Read inputs** (either may be used) cause data to be read from the register specified by the address inputs to the UART.

# **$\overline{\text{RI}}$**

- **Ring indicator** input is placed at logic 0 by the modem to indicate the phone is ringing.

# **$\overline{\text{RTS}}$**

- **Request-to-send** is a signal to the modem indicating that the UART wishes to send data.

# SIN, SOUT

- These are the **serial data pins**. SIN accepts serial data and SOUT transmits serial data.

---

## RXRDY

- **Receiver ready** is a signal used to transfer received data via DMA techniques.

---

## TXRDY

- **Transmitter ready** is a signal used to transfer transmitter data via DMA.

# WR, WR

- **Write** (either may be used) connects to the microprocessor write signal to transfer commands and data to the 16550.

# XIN, XOUT

- These are the main **clock** connections.
- A crystal is connected across these pins to form a crystal oscillator, or XIN is connected to an external timing source.

# Programming the 16550


- Programming is a two-part process & includes the initialization dialog and operational dialog.
- In the PC, which uses the 16550 or its programming equivalent, I/O port addresses are decoded at 3F8H - 3FFH for COM port 0 and 2F8H - 2FFH for COM port 2.

# *Initializing the 16550*

- Initialization dialog after a hardware or software reset, consists of two parts:
  - programming the line control register
  - programming the baud rate generator
- The line control register selects the number of data bits, stop bits, and parity (whether even or odd, or if parity is sent as a 1 or a 0)
- Baud rate generator is programmed with a divisor that determines the baud rate of the transmitter section.

- Fig 11–44 illustrates the line control register.
- The line control register is programmed by outputting information to port 011 ( $A_2$ ,  $A_1$ ,  $A_0$ ).
- The rightmost two bits of the line control register select the number of transmitted data bits (5, 6, 7, or 8).
- Number of stop bits is selected by S in the line control register.
  - if  $S = 0$ , one stop bit is used
  - if  $S = 1$ , 1.5 stop bits are used for five data bits, & two stop bits with six, seven, or eight data bits

**Figure 11–44** The contents of the 16550 line control register.

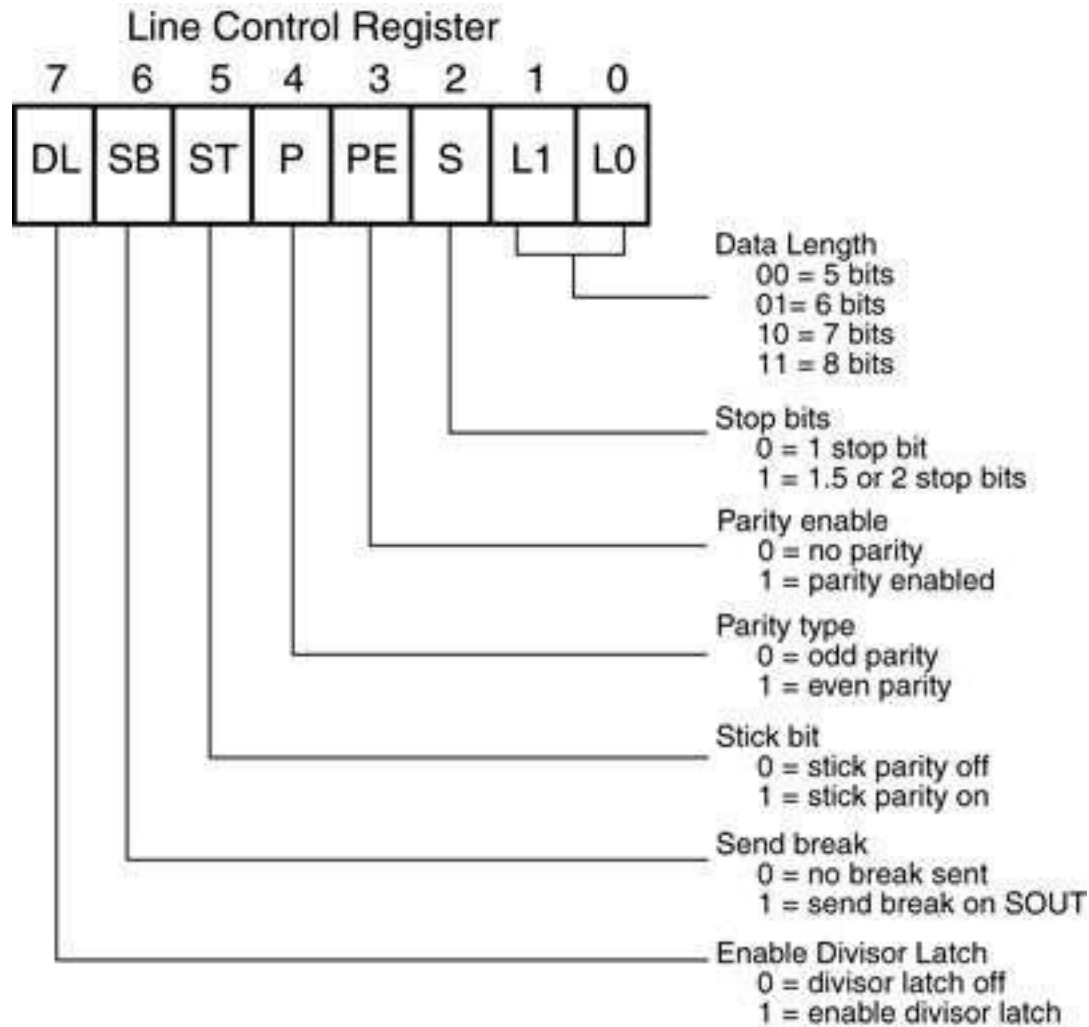




# ***Programming the Baud Rate***

- The baud rate generator is programmed at I/O addresses 000 and 001 ( $A_2, A_1, A_0$ ).
- Port 000 is used to hold the least significant part of the 16-bit divisor and port 001 is used to hold the most significant part.
  - value used for the divisor depends on the external clock or crystal frequency
- Table 11–7 illustrates common baud rates obtainable if an 18.432 MHz crystal is used as a timing source.

# ***Sample Initialization***


- Suppose an asynchronous system requires seven data bits, odd parity a baud rate of 9600, and one stop bit.
- Example 11–24 lists a procedure to initialize the 16550 to function in this manner.
- Fig 11–45 shows the interface to the 8088 microprocessor, using a PLD to decode the 8-bit port addresses F0H through F7H.

**Figure 11–45** The 16550 interfaced to the 8088 microprocessor at ports 00F0H–00F7H.

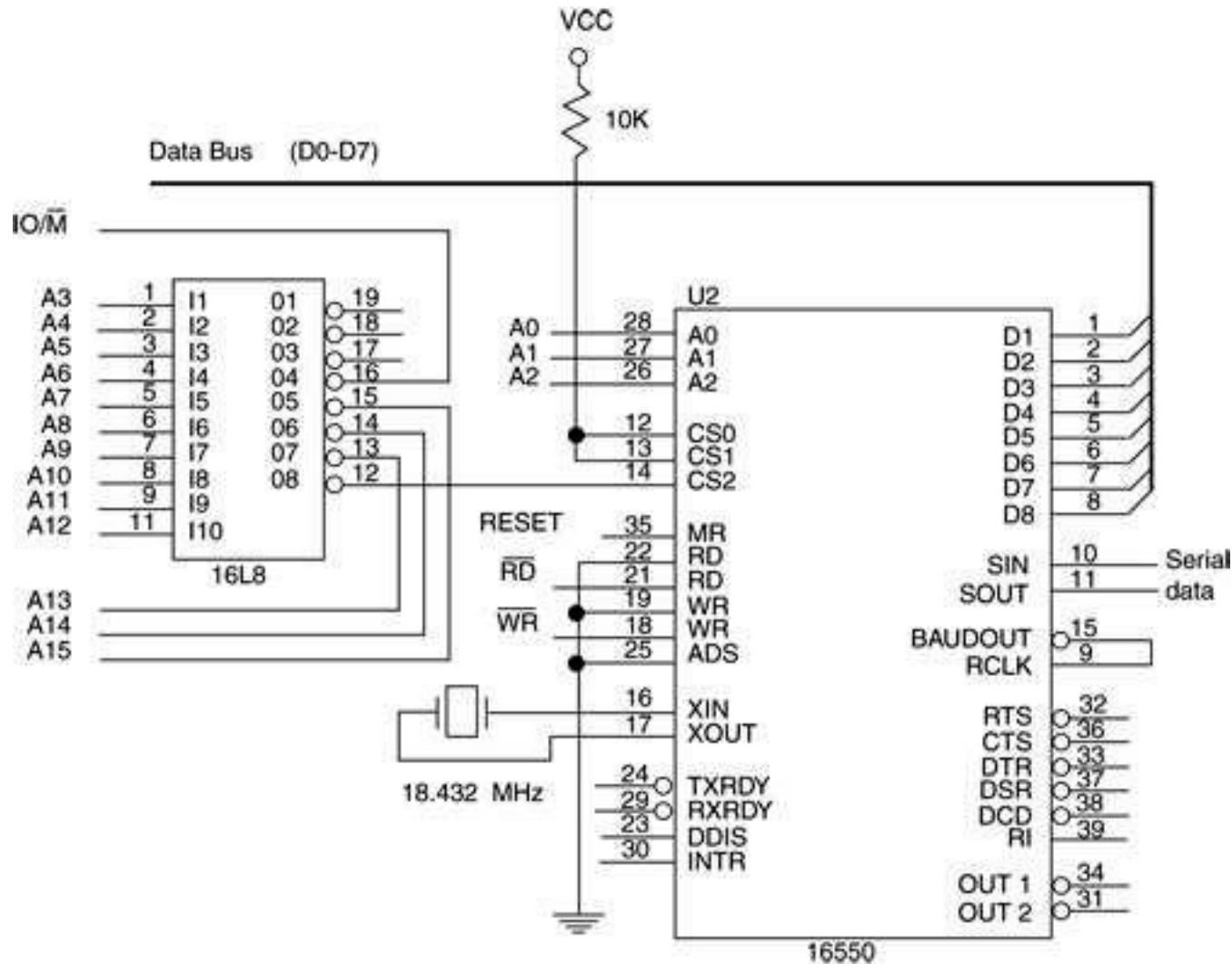

- After the line control register and baud rate divisor are programmed into the 16550, it is still not ready to function.
- The FIFO control register must still be programmed.
  - at port F2H in the circuit of Figure 11–45
- Fig 11–46 illustrates the FIFO control register for the 16550.
  - the register enables the transmitter & receiver (bit 0=1), clears the transmitter & receiver FIFOs
  - it also provides control for the 16550 interrupts

**Figure 11–46** The FIFO control register of the 16550 UART.

 


- The last section of Example 11–26 places a 7 into the FIFO control register.
- This enables the transmitter and receiver, and clears both FIFOs.
- The 16550 is now ready to operate, but without interrupts.
  - interrupts are automatically disabled when the MR (master reset) input is placed at logic 1 by the system RESET signal.

# ***Sending Serial Data***

- Before serial data can be sent or received, we need to know the function of the line status register
  - see Figure 11–47
- The line status register contains information about error conditions and the state of the transmitter and receiver.
- This register is tested before a byte is transmitted or can be received.

**Figure 11–47** The contents of the line status register of the 16550 UART.

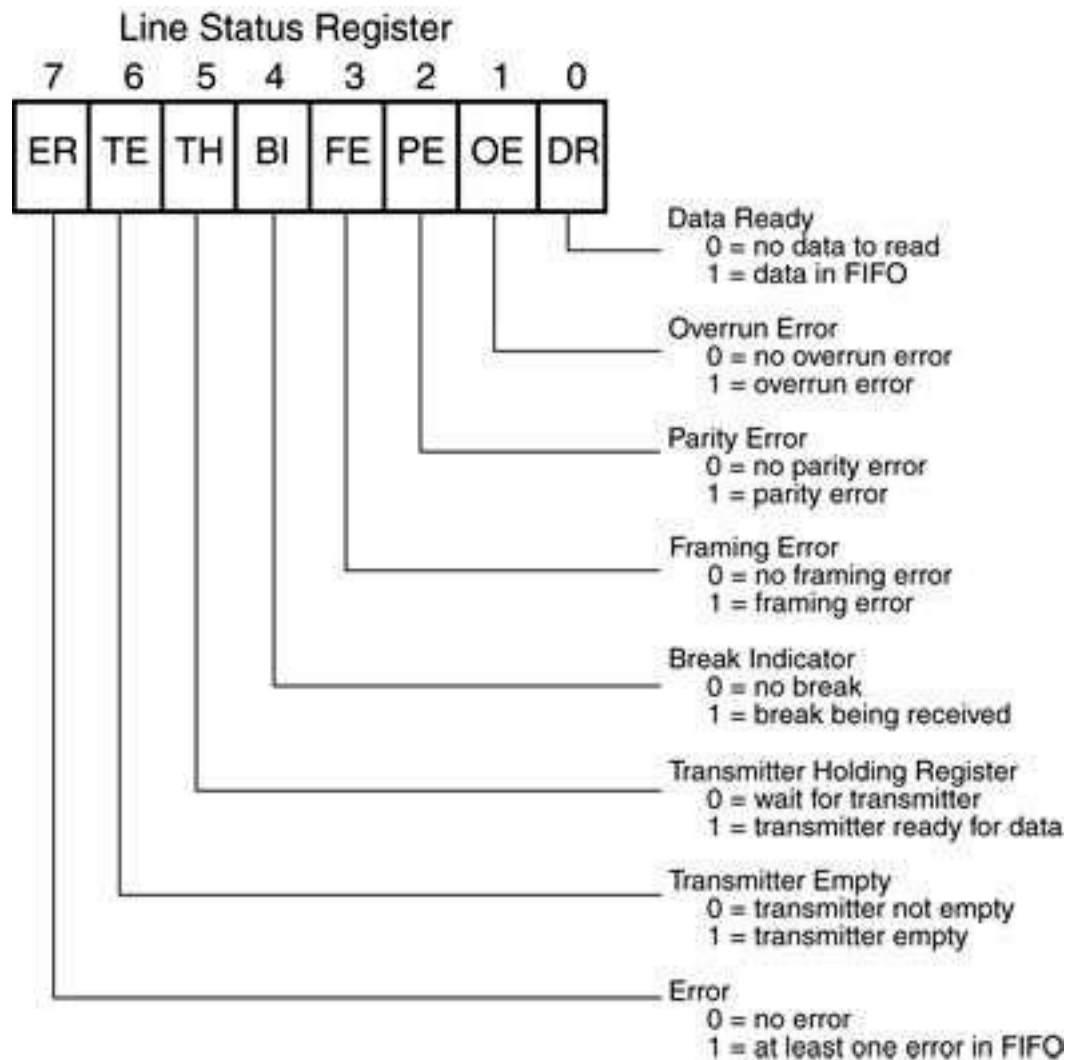



# *Receiving Serial Data*

- To read received information from the 16550, test the DR bit of the line status register.
  - example 11–28 lists a procedure to test the DR bit to decide if the 16550 has received any data
- Upon the reception of data, the procedure tests for errors.
  - if an error is detected, the procedure returns with AL equal to an ASCII ‘?’
  - if no error has occurred, the procedure returns with AL equal to the received character

# ***UART Errors***

- Errors detected by 16550 are:
  - parity, framing, and overrun errors
- These errors should not occur during normal operation.
- A **parity error** indicates the received data contain the wrong parity.
  - if a parity error occurs, it indicates noise was encountered during reception

- A **framing error** indicates the start and stop bits are not in their proper places.
  - occurs if the receiver is receiving data at an incorrect baud rate
- An **overflow error** indicates data have overrun the internal receiver FIFO buffer.
  - occurs only if the software fails to read the data from the UART before the receiver FIFO is full

# 11–6 ANALOG-TO-DIGITAL (ADC) & DIGITAL-TO-ANALOG (DAC) CONVERTERS

- These devices are used to interface the microprocessor to the analog world.
- Many events monitored and controlled by the microprocessor are analog events.
- These range from monitoring all forms of events, even speech, to controlling motors and like devices.


# The DAC0830 Digital-to-Analog Converter

- A fairly common and low-cost digital-to-analog converter is the DAC0830.
  - a product of National Semiconductor Corp
- An 8-bit converter that transforms an 8-bit binary number into an analog voltage.
- Other converters are available that convert from 10-, 12-, or 16-bit binary numbers into analog voltages.

- The number of voltage steps generated by the converter is equal to the number of binary input combinations.
  - an 8-bit converter generates 256 voltage levels
  - a 10-bit converter generates 1024 levels
- The DAC0830 is a medium-speed converter that transforms a digital input to an analog output in approximately  $1.0 \mu\text{s}$ .

- Figure 11–48 shows pin-outs of a DAC0830.
- The device has eight data bus connections for the application of the digital input code.
- Analog outputs labeled IOOUT1 & IOOUT2 are inputs to an external operational amplifier.
- Because this is an 8-bit converter, its output step voltage is defined as  $-V_{REF}$  (reference voltage), divided by 255.
  - the step voltage is often called the resolution of the converter

**Figure 11–48** The pin-out of the DAC0830 digital-to-analog converter.

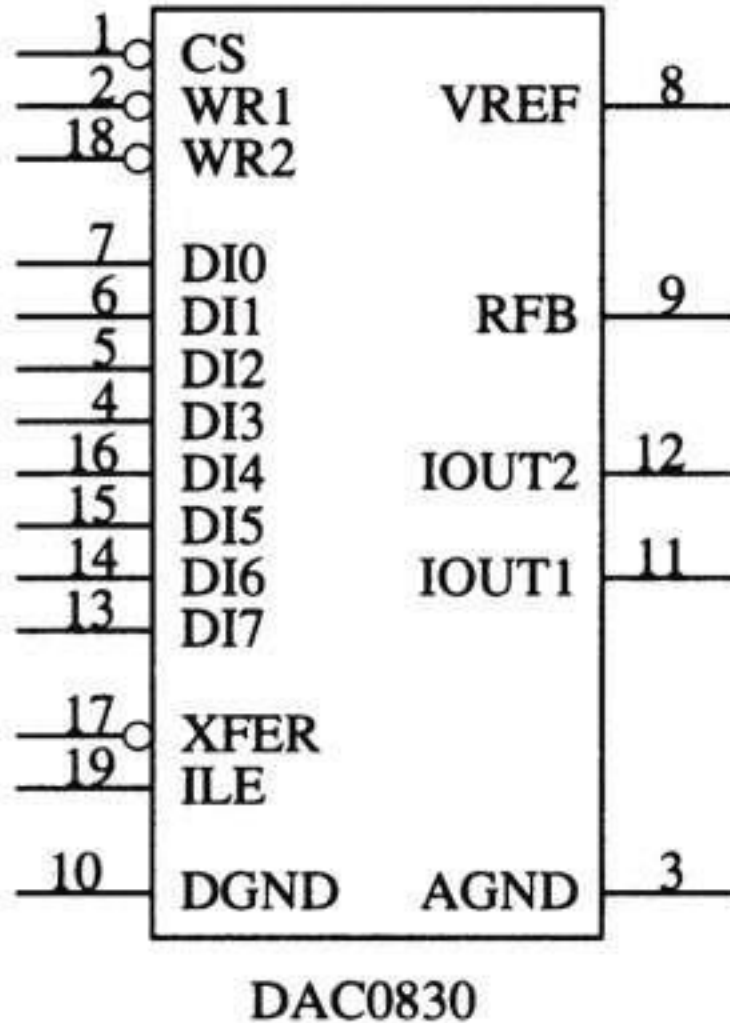




# ***Internal Structure of the DAC0830***

- Fig 11–49 shows the internal structure.
- This device contains two internal registers.
  - the first is a holding register
  - the second connects to the R–2R internal ladder converter
- The two latches allow one byte to be held while another is converted.
- The first latch is often disabled and the second for entering data into the converter.

**Figure 11–49** The internal structure of the DAC0830.

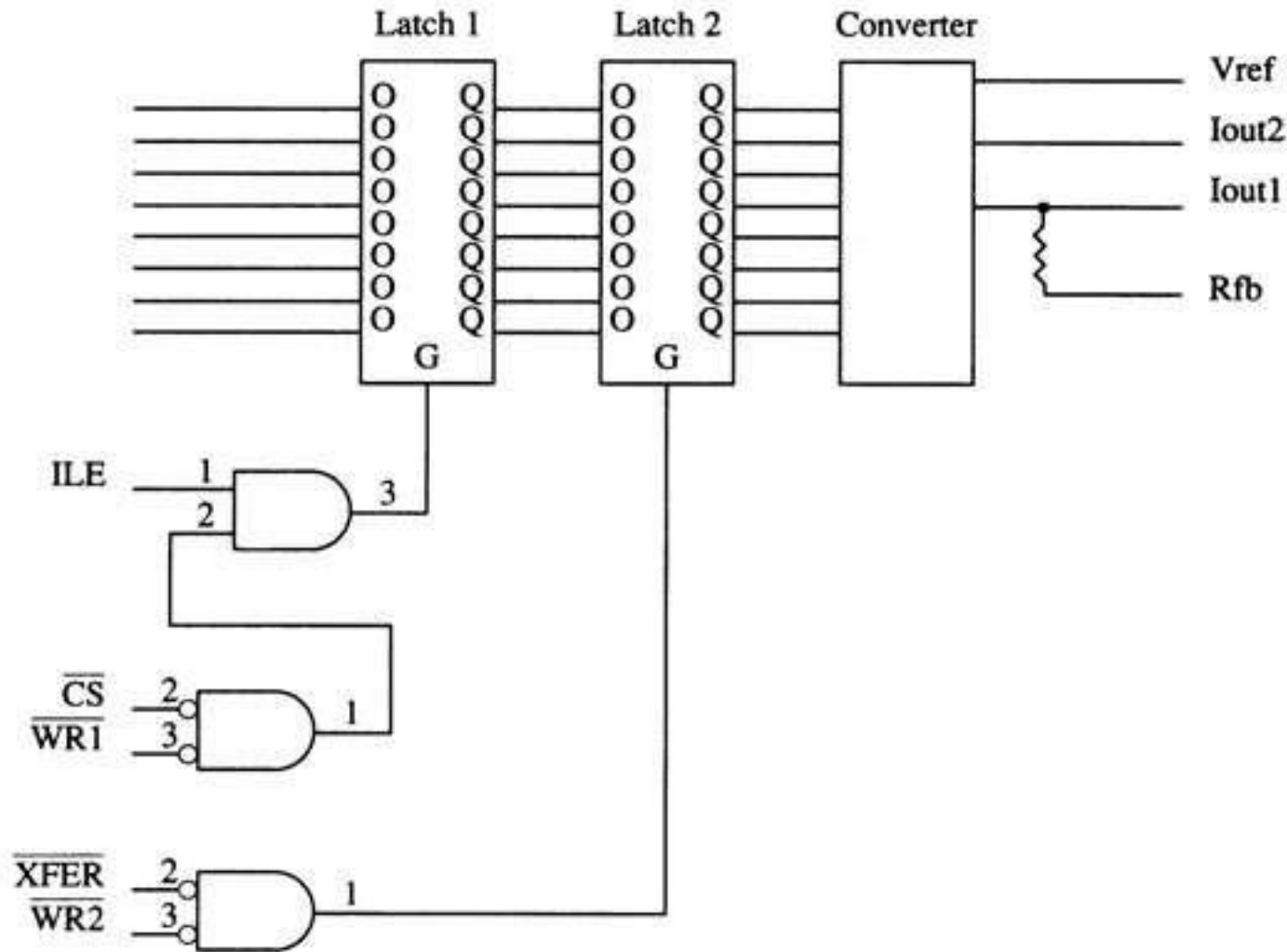


- Both latches within the DAC0830 are transparent latches.
  - when G input is logic 1, data pass through
  - when G input becomes logic 0, data are latched
- The output of the R–2R ladder within the converter appears at IOUT1 and IOUT2.
- These outputs are designed to be applied to an operational amplifier such as a 741 or similar device.

# ***Connecting the DAC0830 to the Microprocessor.***

- A PLD is used to decode the DAC0830 at I/O port address 20H.
  - when an OUT 20H,AL instruction is executed, contents of data bus connections  $AD_0$ – $AD_7$  are passed to the converter in the DAC0830
- The 741 operational amplifier, along with the –12 V zener reference voltage, causes the full-scale output voltage to equal +12 V.
- See Fig 11–50.


**Figure 11–50** A DAC0830 interfaced to the 8086 microprocessor at 8-bit I/O location 20H.

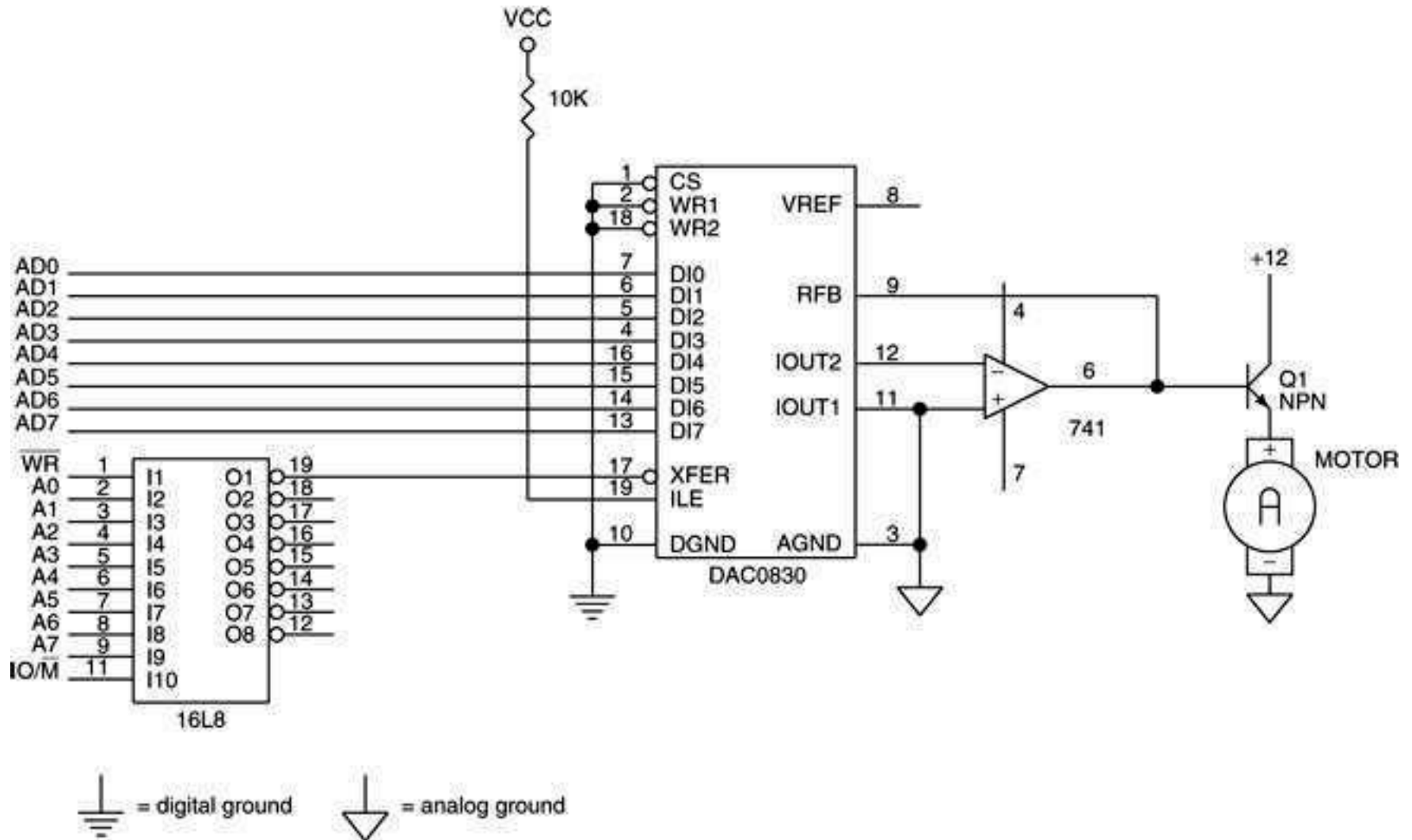

# The ADC080X Analog-to-Digital Converter

- A common, low-cost ADC, compatible with a wide range of microprocessors.
  - while there are faster ADCs available with more resolution, this device is ideal for applications that do not require a high degree of accuracy
- ADC080X requires up to 100  $\mu$ s to convert an analog input voltage into a digital output code.
- Figure 11–51 shows the pin-out of the ADC0804 converter.


**Figure 11–51** The pin-out of the ADC0804 analog-to-digital converter.

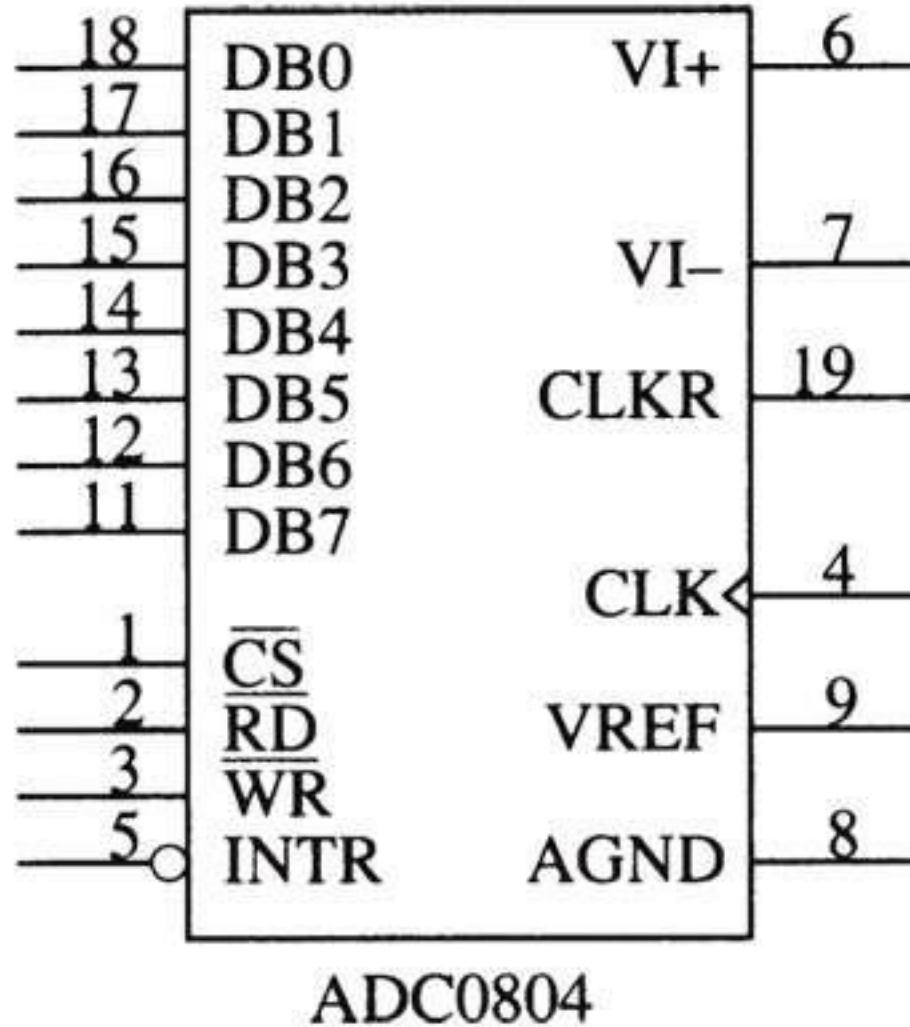

- To operate the converter, the  $\overline{WR}$  pin is pulsed with  $\overline{CS}$  grounded to start the conversion process.
- See Fig 11–52 for a timing diagram that shows the interaction of the control signals.
- If a time delay is used that allows at least 100  $\mu s$  of time, there is no need to test INTR pin.
- Another option is to connect the INTR pin to an interrupt input, so when the conversion is complete, an interrupt occurs.




**Figure 11–52** The timing diagram for the ADC0804 analog-to-digital converter.

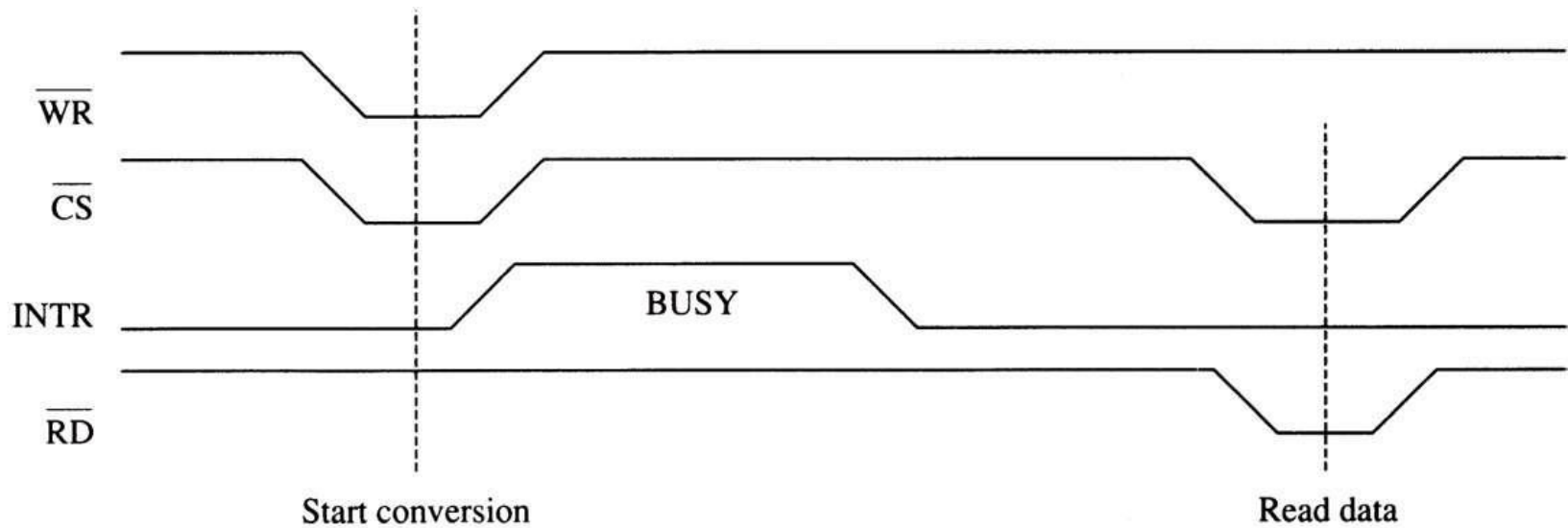


# ***The Analog Input Signal***

- Before ADC0804 can be connected, the two analog inputs must be understood:
  - VIN(+) and VIN(–)
- These differential inputs are summed by the operational amplifier to produce a signal for the internal analog-to-digital converter.
- These inputs are connected to an internal operational amplifier as shown in Fig 11–53.

**Figure 11–53** The analog inputs to the ADC0804 converter. (a) To sense a 0- to +5.0 V input. (b) To sense an input offset from ground.

 

(a)

 


(b)

# ***Generating the Clock Signal***

- ADC0804 requires a clock source to operate.
- It can be an external clock applied to CLK IN pin or can be generated with an RC circuit.
  - permissible range of clock frequencies is 100 KHz - 1460 KHz.
  - desirable to use a frequency as close as possible to 1460 KHz so conversion time is minimized
- If generated with an RC circuit, CLK IN and CLK R pins are connected to an RC circuit, as illustrated in Figure 11–54.


**Figure 11–54** Connecting the RC circuit to the CLK IN and CLK R pins on the ADC0804.

 

# ***Connecting the ADC0804 to the Microprocessor***

- ADC0804 interfaced to an 8086 is illustrated in Figure 11–55.
  - $V_{REF}$  is not attached to anything, which is normal
- Suppose ADC0804 is decoded at I/O port address 40H for the data and address 42H for INTR.
- The procedure to read data is listed in Example 11–29.

**Figure 11–55** The ADC0804 interfaced to the 8086 microprocessor.

 


# Using the ADC0804 and the DAC0830

- This illustrates an example using an ADC0804 and a DAC0830 to capture and replay audio signals or speech.
  - a speech synthesizer has been used in the past to generate speech, but quality was poor
- For human quality speech, we can use an ADC0804 to capture an audio signal and store it for later playback through a DAC0830.



- Fig 11–56 shows circuitry required to connect the ADC0804 at I/O ports 0700H and 0702H.
- The DAC0830 is interfaced at I/O port 704H.
  - These ports are in the low bank of a 16-bit microprocessor such as the 8086/80386SX
- The software appears in Example 11–30.
- It reads a 1-second burst of speech and plays it back 10 times.

**Figure 11–56** A circuit that stores speech and plays it back through the speaker.

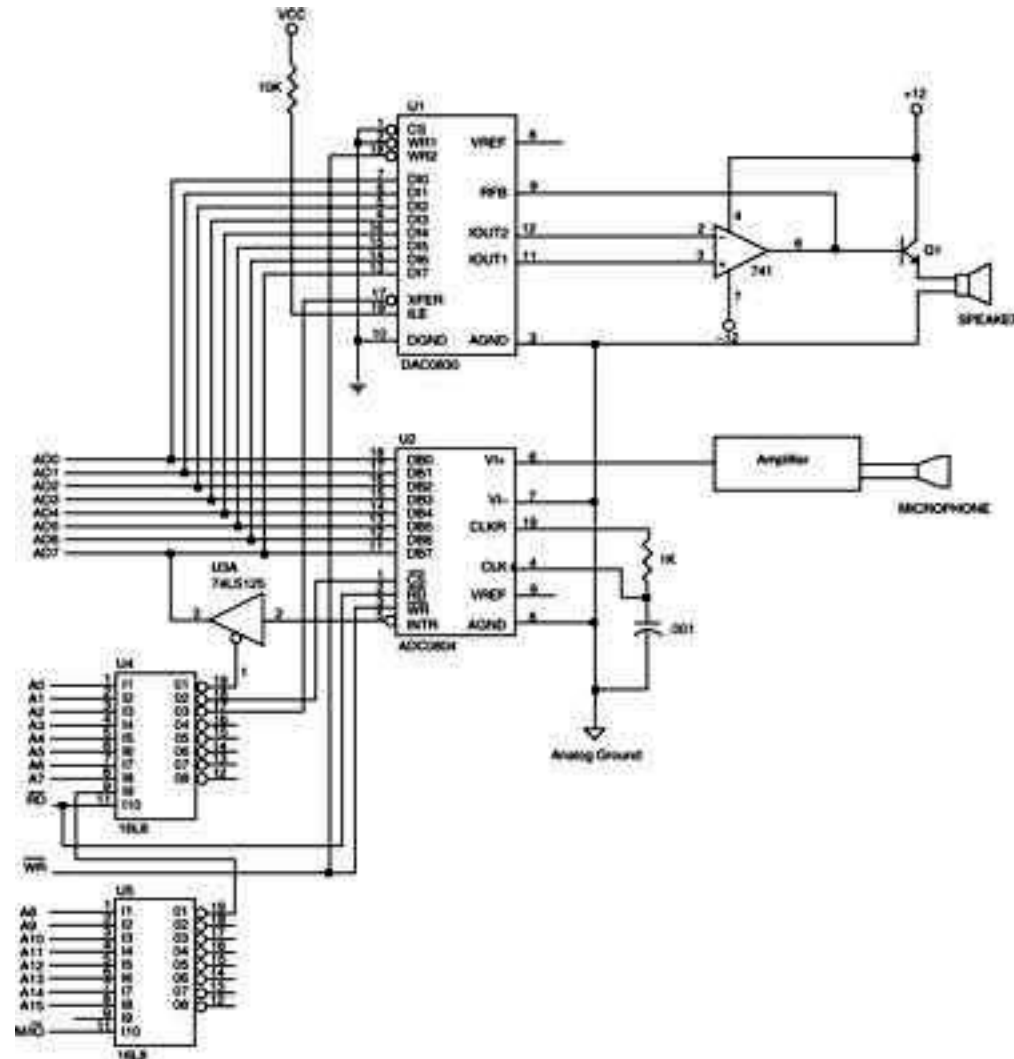

- A procedure called READS reads the speech.
- A second, PLAYS, plays it back.
- The speech is sampled and stored in a section of memory called WORDS.
- The sample rate is chosen at 2048 samples per second, which renders acceptable-sounding speech.

# SUMMARY

- The 8086-Core2 microprocessors have two basic types of I/O instructions: IN and OUT.
- The IN instruction inputs data from an external I/O device into either the AL (8-bit) or AX (16-bit) register.
- The IN instruction is available as a fixed port instruction, a variable port instruction, or a string instruction (80286-Pentium 4) INSB or INSW.

# SUMMARY

(*cont.*)

- The OUT instruction outputs data from AL or AX to an external I/O device and is available as a fixed, variable, or string instruction OUTSB or OUTSW.
- The fixed port instruction uses an 8-bit I/O port address, while the variable and string I/O instructions use a 16-bit port number found in the DX register.

# SUMMARY

(*cont.*)

- Isolated I/O, sometimes called direct I/O, uses a separate map for the I/O space, freeing the entire memory for use by the program.
- Isolated I/O uses the IN and OUT instructions to transfer data between the I/O device and the micro-processor.

# SUMMARY

(*cont.*)

- Memory-mapped I/O uses a portion of the memory space for I/O transfers.
- In addition, any instruction that addresses a memory location using any addressing mode can be used to transfer data between the microprocessor and the I/O device using memory-mapped I/O.

# SUMMARY

(*cont.*)

- All input devices are buffered so that the I/O data are connected only to the data bus during the execution of the IN instruction.
- The buffer is either built into a programmable peripheral or located separately.
- All output devices use a latch to capture output data during the execution of the OUT instruction.



# SUMMARY

(*cont.*)

- Handshaking or polling is the act of two independent devices synchronizing with a few control lines.
- This communication between the computer and the printer is a handshake or a poll.
- Interfaces are required for most switch-based input devices and for most output devices that are not TTL-compatible.

# SUMMARY

(*cont.*)

- The I/O port number appears on address bus connections A7-A0 for a fixed port I/O instruction and on A15-A0 for a variable port I/O instruction (note that A15-A8 contains zeros for an 8-bit port).
- In both cases, address bits above A15 are undefined.

# SUMMARY

(*cont.*)

- Because the 8086/80286/80386SX microprocessors contain a 16-bit data bus and the I/O addresses reference byte-sized I/O locations, I/O space is also organized in banks, as is the memory system.
- In order to interface an 8-bit I/O device to the 16-bit data bus, we often require separate write strobes (an upper and a lower) for I/O write operations.

# SUMMARY

(*cont.*)

- The I/O port decoder is much like the memory address decoder, except instead of decoding the entire address, the I/O port decoder decodes only a 16-bit address for variable port instructions and often an 8-bit port number for fixed I/O instructions.
- The 82C55 is a programmable peripheral interface (PIA) that has 24 I/O pins that are programmable in two groups of 12 pins each (group A and group B).

# SUMMARY

(*cont.*)

- The 82C55 operates in three modes: simple I/O (mode 0), strobed I/O (mode 1), and bidirectional I/O (mode 2).
- When the 82C55 is interfaced to the 8086 operating at 8 MHz, we insert two wait states because the speed of is faster than the 82C55 can handle.
- The LCD display device requires a fair amount of software, but it displays AS-CII-coded information.

# SUMMARY

(*cont.*)

- The 8254 is a programmable interval timer with three 16-bit counters that count in binary or binary-coded decimal (BCD).
- Each counter is independent and operates in six different modes: (1) events counter, (2) retriggerable, monostable multivibrator, (3) pulse generator, (4) square-wave generator, (5) software-triggered pulse generator, and (6) hardware-triggered pulse generator.

# SUMMARY

- The 16550 is a programmable communications interface, capable of receiving and transmitting asynchronous serial data.
- The DAC0830 is an 8-bit digital-to-analog converter that converts a digital signal to an analog voltage within  $1.0 \mu\text{s}$ .
- The ADC0804 is an 8-bit analog-to-digital converter that converts an analog signal into a digital signal within  $100 \mu\text{s}$ .