



## ❖ Counters

The flip-flops are the main logic element, which are used to build these circuits since flip-flops have the ability of saving information (the previous outputs effect on the present output). Flip-flops are connected to each other in a certain way to obtain the counters. The number of flip-flops used and the way in which they are connected determine the number of states (called modulus) and the specific sequence of states that the counter goes through during each complete cycle. So a binary mod-8 counter has eight count states, from  $000_2$  to  $111_2$  (e.g. the mod-8 counter actually counts from  $0$  to  $7$ ). Counters are mainly used in counting applications, where they either measure the time interval between two unknown time instants or measure the frequency of a given signal. Counters are divided in to two categories which are asynchronous and synchronous counters.

### 1- Asynchronous Counters

Asynchronous counter is a cascaded arrangement of flip-flops where the output of one flip-flop drives the clock input of the following flip-flop. The number of flip-flops in the cascaded arrangement depends upon the number of different logic states that it goes through before it repeats the sequence, a parameter known as the modulus of the counter. In an asynchronous, also called a ripple counter or a serial counter, the clock input is applied only to the first flip-flop in the cascaded arrangement. The clock input to any subsequent flip-flop comes from the output of its immediately preceding flip-flop. For instance, the output of the first flip-flop acts as the clock input to the



second flip-flop, the output of the second flip-flop feeds the clock input of the third flip-flop and so on. These counters are used to design the up-counters, down-counters. Asynchronous counters has the following properties:

- 1- are also known as ripple counters;
- 2- are very simple;
- 3- use the minimum possible hardware (logic gates);
- 4- employ flip-flops connected serially, with each one triggering (clocking) the next;
- 5- have an overall count which 'ripples' through, meaning the overall operation is relatively slow;

#### ❖ **Propagation Delay in Ripple Counters**

A major problem with ripple counters arises from the propagation delay of the flip-flops constituting the counter. An increased propagation delay puts a limit on the maximum frequency used as clock input to the counter. We can appreciate that the clock signal time period must be equal to or greater than the total propagation delay. The maximum clock frequency therefore corresponds to a time period that equals the total propagation delay. If  $t_{pd}$  is the propagation delay in each flip-flop, then, in a counter with  $N$  flip-flops having a modulus of less than or equal to  $2^N$ , the maximum usable clock frequency is given by  $f_{max} = 1/(N \times t_{pd})$ . Often, two propagation delay times are specified in the case of flip-flops, one for **LOW-to-HIGH** transition ( $t_{PLH}$ ) and the other for **HIGH-to-LOW** transition ( $t_{PHL}$ ) at the output. In such a case, the larger of the two should be considered for computing the maximum clock frequency. As



an example, in the case of a ripple counter *IC* belonging to the low-power Schottky *TTL (LSTTL)* family, the propagation delay per flip-flop typically is of the order of *25 ns*. This implies that a four-bit counters and from this logic family cannot be clocked faster than *10 MHz*. The upper limit on the clock frequency further decreases with increase in the number of bits to be handled by the counter.

To make these counters do as sequential circuits then the flip-flops must be in a toggle case, for example D flip-flop can be in a toggle case as shown in figure (1):

 


Fig 1 Toggle D flip-flop

For T flip-flop, the toggle operation can be achieved easily by entered logic 1 to the input of T flip-flop as illustrated in figure (2) and for J-K flip-flop; the same modification can be used as shown in figure (3).

 


Fig 2 Toggle T flip-flop

 


Fig 3 Toggle J-K flip-flop

The design steps of sequential counters are:

- Number of flip-flops is equal to the largest bits of the required state.
- All flip-flops must be in a toggle case.
- For up-counters, the  $\bar{Q}$  output of the first flip-flop is used as a clock pulse for the second flip and so on, when the flip-flops respond to the positive edge of the clock pulse.
- For down-counters, , the  $Q$  output of the first flip-flop is used as a clock pulse for the second flip and so on, when the flip-flops respond to the positive edge of the clock pulse.
- The third and four steps are opposite, when the flip-flops respond to the negative edge of the clock pulse.

Ex1/ design up asynchronous counter has the following sequence (00, 01, 10, and 11) using J-K flip-flops with positive edge clock pulse.

Sol:

 



Fig 4 Two bits up counter



Ex2/for the circuit shown in figure (4), draw the timing diagram and truth table.

Sol:

<u>B</u>	<u>A</u>	<u>Output</u>
0	0	0
0	1	1
1	0	2
1	1	3

 

HW<sub>1</sub>: design (*3-bits*) up counter using *J-K* flip-flops with negative edge clock pulse.

Ex3/ design (*3-bits*) down counter using *J-K* flip-flops with positive edge clock pulse.

Sol:


 


Fig 5 Three bits down counter

 

Ex4/ draw the timing diagram and truth table of the counter shown in figure (5).

Sol:



<u>C</u>	<u>B</u>	<u>A</u>	<u>Output</u>
1	1	1	7
1	1	0	6
1	0	1	5
1	0	0	4
0	1	1	3
0	1	0	2
0	0	1	1
0	0	0	0

Ex5/ design a (*3-bits*) down counter using T flip-flops with negative edge clock pulse, draw the timing diagram and truth table for this counter.

Sol:


 


Fig 6 (3-bits) T down counter

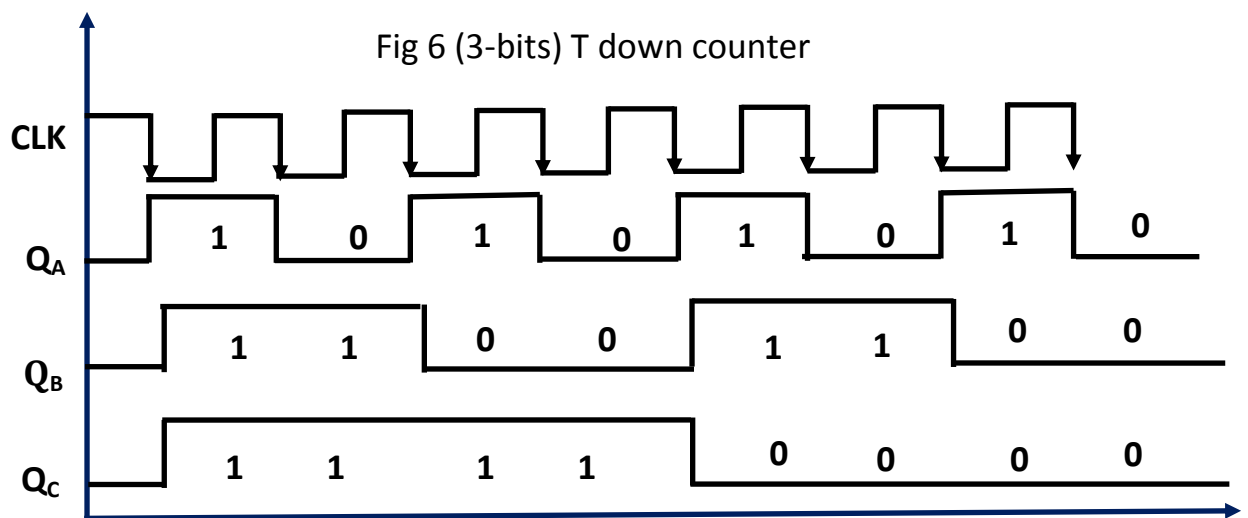

<u>C</u>	<u>B</u>	<u>A</u>	<u>Output</u>
0	0	0	0
1	1	1	7
1	1	0	6
1	0	1	5
1	0	0	4
0	1	1	3
0	1	0	2
0	0	1	1
0	0	0	0



HW<sub>2</sub>: design a (**3-bits**) up counter using *T* flip-flops with negative edge clock pulse, draw the timing diagram and truth table for this counter.

HW<sub>3</sub>: design a (**4-bits**) up counter using *D* flip-flops with negative edge clock pulse, draw the timing diagram and truth table for this counter.

HW<sub>4</sub>: design a (**2-bits**) down counter using *D* flip-flops with negative edge clock pulse, draw the timing diagram and truth table for this counter.

**Important Note:** to design up-down counter at the same time, enable element can be used with the circuit shown in figure (7).

 


Fig 7 up-down counter enable circuit

Ex6/ design (**4-bits**) up-down counter using *J-K* flip-flops with positive edge clock pulse.

Sol:

 


Fig 8 Three bits up-down counter





❖ **Maximum Count (N)**

The maximum count of the counter is related to the number of (flip-flops) that build the counter which can be expressed as:

$$N = 2^n - 1$$

For example for four flip-flops, the maximum count is  $N = 2^4 - 1 = 15$  which equivalent to (1111) in binary system.

❖ **Modulus Counters**

This type of counters is used when the application needs certain count such as to (1001). These counters are build by controlling the clear element of the flip-flops thus when reach the required count clear all flip-flops of the counter.

Ex7/ design (*Mod 5*) up counter using T flip-flops using **AND** gate as control element.

Sol:

The truth table of this counter is

<u>C</u>	<u>B</u>	<u>A</u>	<u>COUNT</u>
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
0	0	0	0

 


Fig 9 (Mod 5) T up counter

HW<sub>5</sub>: design a (*Mod8*) up counter using *D* flip-flops with negative edge clock pulse, use **AND** gate as a control unit. Draw the timing diagram and truth table for this counter.

Ex8/ design Mod (6) (JK) up counter using NAND gate as a control element.

Sol:

the truth table of this counter is

<u>C</u>	<u>B</u>	<u>A</u>	<u>COUNT</u>
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
0	0	0	0

 


Fig 10(Mod 6) T up counter

HW<sub>6</sub>: design a (*Mod11*) up counter using *T* flip-flops with negative edge clock pulse, use **NAND** gate as a control unit. Draw the timing diagram and truth table for this counter.

### ❖ Synchronous counters

Synchronous counters are different from asynchronous (ripple) counters in that clock pulses are applied to the inputs of all flip-flops. A common clock triggers all flip-flops simultaneously, rather than one at a time in succession as in a ripple counter, the decision whether a flip-flop is to be complemented is determined from the values of the data inputs, such as *T* or *J* and *K* at the time of the clock edge. If  $T = 0$  or  $J = K = 0$ , the flip-flop doesn't change state. If  $T = 1$  or  $J = K = 1$ , the flip-flop complements. Synchronous counters are:

- 1- Use interconnected flip-flops, but all are clocked together by the system clock.
- 2- Use the outputs from the flip-flops, to determine the next states of the following flip-flops (rather than simply clocking them)



- 3- Require no settling time due to rippling (as all flip-flops are clocked synchronously)
- 4- Need designing, to determine how the present state of the circuit must be used to determine the next state (i.e. count)
- 5- Usually need more logic gates for their implementation.

To design the synchronous counters the following steps must be applied:

- ☒ Find the number of flip-flops that used in the design of the counter which can be found from the following equation

$N = 2^n$ , where  $N$  is the maximum count and  $n$  represent the number of flip-flops.

- ☒ Draw the excitation table for the flip-flop that used in the design of this counter.
- ☒ Find the equations of the flip-flops inputs depending on the required counts and excitation table using *K-Maps*.
- ☒ Draw the state diagram.
- ☒ Finally draw the logic circuit of the counter.

Ex9/ design (*3bits*) synchronous up counter using (*SR* flip-flops)

Sol: the excitation table of *SR* flip-flop is

$Q_t$	$Q_{t+1}$	$S$	$R$
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

To find the equations of *SR* of each flip-flop the following table must be used.





Lecture one:  
Counters



Asst. Lec. Hussien  
Y. Radhi

<u>C</u>	<u>B</u>	<u>A</u>	<u>S<sub>A</sub></u>	<u>R<sub>A</sub></u>	<u>S<sub>B</sub></u>	<u>R<sub>B</sub></u>	<u>S<sub>C</sub></u>	<u>R<sub>C</sub></u>
0	0	0	1	0	0	X	0	X
0	0	1	0	1	1	0	0	X
0	1	0	1	0	X	0	0	X
0	1	1	0	1	0	1	1	0
1	0	0	1	0	0	X	X	0
1	0	1	0	1	1	0	X	0
1	1	0	1	0	X	0	X	0
1	1	1	0	1	0	1	0	1

    From the previous table, it is clear that  $S_A = \bar{A}$  &  $R_A = A$ . To find other inputs, *K-Maps* can be used as follow:



The state diagram of this sequence is

 
 


Fig 11 *3bits SR* synchronous up counter using

HW<sub>7</sub>: design a synchronous (*4bits*) down counter using *D* flip-flops with negative edge clock pulse.

HW<sub>8</sub>: design (*2bits*) up-down counter using *JK* flip-flops with positive edge clock pulse.

HW<sub>9</sub>: using *T* flip-flops to design (*3bits*) down counter with negative edge clock pulse.

Ex 10 / design (*3bits*) counter, that counts only even numbers, using *T* flip-flops with negative edge clock pulse.

Sol: the excitation table of *T* flip-flop is

Lecture one:  
Counters



Asst. Lec. Hussien  
Y. Radhi

$Q_t$	$Q_{t+1}$	$T$
0	0	0
0	1	1
1	0	1
1	1	0


Now T inputs of each flip-flop can be found from the following table

$C$	$B$	$A$	$T_A$	$T_B$	$T_C$
0	0	0	0	1	0
0	1	0	0	1	1
1	0	0	0	1	0
1	1	0	0	1	1

From above  $T.T$ ,  $T_A = 0$  &  $T_B = 1$

		$CB$			
		$\bar{C}\bar{B}$	$\bar{C}B$	$CB$	$C\bar{B}$
$A$	$\bar{A}$	0	1	1	0
	$A$	X	X	X	X

$$T_C = B$$

 

 


Fig 14 3bits T that counts only even numbers

HW<sub>10</sub>: design (**3bits**) counter that counts only odd numbers, using *D* flip-flops with positive edge clock pulse.

HW<sub>11</sub>: design (**4bits**) counter that counts only primary numbers, using *JK* flip-flops with positive edge clock pulse.

Ex11/ design a counter that have the following counts (**0, 2, 6, 9, 7, and 3**) using *D* flip-flops with negative edge clock pulse.

Sol: the excitation table of *D* flip-flop is

$Q_t$	$Q_{t+1}$	$D$
0	0	0
0	1	1
1	0	0
1	1	1



Lecture one:  
Counters



Asst. Lec. Hussien  
Y. Radhi

<u>D</u>	<u>C</u>	<u>B</u>	<u>A</u>	<u>D<sub>A</sub></u>	<u>D<sub>B</sub></u>	<u>D<sub>C</sub></u>	<u>D<sub>D</sub></u>
0	0	0	0	0	1	0	0
0	0	1	0	0	1	1	0
0	1	1	0	1	0	0	1
1	0	0	1	1	1	1	0
0	1	1	1	1	1	0	0
0	0	1	1	0	0	0	0

DC BA		DC			
		$\bar{D}\bar{C}$	$\bar{D}C$	$DC$	$D\bar{C}$
$\bar{B}\bar{A}$	0	X	X	X	
$\bar{B}A$	X	X	X	1	
$BA$	0	1	X	X	
$B\bar{A}$	0	1	X	X	

$$D_A = D + C$$

DC BA		DC			
		$\bar{D}\bar{C}$	$\bar{D}C$	$DC$	$D\bar{C}$
$\bar{B}\bar{A}$	1	X	X	X	
$\bar{B}A$	X	X	X	1	
$BA$	0	1	X	X	
$B\bar{A}$	1	0	X	X	


$$D_B = D + AC + \bar{A}C$$

DC BA		DC			
		$\bar{D}\bar{C}$	$\bar{D}C$	$DC$	$D\bar{C}$
$\bar{B}\bar{A}$	0	X	X	X	
$\bar{B}A$	X	X	X	1	
$BA$	0	0	X	X	
$B\bar{A}$	1	0	X	X	

$$D_C = D + B\bar{A}C$$

DC BA		DC			
		$\bar{D}\bar{C}$	$\bar{D}C$	$DC$	$D\bar{C}$
$\bar{B}\bar{A}$	0	X	X	X	
$\bar{B}A$	X	X	X	0	
$BA$	0	0	X	X	
$B\bar{A}$	0	1	X	X	

$$D_D = \bar{A}C$$

 

 


Fig.15 (0, 2, 6, 9, 7, 3 D counter

HW<sub>12</sub>: design a (*JK*) synchronous counter that has the counts (0, 5, 4, and 7) with positive edge clock pulse.

HW<sub>13</sub>: design (*T*) synchronous counter that has the counts (5, 10, 12, 0, 1, and 6).

### ❖ Shift Register Counters

We have seen that both counters and shift registers are some kinds of cascade arrangement of flip-flops. A shift register, unlike a counter, has no specified sequence of states. However, if the serial output of the shift register is fed back to the serial input, we do get a circuit that exhibits a specified sequence of states. The resulting circuits are known as shift register counters. Depending upon the nature of the feedback, we have two types of shift register counter, namely the ring counter and the shift counter, also called the Johnson counter. These are briefly described in the following paragraphs.



### 1- Ring Counter

A ring counter is obtained from a shift register by directly feeding back the true output of the output flip-flop to the data input terminal of the input flip-flop. If  $D$  flip-flops are being used to construct the shift register, the ring counter, also called a circulating register, can be constructed by feeding back the  $Q$  output of the output flip-flop back to the  $D$  input of the input flip-flop. If  $JK$  flip-flops are being used, the  $Q$  and  $\bar{Q}$  outputs of the output flip-flop are respectively fed back to the  $J$  and  $K$  inputs of the input flip-flop. Figure 11.45 shows the logic diagram of a four-bit ring counter. Let us assume that flip-flop  $FF0$  is initially set to the logic '1' state and all other flip-flops are reset to the logic '0' state. The counter output is therefore  $1000$ . With the first clock pulse, this '1' gets shifted to the second flip-flop output and the counter output becomes  $0100$ . Similarly, with the second and third clock pulses, the counter output will become  $0010$  and  $0001$ . With the fourth clock pulse, the counter output will again become  $1000$ . The count cycle repeats in the subsequent clock pulses. Circulating registers of this type find wide application in the control section of microprocessor-based systems where one event should follow the other. The timing waveforms for the circulating register of Figure (16), as shown in Figure (17), further illustrate their utility as a control element in a digital system to generate control pulses that must occur one after the other sequentially.

 


Fig 16 four bits D ring counter

 


Fig 17 Timing diagram of four bits D ring counter

## 2- Shift Counter

A shift counter on the other hand is constructed by having an inverse feedback in a shift register. For instance, if we connect the  $Q$  output of the output flip-flop back to the  $K$  input of the input flip-flop and the  $Q$  output of the output flip-flop to the  $J$  input of the input flip-flop in a serial shift register, the result is a shift counter, also called a Johnson



counter. If the shift register employs  $D$  flip-flops, the  $Q$  output of the output flip-flop is fed back to the  $D$  input of the input flip-flop. If  $RS$  flip-flops are used, the  $Q$  output goes to the  $R$  input and the  $Q$  output is connected to the  $S$  input. Figure 37 shows the logic diagram of a basic four-bit shift counter. Let us assume that the counter is initially reset to all  $0s$ . With the first clock cycle, the outputs will become  $1000$ . With the second, third and fourth clock cycles, the outputs will respectively be  $1100$ ,  $1110$  and  $1111$ . The fifth clock cycle will change the counter output to  $0111$ . The sixth, seventh and eighth clock pulses successively change the outputs to  $0011$ ,  $0001$  and  $0000$ . Thus, one count cycle is completed in eight cycles. Figure (18) shows the timing waveforms. Different output waveforms are identical except for the fact that they are shifted from the immediately preceding one by one clock cycle. Also, the time period of each of these waveforms is  $8$  times the period of the clock waveform. That is, this shift counter behaves as a divide-by- $8$  circuit. In general, a shift counter comprising  $n$  flip-flops acts as a divide-by- $2n$  circuit. Shift counters can be used very conveniently to construct counters having a modulus other than the integral power of  $2$ .

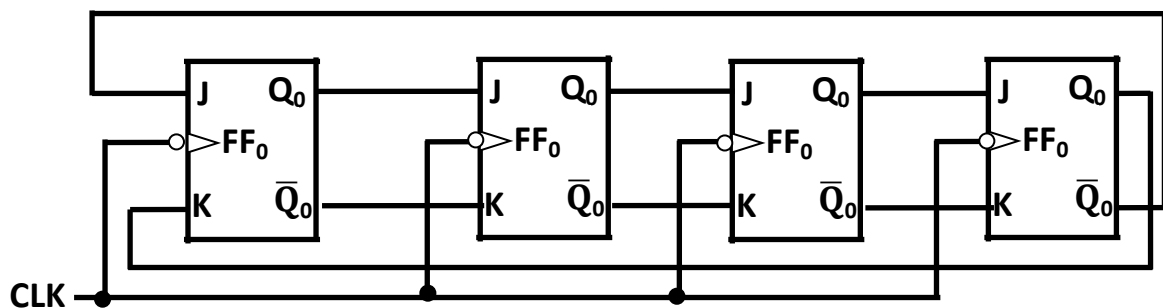


Fig18 Four-bit shift counter



❖ **Cascading counters:**

This technique is used to obtain higher modulus operation, in this technique; the last stage output of one counter derives the input of the next counter.

**1- Asynchronous cascading**

When two (*2bits*) asynchronous counters, the overall modulus of the two cascaded counters is  $4*4 = 16$  that act as a divided- by-*16* counter. The logic cct. of this cascaded counter with its timing diagram is given in figure (19).

 


Fig 19 Two bits cascaded counter with its timing diagram



## 2- Synchronous counters

In this type of cascading counters, the output of final stage is called the terminal count ( $TC$ ) which entered into next counter, which represent the count enable input ( $CTEN$ ). By connecting two mod 10 counters as shown in figure (20) then for every ten cycles of counter one, counter two goes through one cycle. Thus, counter two will complete one cycle after one hundred clock pulses. The overall modulus of these two-cascaded counters is  $10 \times 10 = 100$ . Therefore, this technique is used as frequency divider.

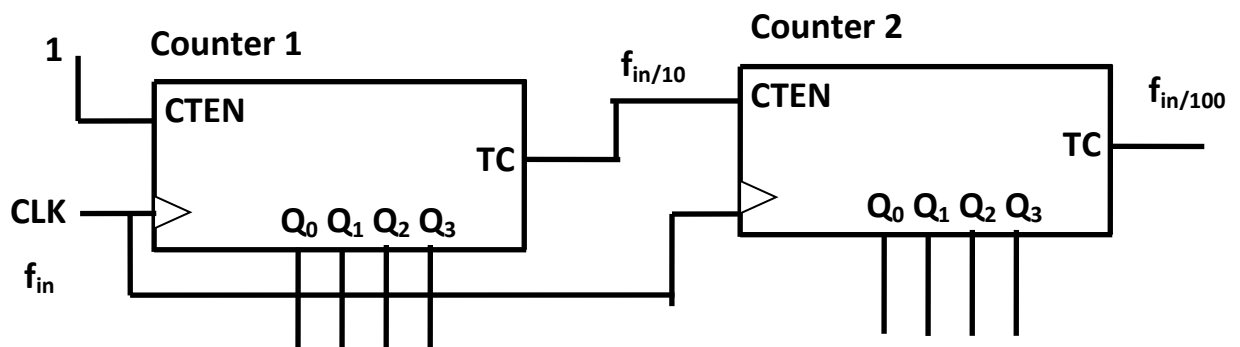


Fig 20 two mod 10 cascaded counters

Ex12/ how many-cascaded decade counters that required to divide a clock frequency by  $10000$ .

Sol: using four mod 10 counters then each one of them divides by 10 then the overall frequency division is  $(f_{in}/10000)$ .

### Note:

Some applications do not require full modulus cascaded counter instead, it needs truncated sequences. To achieve the truncated cascaded counters consider the following steps:



- ✚ From the required sequence, find the number of counters for the cascaded counter.
- ✚ Subtract the required state from the full modulus states.
- ✚ Convert the difference state to binary system.
- ✚ Load these binary numbers equally to each counter to preset these counters to difference state and count to the full state and obtain the required state.

Ex13/ design a cascaded counter divided by 3000 using 74HC161 four bits counter only. Where 74HC161 is shown in figure (15).

 


Fig 21 74HC161 four bit counter

Sol: Since the required state is 3000, then three 74HC161 4-bits counters can be used.

$$\text{Full state} = 16 * 16 * 16$$

$$= 4096$$

$$\text{Difference state} = \text{full state} - \text{required state}$$

$$= 4096 - 3000$$

$$= (1096)_{\text{Dec}}$$

$$= (448)_{\text{Hex}}$$





This means that the first counter is loaded by (1000), the second counter is loaded by (0100), and the third one is loaded by (0100). The logic block diagram of such cascaded truncated counter is given in figure (22).

 


Fig 22 Cascaded counter divided by 3000 using 74HC161 4-bits counters

HW<sub>13</sub>: use 74HC161 4-bits counters to design a divide-by-1000 counter (modulus 1000)

**Note:**

Sometimes the cascaded counters are not working properly, in this case the following steps are considered:

- Calculate the truncated modulus
- From the truncated modulus find the correct frequency
- Find the modulus of the counter
- According to the modulus of the counter, the preset count must be calculated.
- Redesign the counter for the new preset count

Ex14/ determine if the cascaded counter shown in figure (23) is working properly or not. If not, make it work in correct way.

Sol: from figure (23), it is found that






Ex17/ implement the decoding of binary state (2) of a  $JK$  synchronous counter. Draw the timing diagram and the outputs waveforms of the coding gate.


Sol: use the following table to find JK inputs of each flip-flop

$\underline{B}$	$\underline{A}$	$\underline{J}_A$	$\underline{K}_A$	$\underline{J}_B$	$\underline{K}_B$
0	0	0	X	1	X
0	1	1	X	X	1
1	0	X	0	1	X
1	1	X	1	X	1

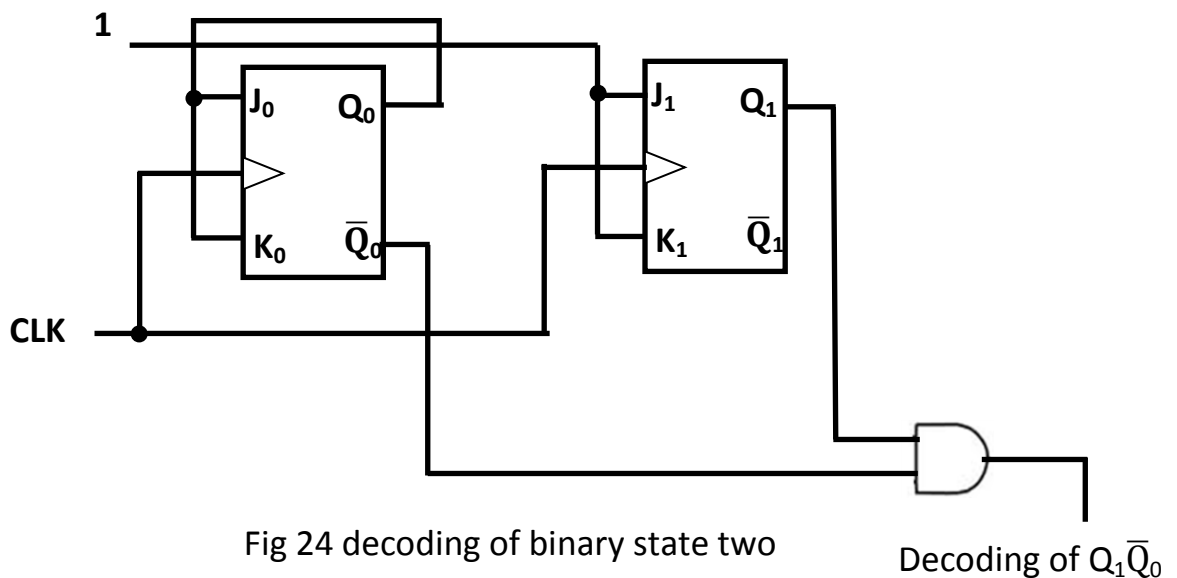From this table it is found that  $J_B = K_B = 1$  &  $J_A = K_A = A$  then the logic block circuit will be as shown in figure (24)



 The timing diagram of this counter is given below



HW<sub>14</sub>: implement the logic for the decoding states  $\mathcal{B}$  in the (4bits)  $D$  synchronous counter.

### ❖ Counter applications

The counters are useful in more digital applications and devices, some of the counters applications are:

#### 1- Digital Clock

The counters can be used as a digital clock system by using the principle of cascading counters. The input  $AC$  voltage with  $60\text{ Hz}$  frequency and the outputs are the seconds, minutes, and hours. This logic circuit consists of

- ✓ Wave shaping circuit.
  - ✓ Synchronous counters divided-by-10 & divided-by-6.
  - ✓ An ( $JK$  flip-flop).
- 2-  $BCD/7$ -segment.
  - 3- Automobile Parking Control
  - 4- Parallel-to-serial data conversion (multiplexing)
  - 5- Frequency divider